


FY BTech
BEEE Lab
Expt No. 8

Based on Unit 6 : AC circuits

R L C Series Resonant Circuit

Inductive reactance Vs frequency

Capacitive reactance Vs frequency

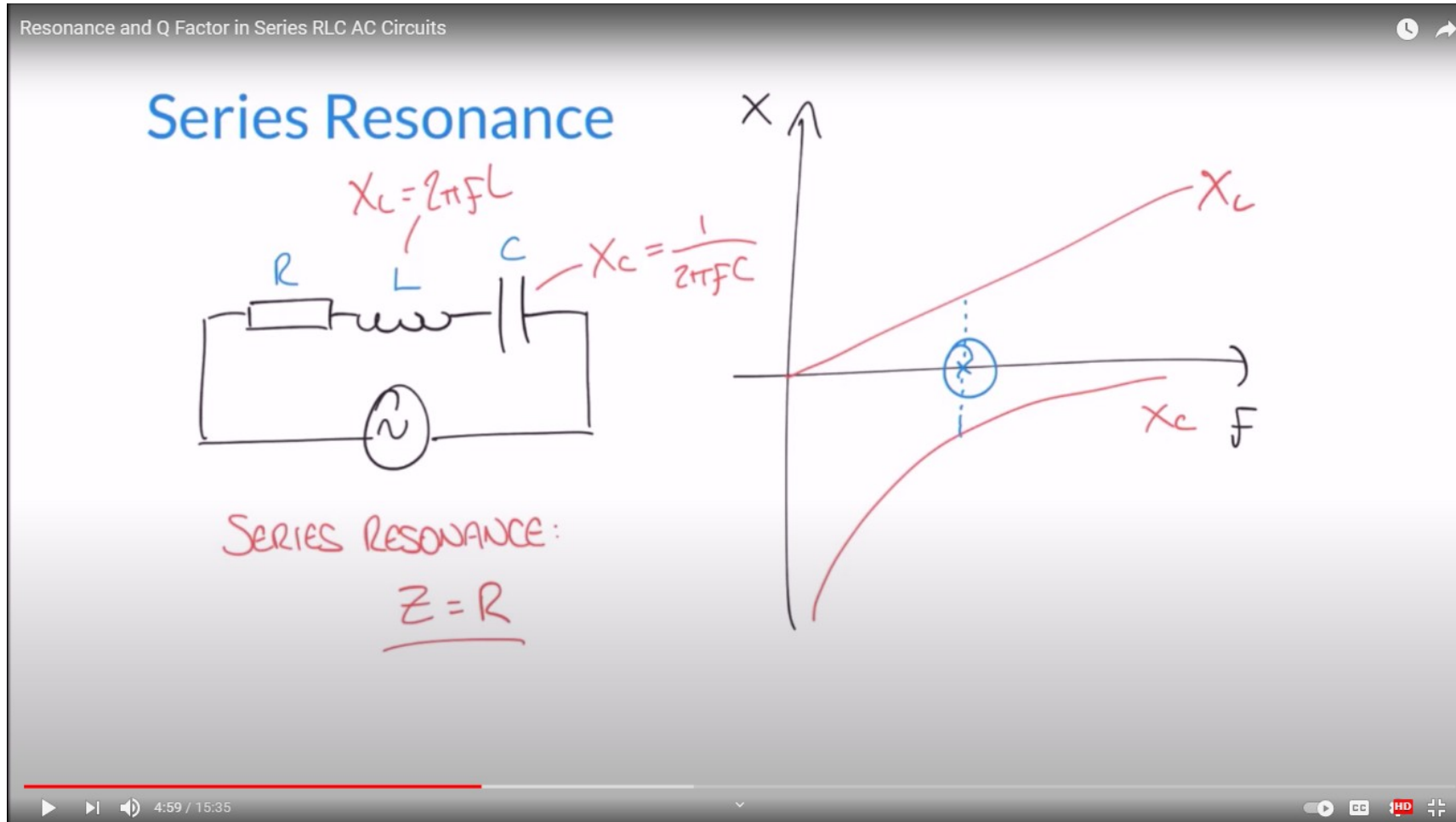

Alternating current in an RLC circuit

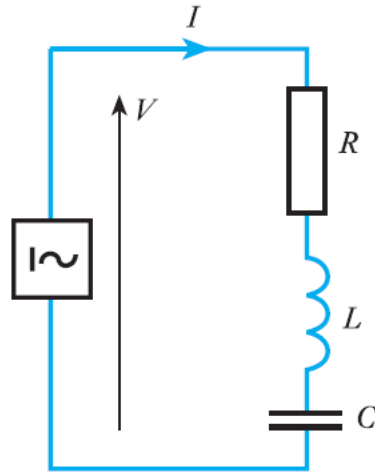


Fig. 10.25 Circuit with R , L and C in series

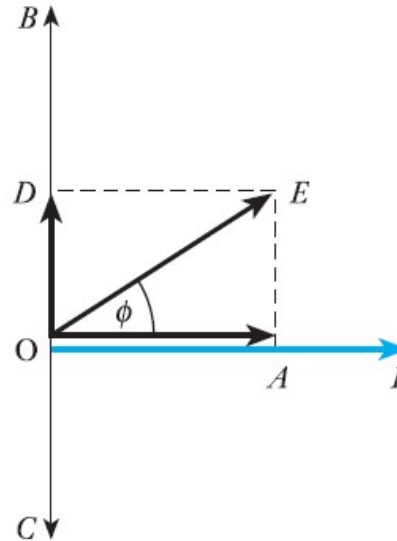


Fig. 10.26 Phasor diagram for Fig. 10.25

$$\begin{aligned}\tan \phi &= \frac{AE}{OA} = \frac{OD}{OA} = \frac{OB - OC}{OA} = \frac{2\pi f L I - I/(2\pi f C)}{R I} \\ &= \frac{\text{inductive reactance} - \text{capacitive reactance}}{\text{resistance}}\end{aligned}$$

\therefore

$$\tan \phi = \frac{X_L - X_C}{R}$$

$$OE^2 = OA^2 + OD^2 = OA^2 + (OB - OC)^2$$

$$\therefore V^2 = (RI)^2 + \left(2\pi f L I - \frac{I}{2\pi f C}\right)^2$$

so that

$$I = \frac{V}{\sqrt{\left\{R^2 + \left(2\pi f L - \frac{1}{2\pi f C}\right)^2\right\}}} = \frac{V}{Z}$$

where $Z = \text{impedance of circuit in ohms}$

$$Z = \frac{V}{I} = \sqrt{\left\{R^2 + \left(2\pi f L - \frac{1}{2\pi f C}\right)^2\right\}}$$

From this expression it is seen that


$$\text{Resultant reactance} = 2\pi f L - \frac{1}{2\pi f C}$$

= inductive reactance – capacitive reactance

Series Resonance




Variation of reactance with frequency

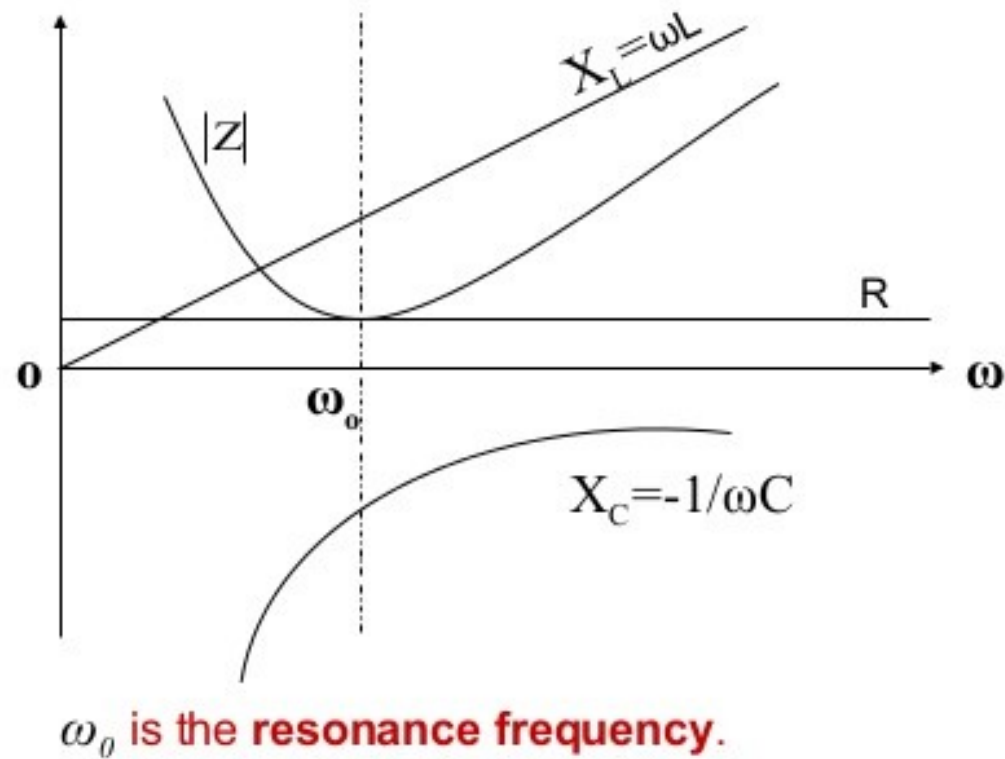

Calculation of resonant frequency

Resonance and Q Factor in Series RLC AC Circuits


Series Resonance

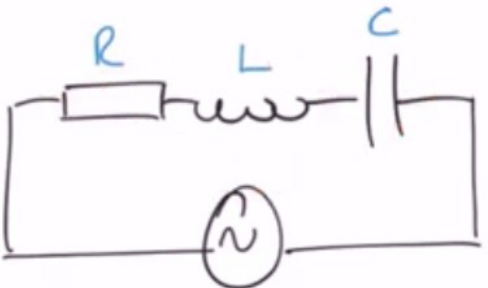
$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$
$$f_0 = \frac{1}{2\pi \times \sqrt{56 \times 10^{-3} \times 7.2 \times 10^{-6}}}$$
$$= 250.65 \text{ Hz}$$


$R = 50 \Omega$
 $L = 56 \text{ mH}$
 $C = 7.2 \mu\text{F}$

7:49 / 15:35


Resonance Curves

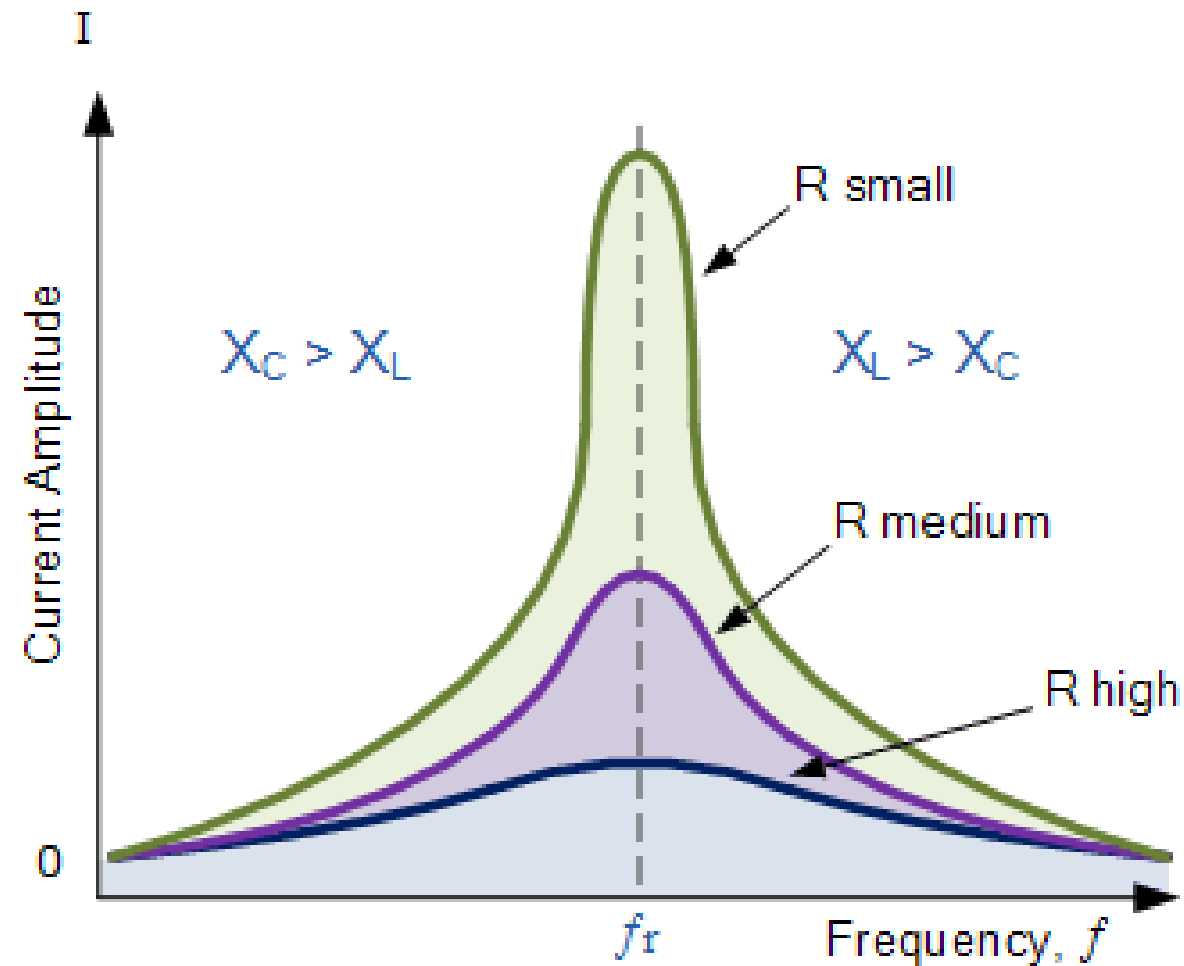


Q Factor

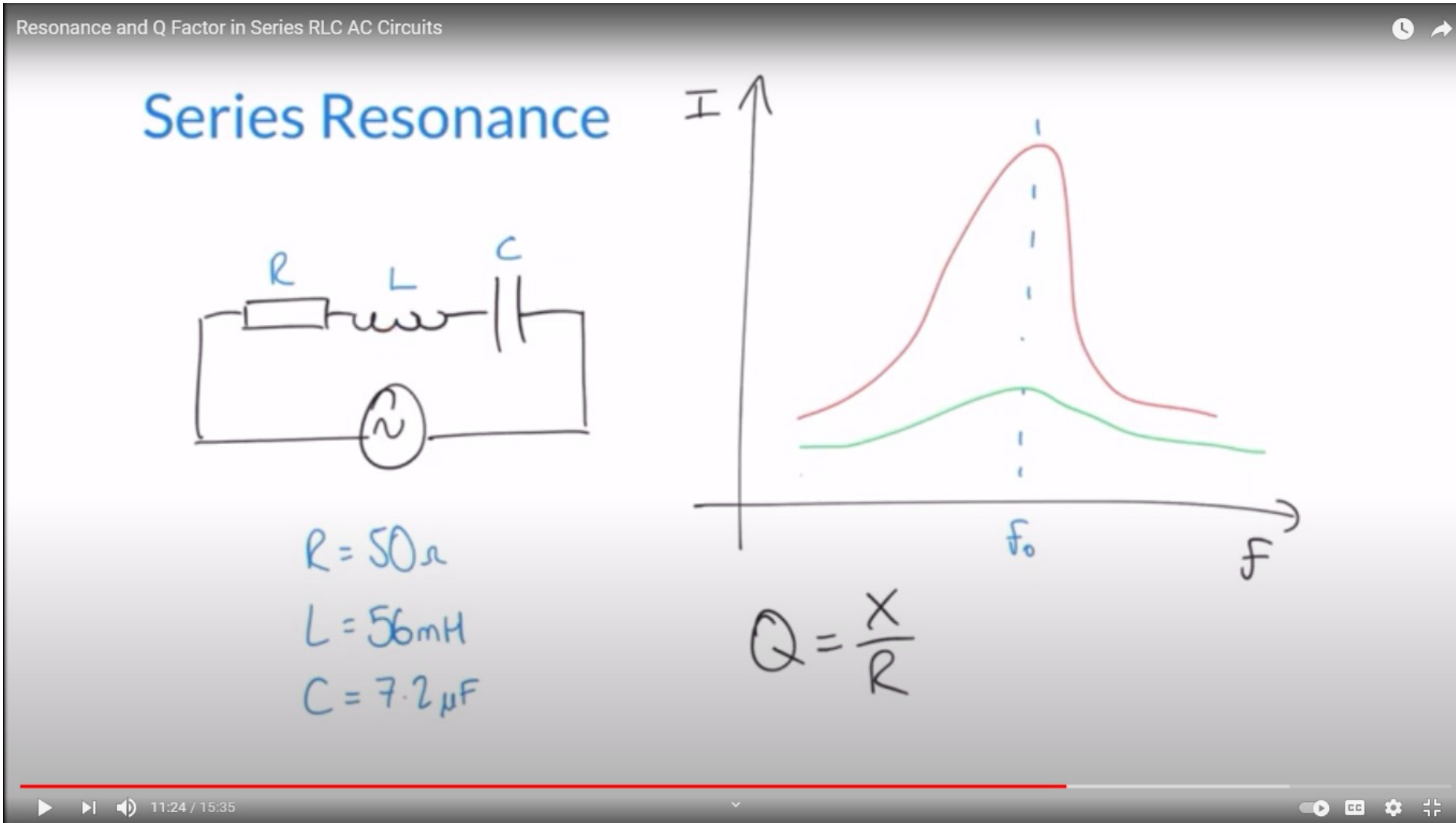

Q Factor

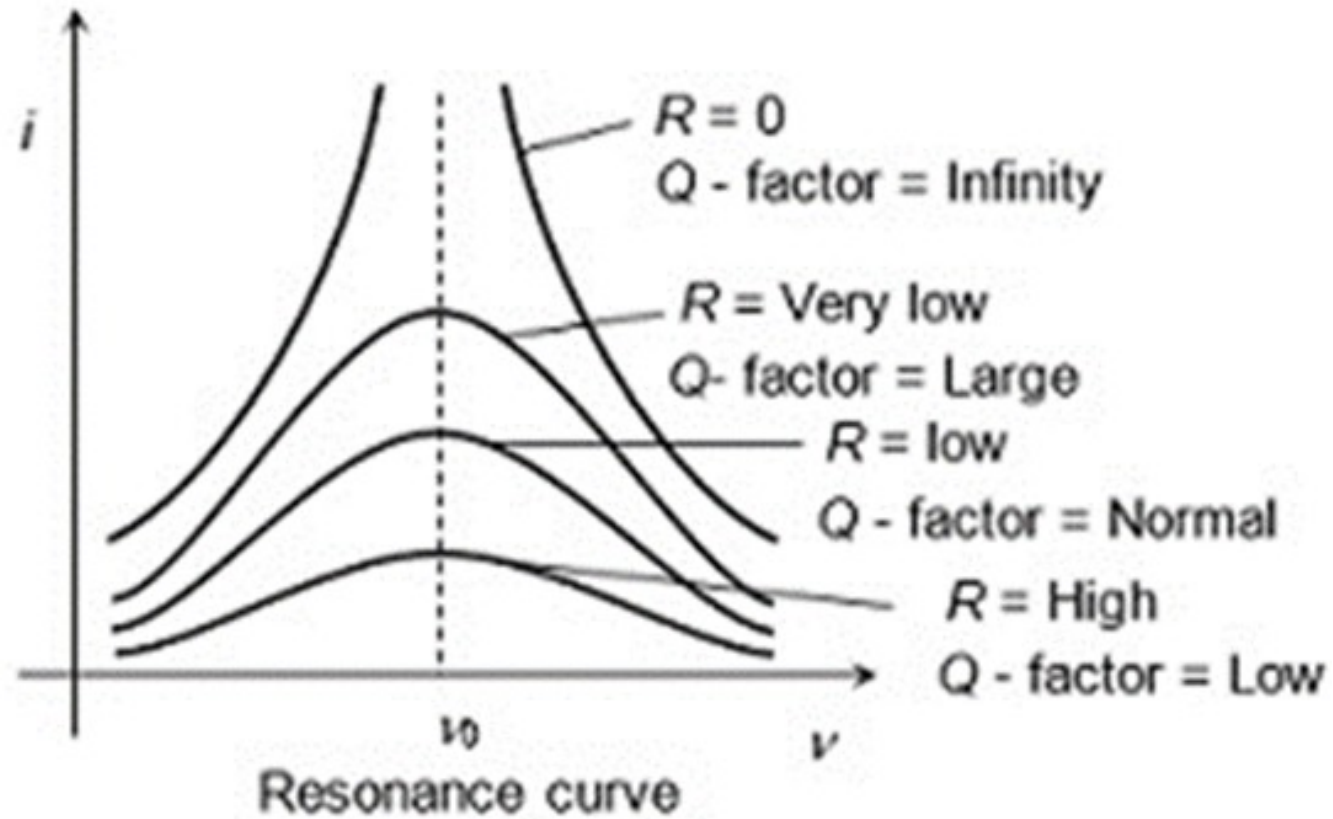

Resonance Curve

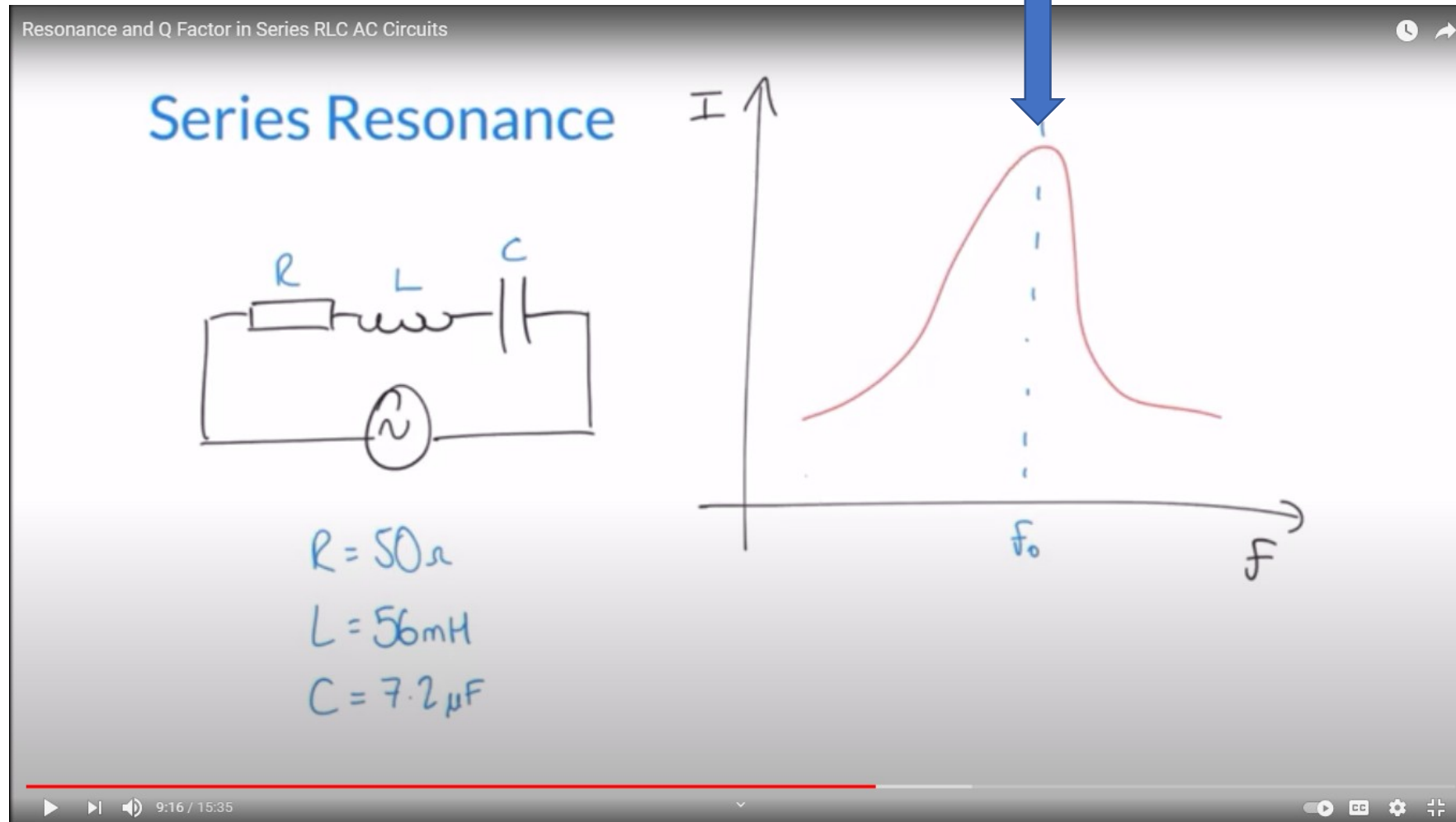

es resonan x

ercad.com/things/fmZEPL76gIC-rlc-series-resonance-cct/editel

es resonance cct

All changes saved

Simulator time: 00:00:00.639

Code

Stop Simulation

Export

Share

AC Voltage Source

1.59 kHz

5.00 V

0.00 V

R_L_C Resonant Circuit

30 ohms

10 mH

1 microF

Voltage across R on CRO

Resonant Frequency= 1592Hz

Function Generator

Name	1	
Frequency	1592	Hz
Amplitude	5	V
DC Offset	0	V
Function	Sine	

Observation Table

Sr. No	Frequency (Hz)	AC Voltage across R (V)
1	800	1
2	900	1.2
3	1000	1.5
4	1100	1.8
5	1300	3.0
6	1400	3.8
7	1500	4.75
8	1600	5
9	1700	4.5
10	2000	2.8
11	2200	2
12	2500	1.5
13	2800	1.2