 Drive

Search in Drive

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

Shared with me &gt; Screenshot

The phase difference between input and output of the common-collector and common-base amplifiers is:

 90 degrees 180 degrees 270 degrees 0 degrees

## Drive

Search in Drive



New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

A certain transistor exhibits an  $\alpha_{DC}$  of 0.96. Determine  $I_C$  when  $I_E = 9.35 \text{ mA}$ .

8.81mA

9.1mA

8.976mA

9.876mA

 Drive

Search in Drive

Tag to Revisit

Sum expression of half adder with inputs A and B is ....

  $A'B + AB'$   $AB$   $A+B$   $AB + A'B$ 

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

## Drive

Search in Drive

Tag to Revisit

A parallel LC network with  $L = 100 \text{ mH}$  and  $C = 25 \mu\text{F}$  will resonate at what frequency?

 25 Hz 100 Hz 45.5 Hz 75.6 Hz 151 Hz 30.4 Hz

New

My Drive

Shared with me

Recent


Starred

Trash

Storage

720.3 MB of 15 GB used


Buy storage

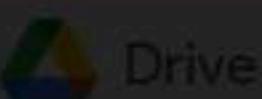

Drive



Search in Drive

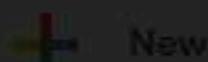

New



My Drive



Shared with me



Recent



Starred



Trash



Storage

720.3 MB of 15 GB used

Buy storage

Shared with me > Snapshot

Tag to Revisit

Compared to a visible red LED, an infrared LED

Reset Next >

Produces light with longer wavelengths

Produces light with shorter wavelengths

Produces light of all wavelengths

Produces only one color of light

## Drive

Search in Drive



New

My Drive

Shared with me

Recent


Starred


Trash

Storage

720.3 MB of 15 GB used

Buy storage

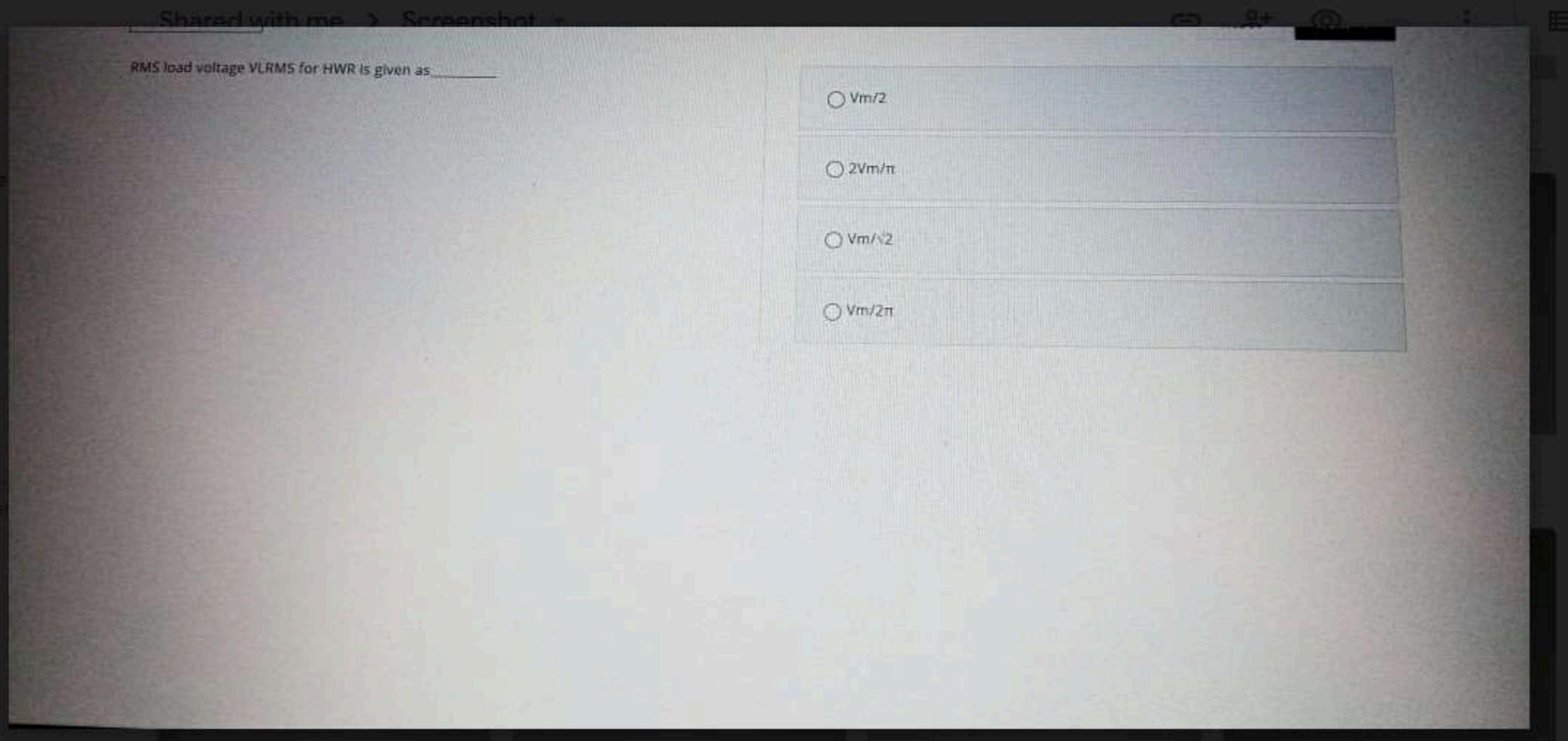

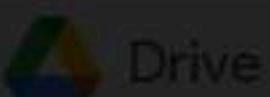

Drive



Search in Drive



Shared with me &gt; Screenshot

Tag to Revisit

Which process of the Electron-hole pair is responsible for emitting of light?

 Diffusion Recombination Movement Generation

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage



Drive



Search in Drive




New




My Drive



Shared with me

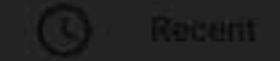

Recent

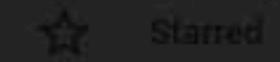

Starred



Trash



Storage

720.3 MB of 15 GB used

Buy storage

A half wave rectifier with  $RL = 1k\Omega$  is given an input of 10 V peak from a step-down transformer. DC load voltage using ideal diode is

3.18V

2.13V

9.18V

5.18V

## Drive



Search in Drive

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

Tag to Revisit

A half wave rectifier with  $R_L = 1k\Omega$  is given an input of 10 V peak from a step-down transformer. DC load voltage using ideal diode is

 9.18 V 2.13 V 3.18 V 5.18 V

## Drive



Search in Drive

New

My Drive

Shared with me

Recent


Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

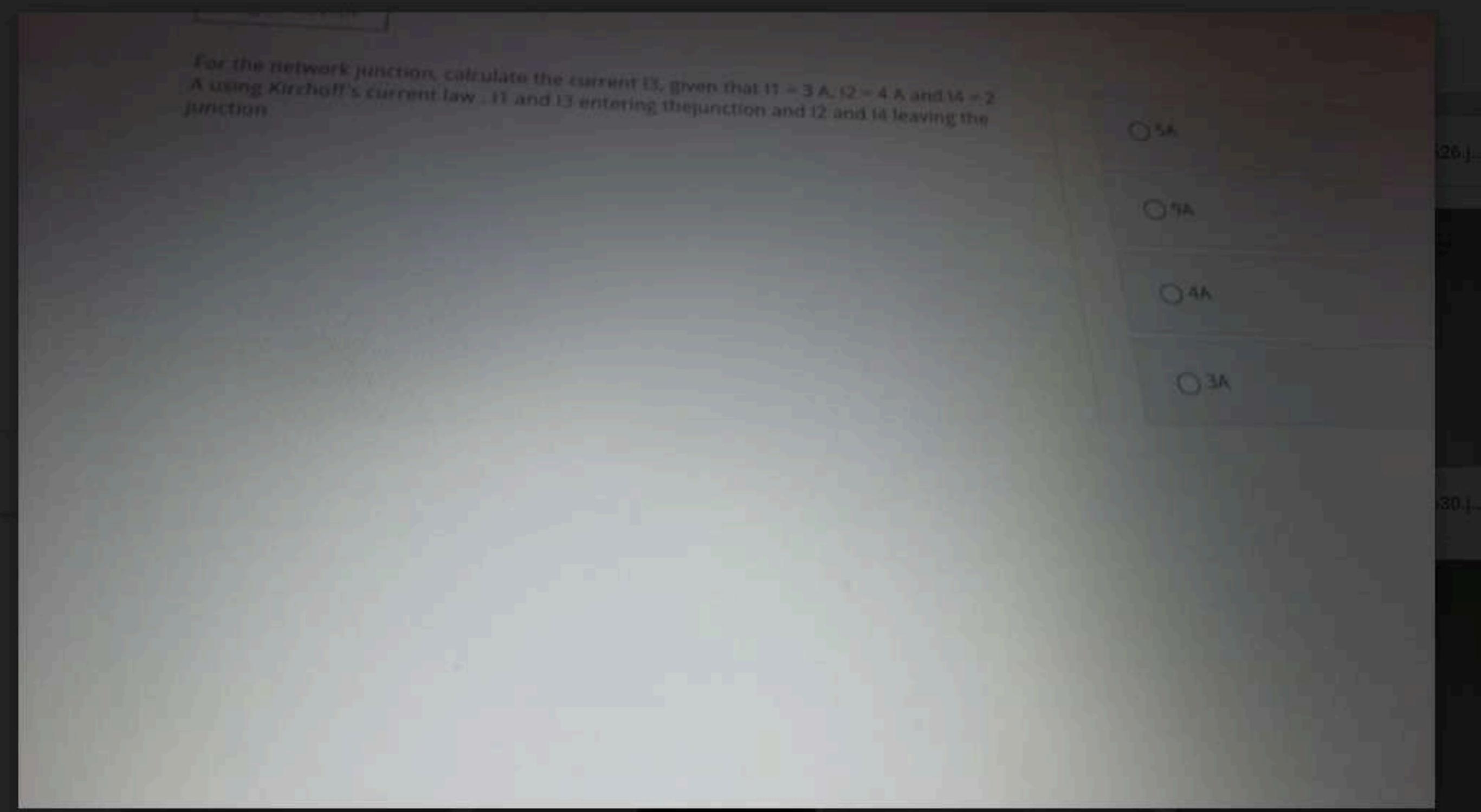

 Drive

Search in Drive

Tag to Revisit

A parallel LC network with  $L = 100 \text{ mH}$  and  $C = 25 \mu\text{F}$  will resonate at what frequency?

 25 Hz 100 Hz 45.5 Hz 75.6 Hz 151 Hz

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

App

Trade at Zerodha - T...

eConnect- Login BP...

Welcome to HDFC...

Home - Union Bank

Search in Drive

Shaverfame &gt; Screenshot

Tag to Revisit

A half wave rectifier with  $RL = 1k\Omega$  is given an input of 10 V peak from a step-down transformer. DC load voltage using ideal diode is

 3.18V 2.13V 9.18V 5.18 V

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

## Drive

Search in Drive

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

47 of 50 answer

Tag to Revisit      Reset      Next >


A certain inverting amplifier has input signal voltage is 10 mVrms, R<sub>1</sub> of 100 kΩ and R<sub>f</sub> of 100 kΩ, find the output voltage.

-10mVrms, out of phase

-10Vrms, out of phase

-10mVrms, in phase

-1Vrms, out of phase

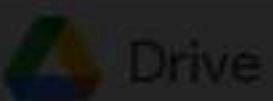

Drive




Search in Drive



New



My Drive

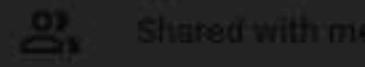

Shared with me




Recent



Starred



Trash

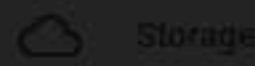

Storage

720.3 MB of 15 GB used

Buy storage

The transistor in CE configuration has a  $V_{BB} = 5V$ ,  $R_B = 15\text{ k}\Omega$  and a  $\beta_{DC} = 100$ , then  $I_C$  equal to:

28 mA

0.028 mA

2.8 mA

50 mA

## Drive



Search in Drive

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

Tag to Revisit

For a Zener diode, its reverse current increases from 30 mA to 45 mA when the Zener voltage changes from 6.7 V to 6.77 V, then its zener resistance is

4.477 Ω

10 Ω

4.667 Ω

50

## Drive

Search in Drive

Tag to Revisit

Reset

Gain-bandwidth product of a practical OP-AMP is...

 1 MHz zero infinite 10 MHz

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

 Drive

Search in Drive

New

My Drive

Shared with me

Recent


Starred


Trash

Storage

720.3 MB of 15 GB used

Buy storage

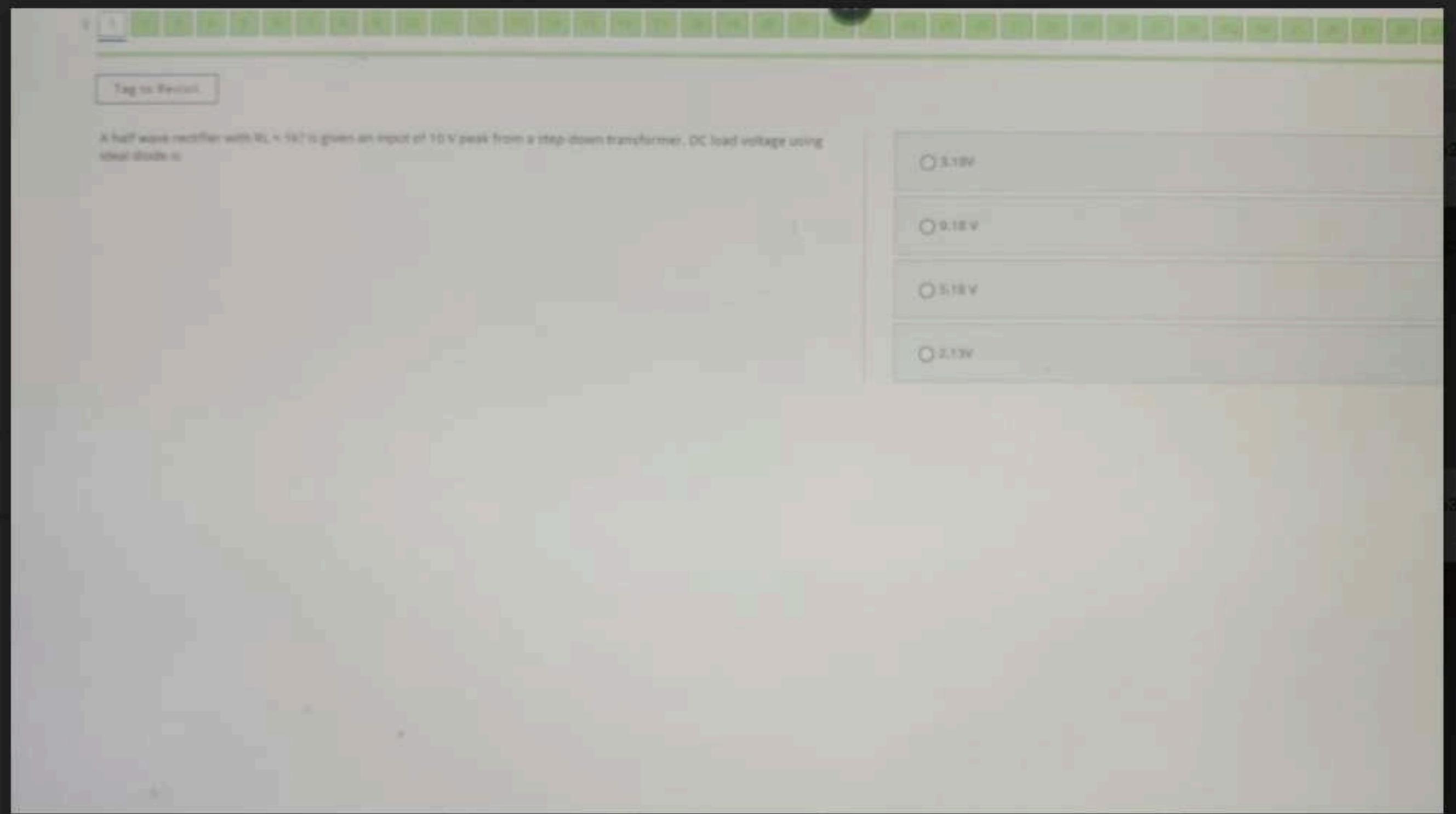

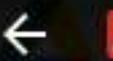

IMG-20210404-WA0744.jpg



Open with ▾



New

My Drive

Shared with me

Recent


Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

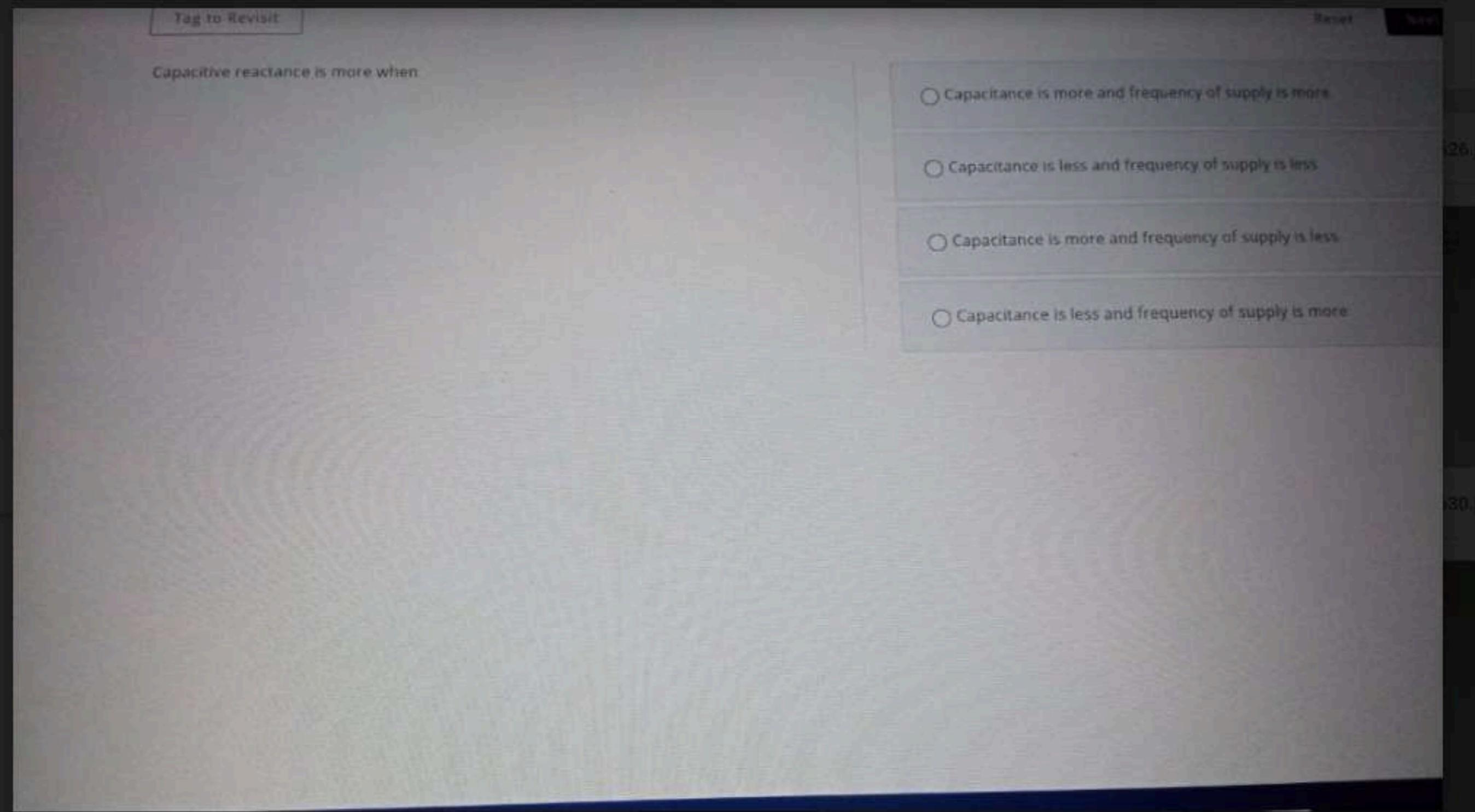

## Drive

Search in Drive

New

My Drive

Shared with me

Recent


Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

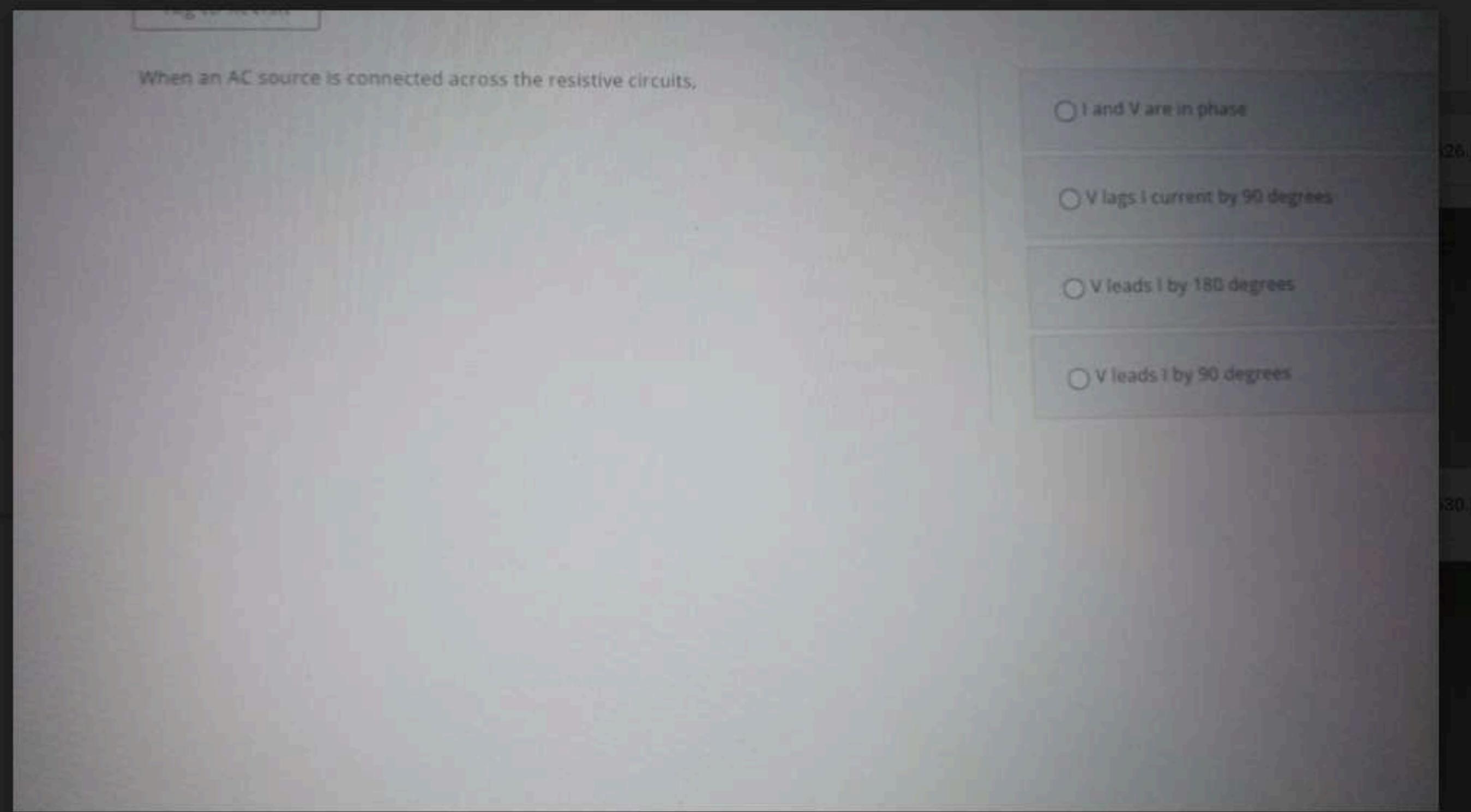

## Drive

Search in Drive

TAG TO REVIEW

The correct expression for generated alternating emf is \_\_\_\_\_

 e=B.I.v.CosΦ e=B.I.v.Sinθ e=B.I.v.SinΦ None

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage



Drive



Search in Drive



New



My Drive



Shared with me



Recent



Starred



Trash



Storage

720.3 MB of 15 GB used

Buy storage

Shared with me &gt; Screenshot

The phase difference between input and output of the common-emitter amplifiers is:

 270 degrees 0 degrees 180 degrees 90 degrees

## Drive



Search in Drive

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

Tag to Revisit

Calculate the effective resistance of parallel combination of  $R_1 = 6.8\ \Omega$ ,  $R_2 = 4.7\ \Omega$  and  $R_3 = 2.2\ \Omega$ .

Reset Next

30 of 50 answers

0.213 ohms

0.815 ohms

0.147 ohms

0.455 ohms

## Drive

Search in Drive

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

Find the total voltage applied in a series RLC circuit when  $I = 3 \text{ mA}$ ,  $V_L = 30 \text{ V}$ ,  $V_C = 18 \text{ V}$  and  $R = 1000 \Omega$ .

 3.95V 6.67V 32.67V 51V

App at Zerodha - T...

eConnect- Login BP...

Welcome to HDFC...

Home - Union Bank

Search in Drive

A silicon transistor connected in common emitter configuration with voltage divider bias is shown in figure. If  $V_{cc} = 10V$ ,  $R_C = 1\text{ k}\Omega$ ,  $R_1 = 100\text{ k}\Omega$ ,  $R_2 = 10\text{ k}\Omega$ ,  $R_E = 100\text{ }\Omega$ . The Q point is at:

 1.8 mA, 6.7V 1.2 mA, 7.8V 2.5 mA, 5.5V 2 mA, 7.8V

## Drive

Search in Drive

If  $R_1 = 2 \Omega$ ,  $R_2 = 4 \Omega$ ,  $R_3 = 8 \Omega$  are connected in series and 2 A current is flowing through the series combination. Voltage drop  $V_{R2} =$

 8V 16V 4V 28V

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used


Buy storage



Drive



Search in Drive

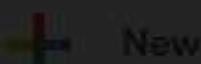

New



My Drive



Shared with me



Recent



Starred



Trash



Storage

720.3 MB of 15 GB used

Buy storage

The ends of a load line drawn on a family of curves determine:

- the operating point
- the power curve
- the amplification factor
- saturation and cutoff

## Drive

Search in Drive

New

My Drive

Shared with me

Recent


Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

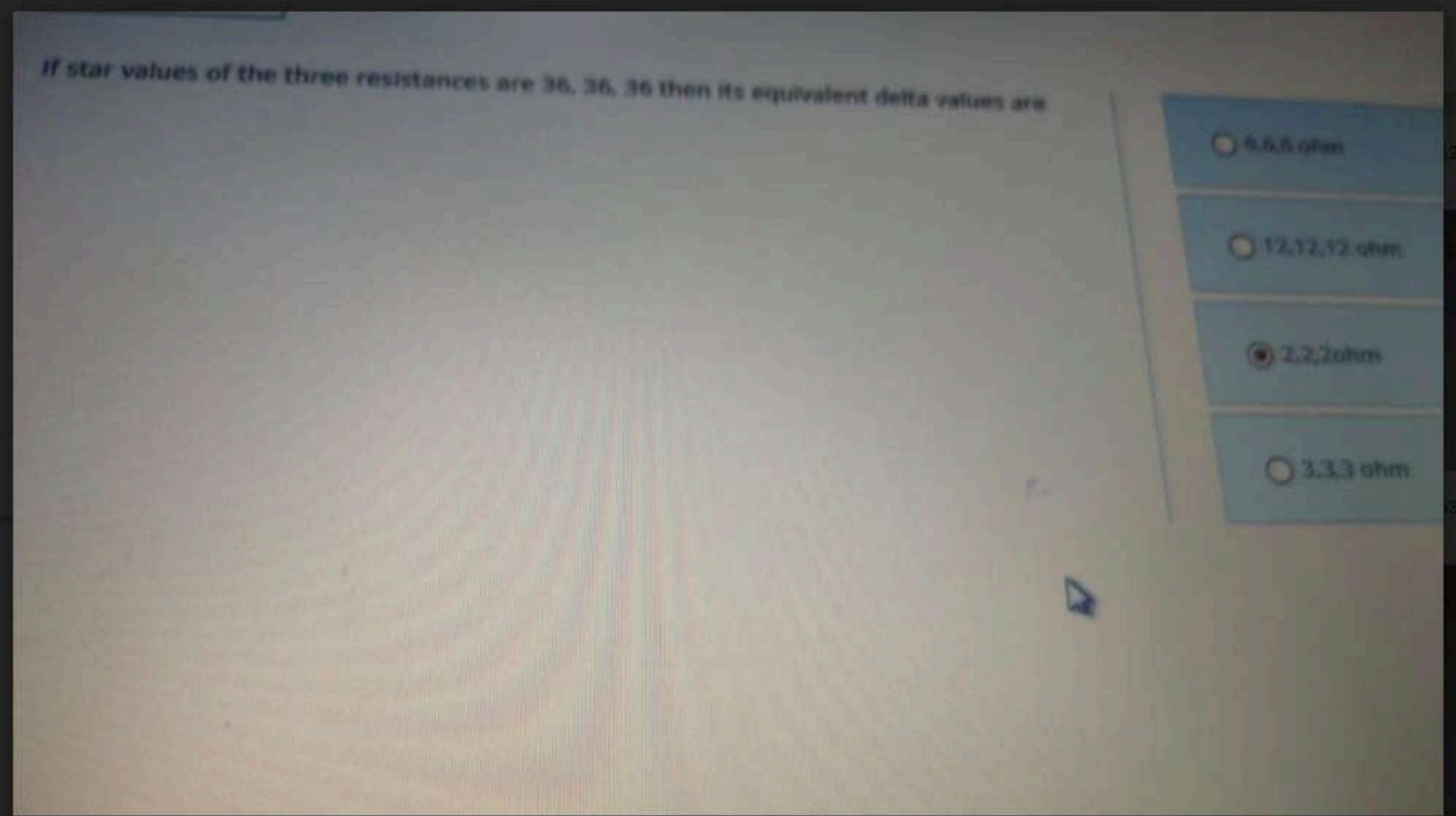

## Drive

Search in Drive



New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

A certain transistor exhibits an  $\alpha_{DC}$  of 0.96. Determine  $I_C$  when  $I_E = 9.35 \text{ mA}$ .

8.81mA

9.1mA

8.976mA

9.876mA

## Drive

Search in Drive

New

My Drive

Shared with me

Recent

Starred

Trash


Storage

720.3 MB of 15 GB used

Buy storage

An ideal transformer will have maximum efficiency at a load such that \_\_\_\_\_

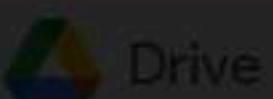- copper loss < iron loss
- cannot be determined
- copper loss = iron loss
- copper loss > iron loss



Drive



Search in Drive



New



My Drive



Shared with me



Recent



Starred



Trash



Storage

720.3 MB of 15 GB used

Buy storage

For a Zener diode, its reverse current increases from 30 mA to 45 mA when the Zener voltage changes from 6.7 V to 6.77 V, then its zener resistance is

10 Ω

4.667 Ω

4.477 Ω

50

## Drive

Search in Drive

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

Shared with me &gt; Screenshot

The phase difference between input and output of the common-collector and common-base amplifiers is:

 90 degrees 180 degrees 270 degrees 0 degrees

## Drive

Search in Drive

New

My Drive

Shared with me

Recent


Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

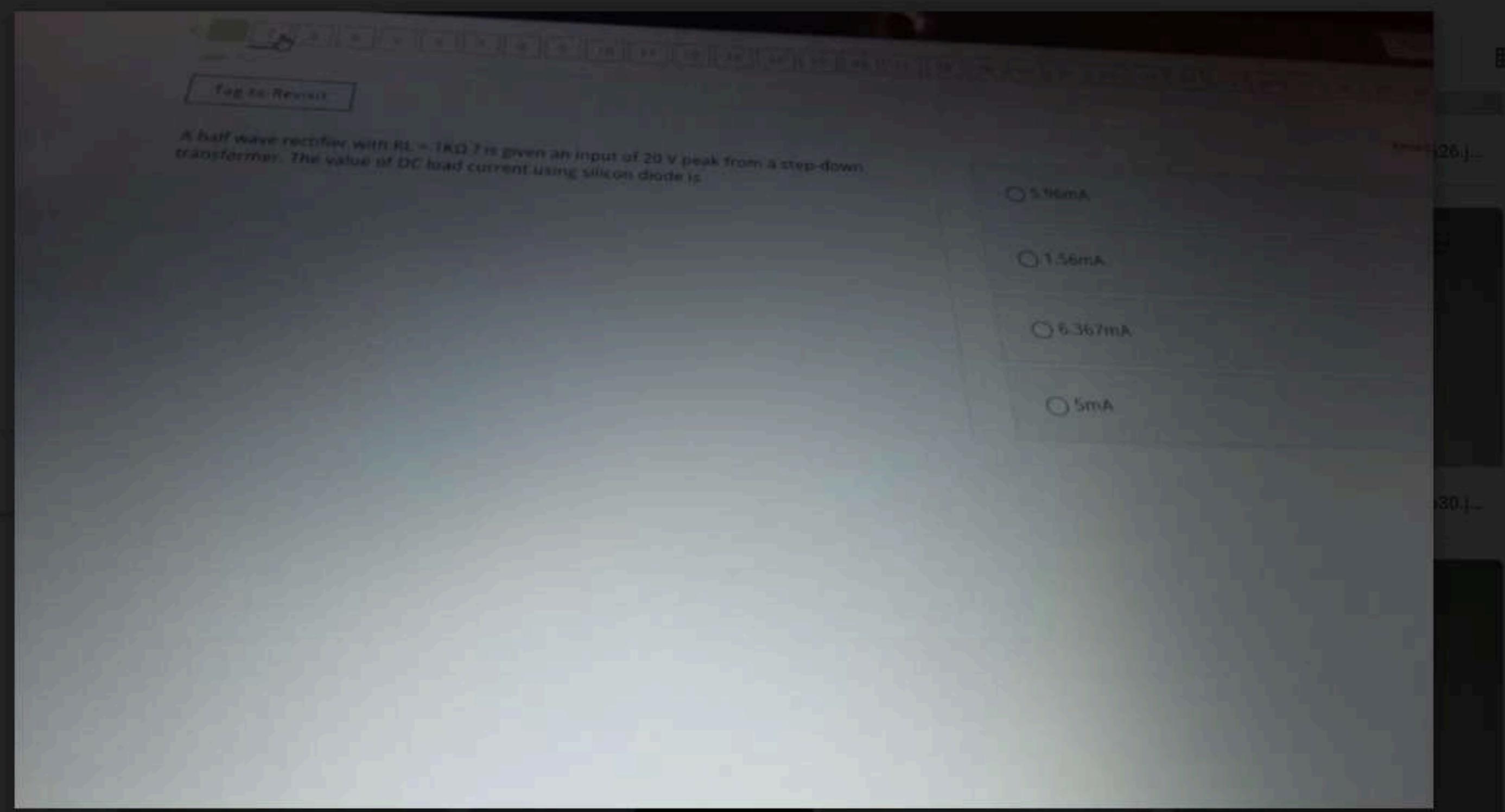

## Drive

Search in Drive

New

My Drive

Shared with me

Recent


Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

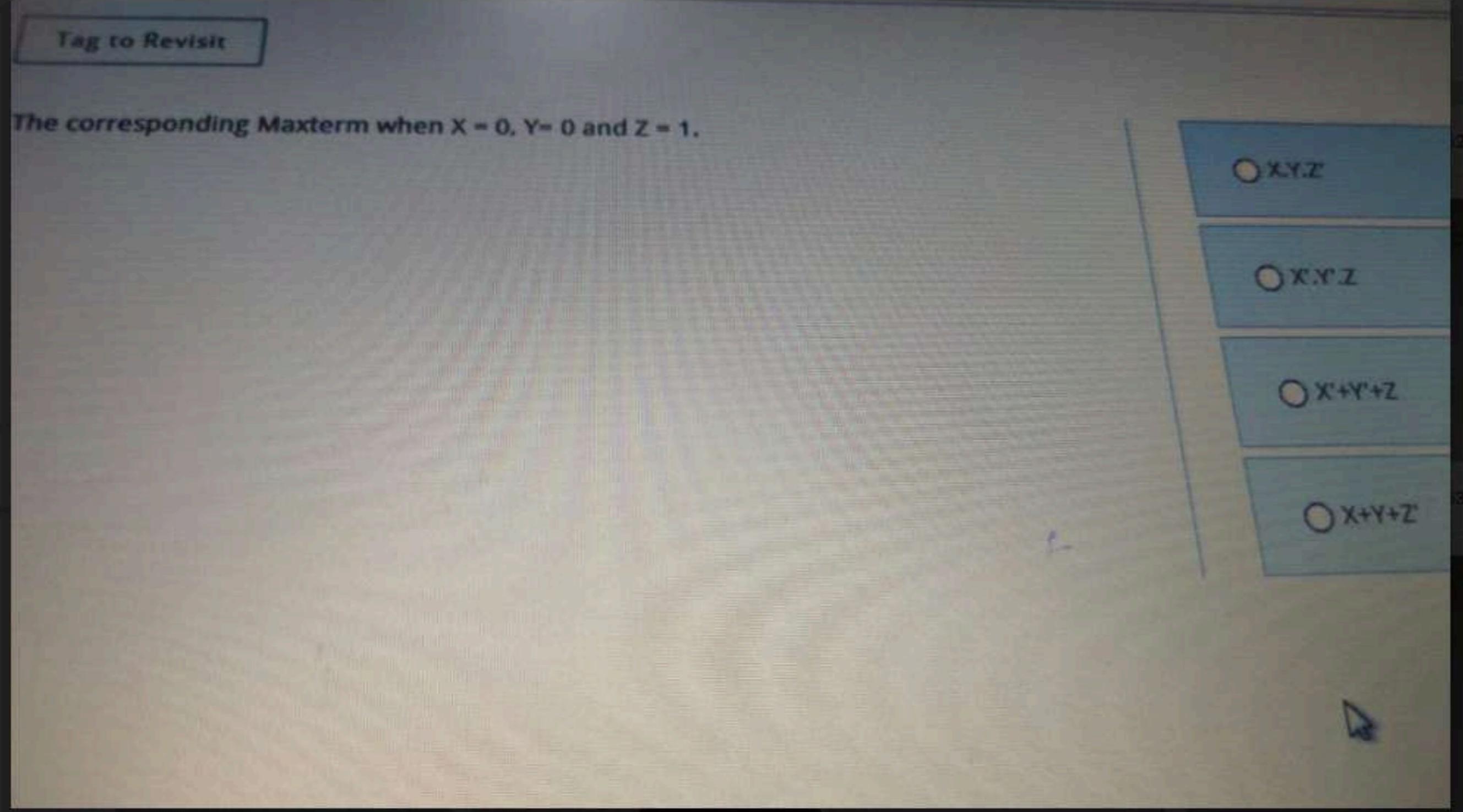

 Drive Search in Drive


Tag to Revisit



New



My Drive

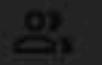

Shared with me



Recent



Starred



Trash



Storage

720.3 MB of 15 GB used

Buy storage

The peak value of a sine wave is 200 V. Its average value is

282.8 V

127.4 V

200V

141.4 V

 Drive

Search in Drive

New

My Drive

Shared with me

Recent


Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

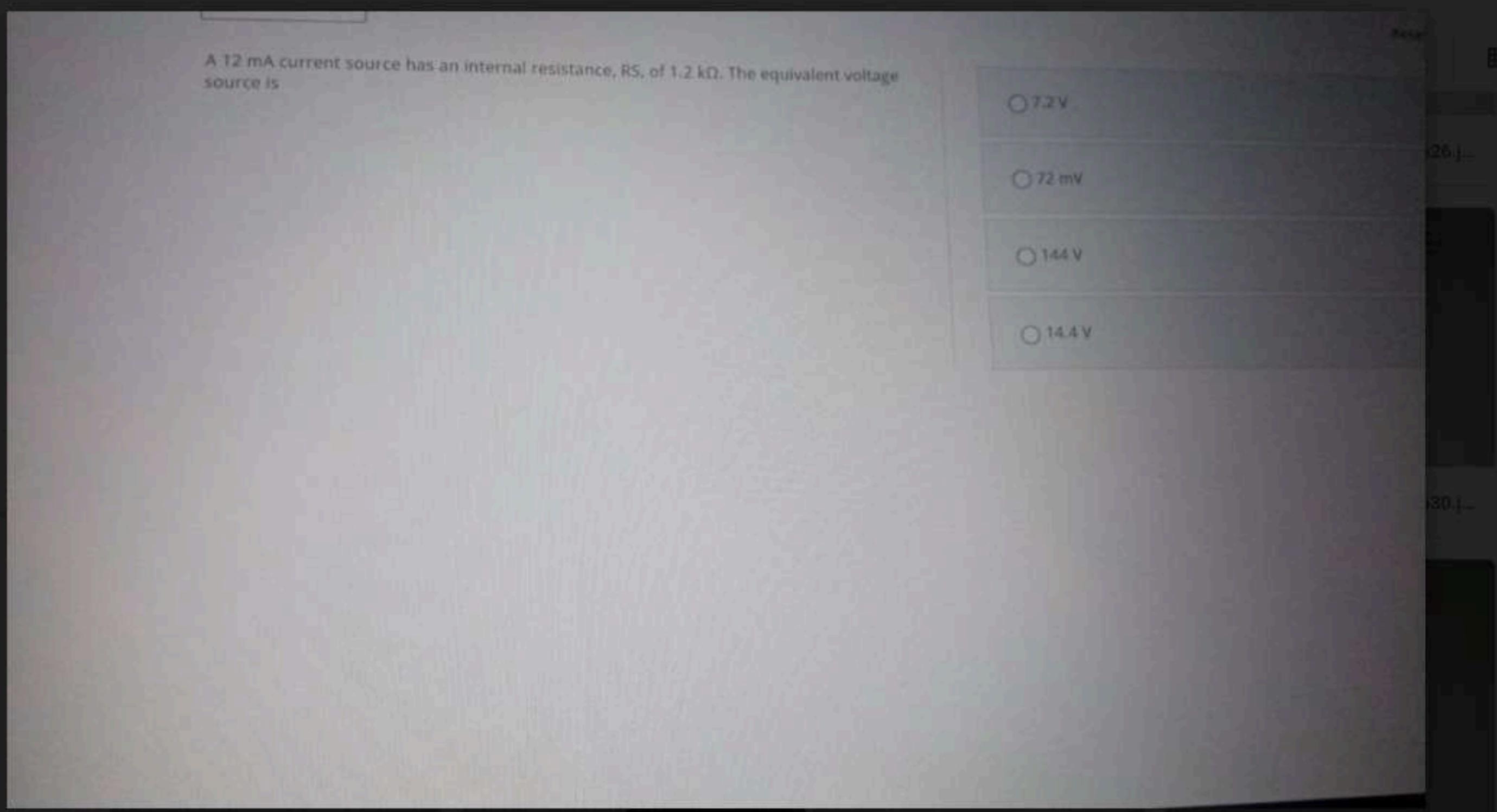

 Drive

Search in Drive

New

My Drive

Shared with me

Recent


Starred


Trash

Storage

720.3 MB of 15 GB used

Buy storage

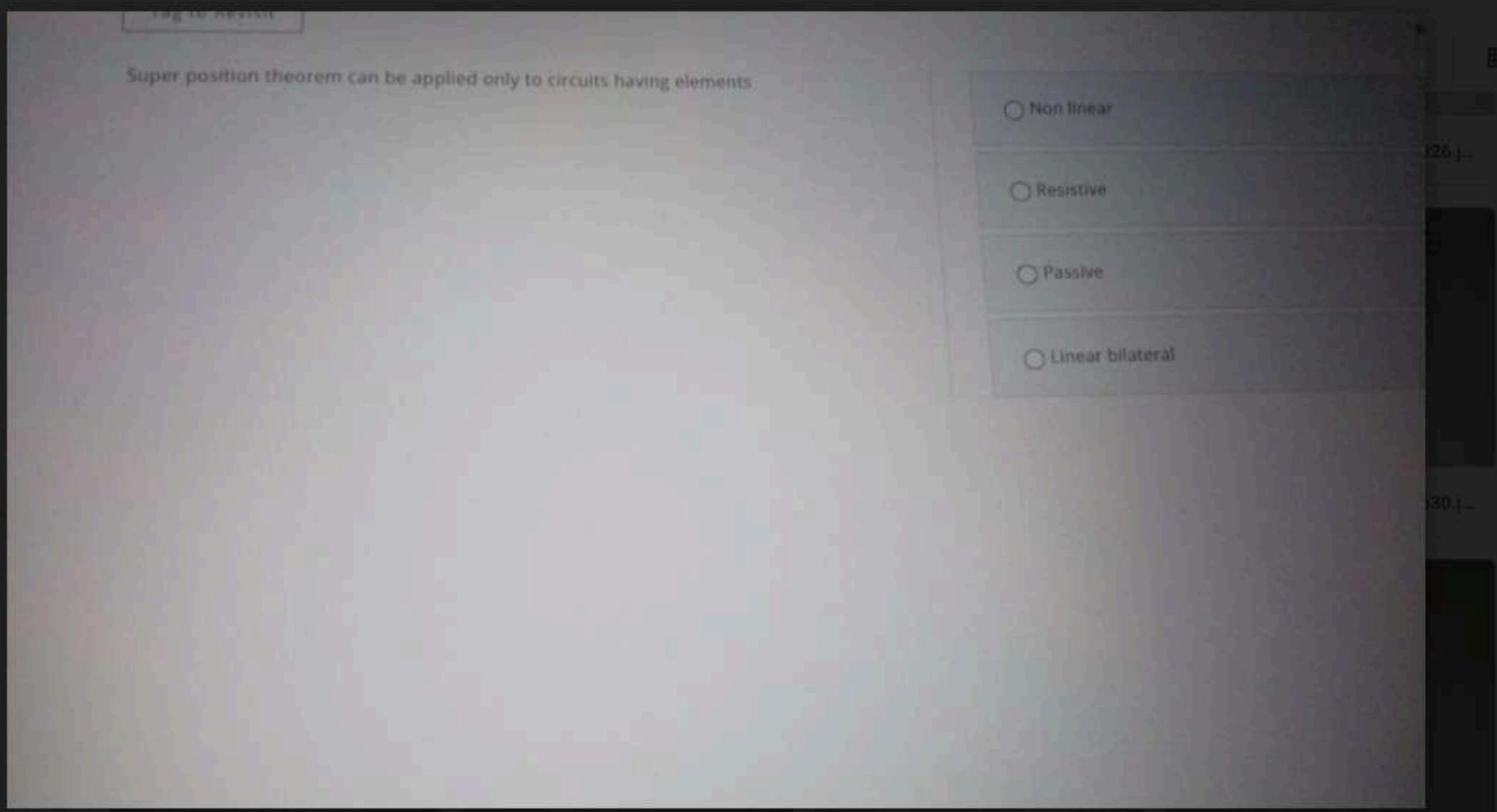

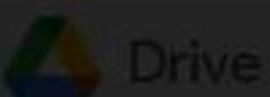

Drive




Search in Drive




New



My Drive

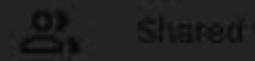

Shared with me

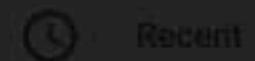


Recent



Starred




Trash

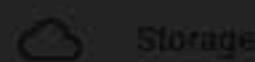


Storage

720.3 MB of 15 GB used

Buy storage

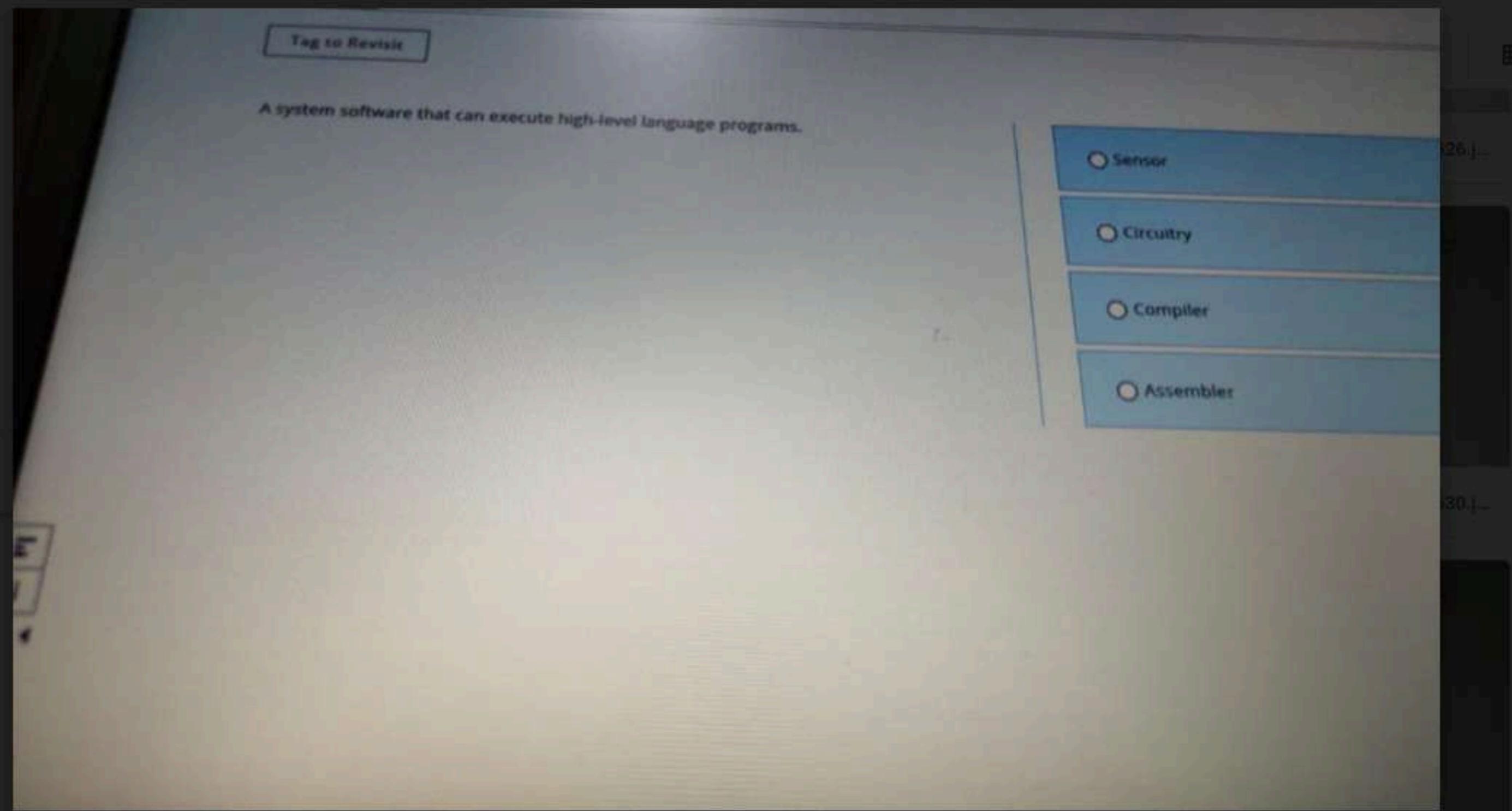

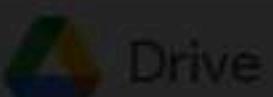

Drive



Search in Drive



New




My Drive



Shared with me



Recent

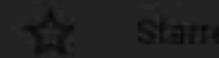

Starred



Trash



Storage

720.3 MB of 15 GB used

Buy storage

If the star connected circuit is transformed into delta connected circuit, which of the following statement is true?

Ra = R3/R1 R2 + R2R3+R1R3

Ra = R1R2+ R2R3+ R1R3 /R3

Ra = R3/R1+ R2

Ra = R1 + R2 + R3 /R1 + R2

 Drive

Search in Drive

Tag to Revisit

Reset

Gain-bandwidth product of a practical OP-AMP is...

 1 MHz zero infinite 10 MHz

New

My Drive

Shared with me

Recent


Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

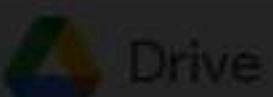

Drive




Search in Drive




New




My Drive

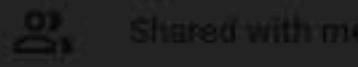

Shared with me

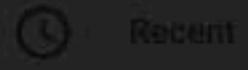


Recent

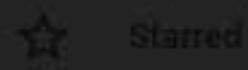

Starred



Trash

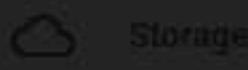

Storage

720.3 MB of 15 GB used

Buy storage

The transistor in CE configuration has a  $V_{BB} = 5V$ ,  $R_B = 15\text{ k}\Omega$  and a  $\beta_{DC} = 100$ , then  $I_C$  equal to:

28 mA

0.028 mA

2.8 mA

50 mA



Drive



Search in Drive



New



My Drive



Shared with me



Recent



Starred



Trash



Storage

720.3 MB of 15 GB used

Buy storage

Often a common-collector will be the last stage before the load; the main function(s) of this stage is to:

buffer the voltage amplifiers from the low resistance load and provide impedance matching for maximum power transfer

provide phase inversion

provide voltage gain

provide a high-frequency path to improve the frequency response

## Drive

Search in Drive

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

The corresponding Maxterm when X = 0, Y= 0 and Z = 1.

 XYZ XNYZ X+Y+Z X+Y+Z

App

Trade at Zerodha - T...

eConnect- Login BP...

Welcome to HDFC...

Home - Union Bank

Search in Drive

Shared with me &gt; Screenshot

Tag to Revisit

A voltage  $V = 300 \cos 100 t$  is applied to a HWR with  $RL = 5 \text{ k}\Omega$ . The rectifier may be represented by an ideal diode in series with a resistance of  $1\text{k}\Omega$ . The value of  $I_m$  is given as

 50 mA 500mA 56.56 mA 52 mA



Drive



Search in Drive



New



My Drive



Shared with me



Recent



Starred




Trash



Storage

720.3 MB of 15 GB used

Buy storage

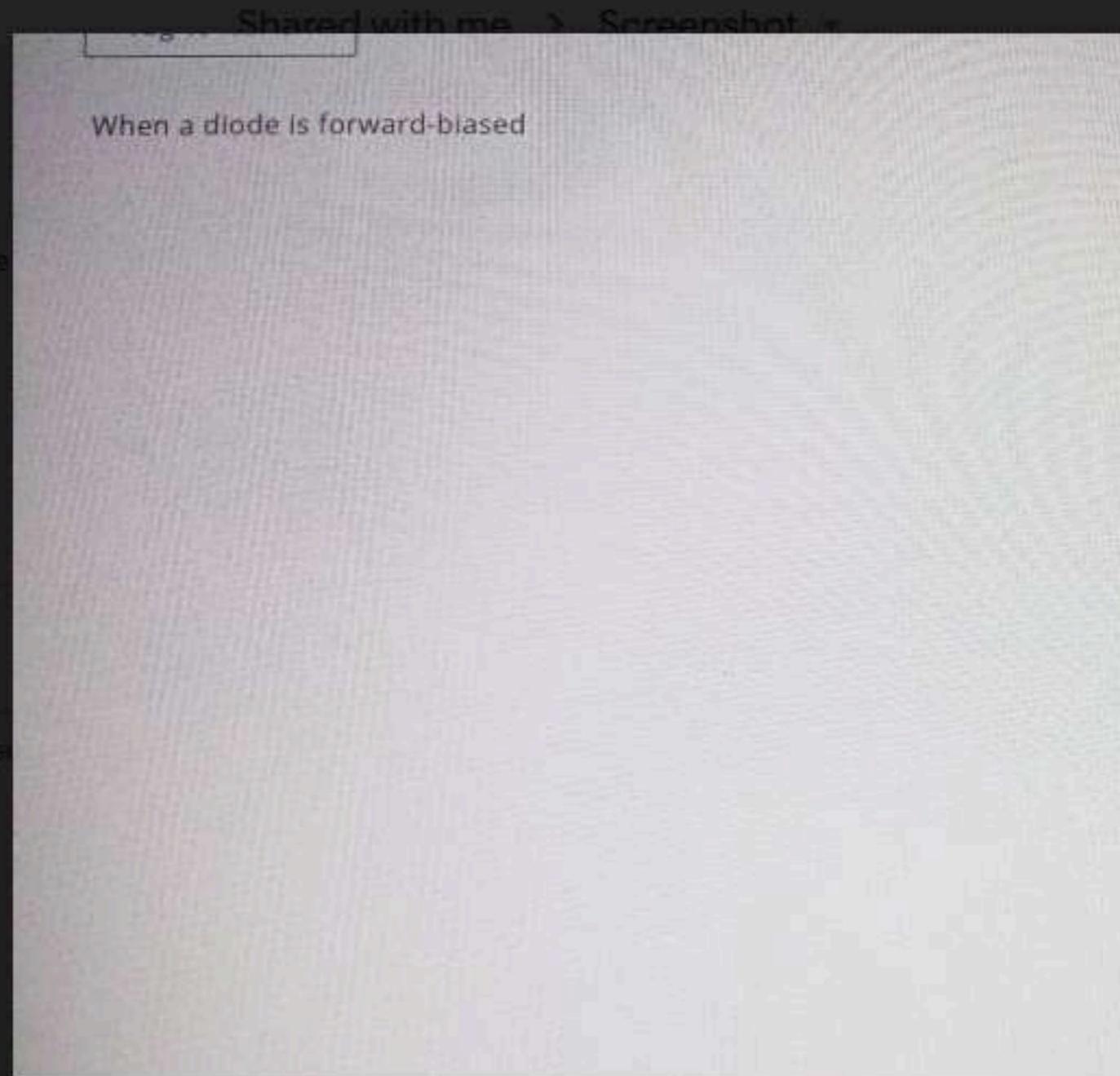 the current is produced by both holes and electrons the only current is hole current the only current is electron current the only current is produced by majority carriers

## Drive



Search in Drive

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

Tag to Revisit

For a Zener diode, its reverse current increases from 30 mA to 45 mA when the Zener voltage changes from 6.7 V to 6.77 V, then its zener resistance is

4.477 Ω

10 Ω

4.667 Ω

50

 Drive

Search in Drive

Tag to Revisit

Sum expression of half adder with inputs A and B is ....

  $A'B + AB'$   $AB$   $A+B$   $AB + A'B$ 

New

My Drive

Shared with me

Recent

Starred

Trash


Storage

720.3 MB of 15 GB used

Buy storage


 Drive

Search in Drive

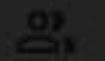 New My Drive Shared with me Recent Starred Trash Storage

720.3 MB of 15 GB used

Buy storage

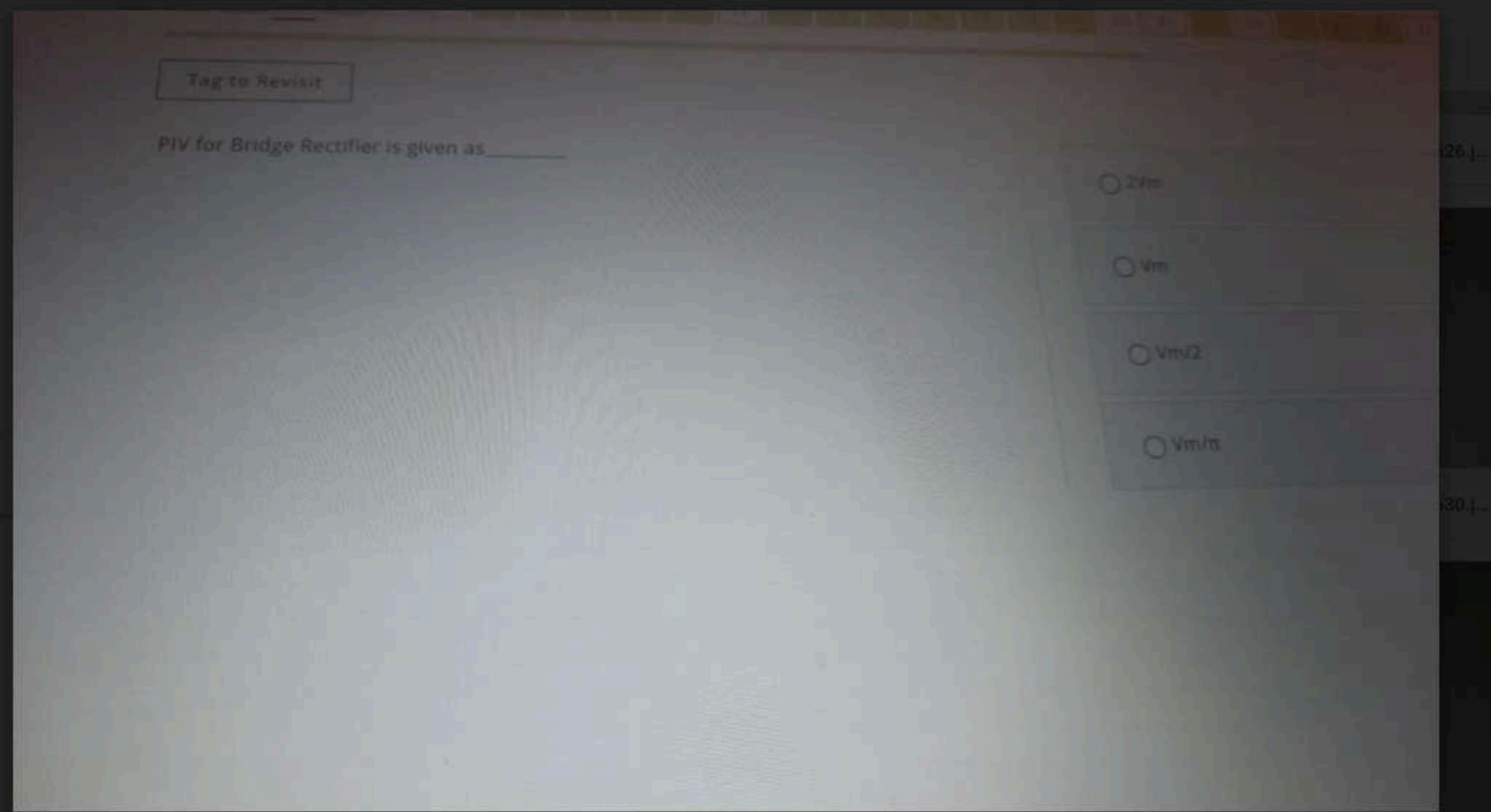



IMG-20210404-WA0729.jpg



Search in Drive

Open with




New



My Drive



Shared with me

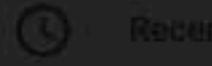

Recent



Starred



Trash




Storage

720.3 MB of 15 GB used

Buy storage

A power-supply transformer has a turns ratio of 5:1. What is the secondary voltage if the primary is connected to a 120 V rms source?

 24 Vrms 48 Vrms 60 Vrms 15 Vrms

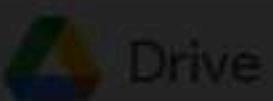

Drive

Search in Drive

Shared with me &gt; Screenshot



New



My Drive



Shared with me



Recent



Starred




Trash



Storage

720.3 MB of 15 GB used

Buy storage

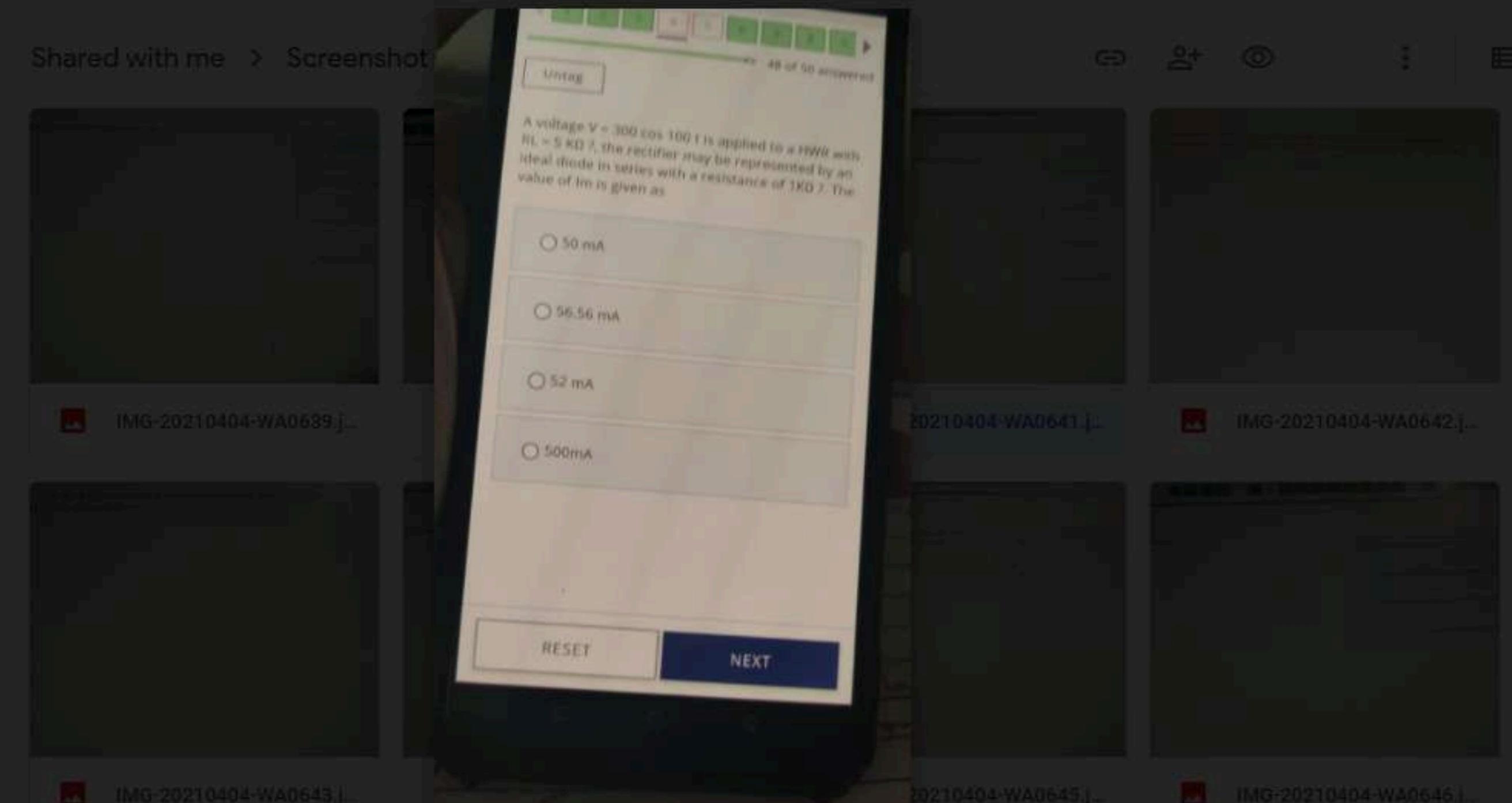



Drive



Search in Drive



New



My Drive



Shared with me



Recent



Starred



Trash



Storage

720.3 MB of 15 GB used

Buy storage

Shared with me > Screenshot

Tag to Revisit

When a diode is forward-biased

0 of 50 answered

Reset Next

the current is produced by both holes and electrons.

the only current is hole current.

the only current is electron current.

the only current is produced by majority carriers.

 Drive

Search in Drive

Tag to Revisit

Three different Q points are shown on a dc load line. The upper Q point represents the:

- cutoff point
- intermediate current gain
- minimum current gain
- maximum current gain

New

My Drive

Shared with me

Recent

Starred

Trash

Storage


720.3 MB of 15 GB used

Buy storage

## Drive




Search in Drive

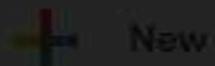

New



My Drive

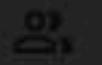

Shared with me



Recent



Starred



Trash



Storage

720.3 MB of 15 GB used

Buy storage

By Superposition Principle if only 10V source is acting  $I_{AB1} = 5 \text{ A}$  from A to B and if only 20 V source is acting  $I_{AB2}$  is 3.8 A from B to A. What will be the current when both the sources are acting simultaneously?

1.2 A from A to B

1.2 A from B to A

5.2 A from A to B

11.2 A from A to B

## Drive

Search in Drive

New

My Drive

Shared with me

Recent


Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

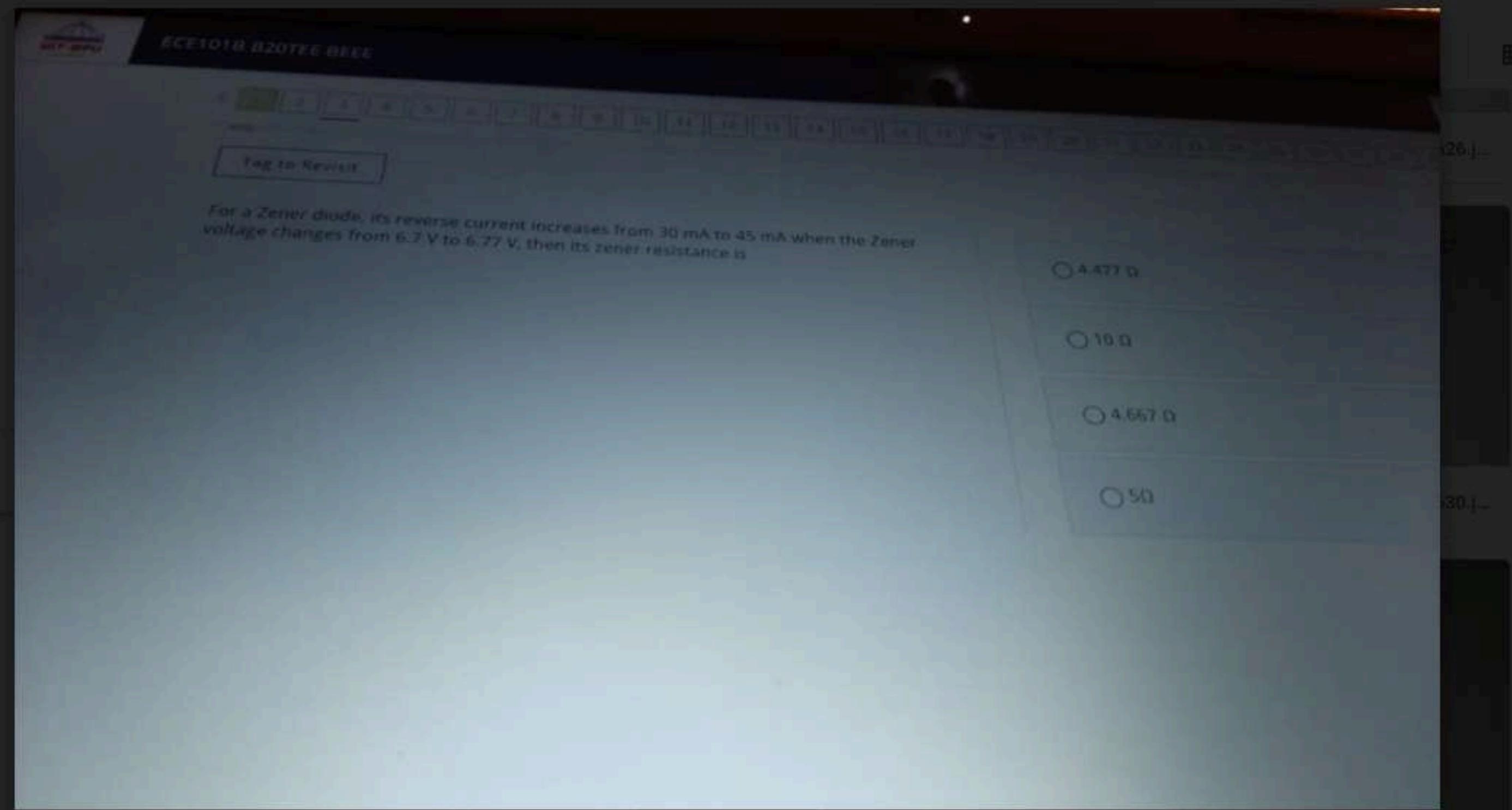

## Drive

Search in Drive

New

My Drive

Shared with me

Recent


Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

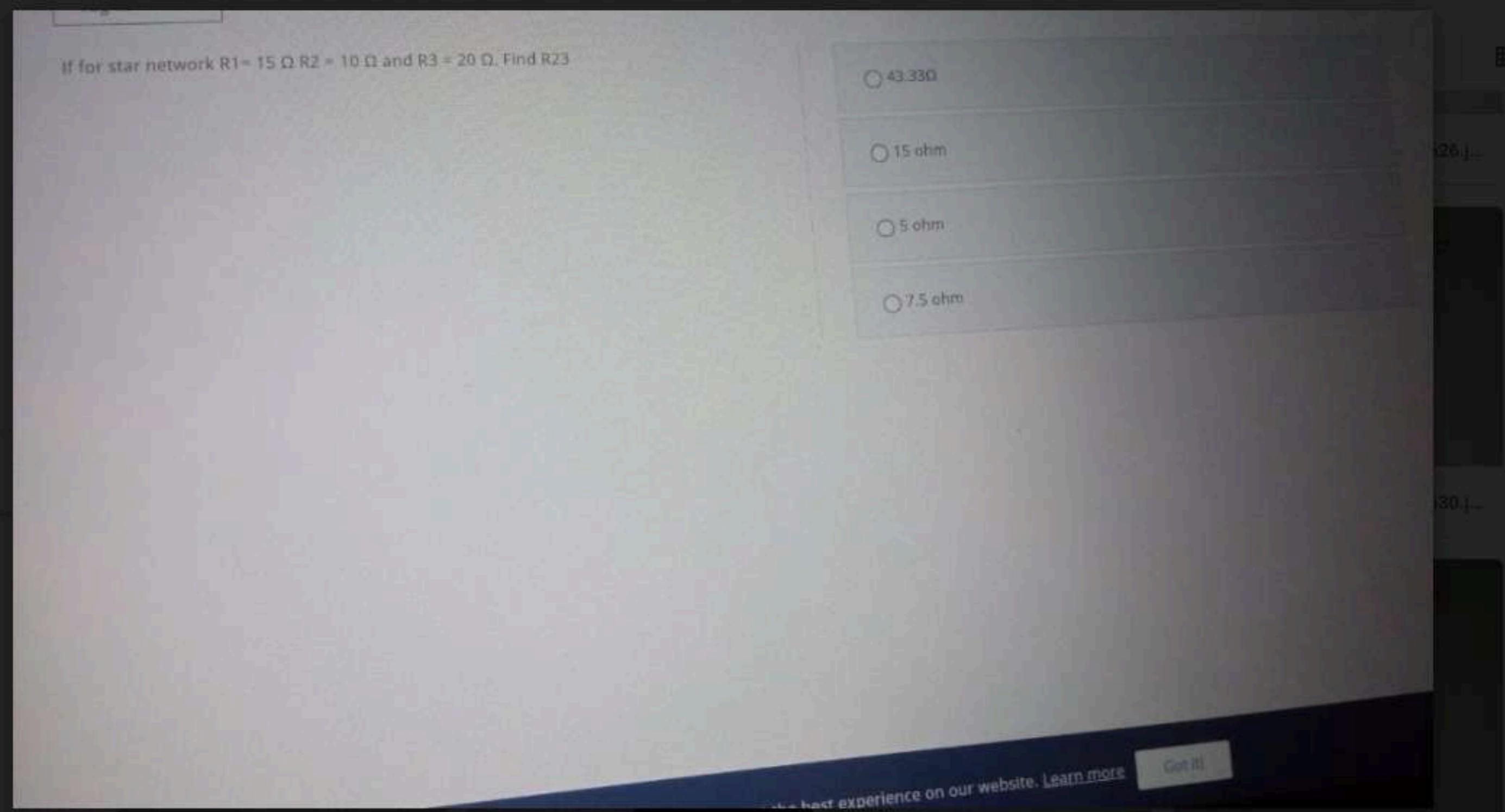

## Drive



Search in Drive

New

My Drive

Shared with me

Recent


Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

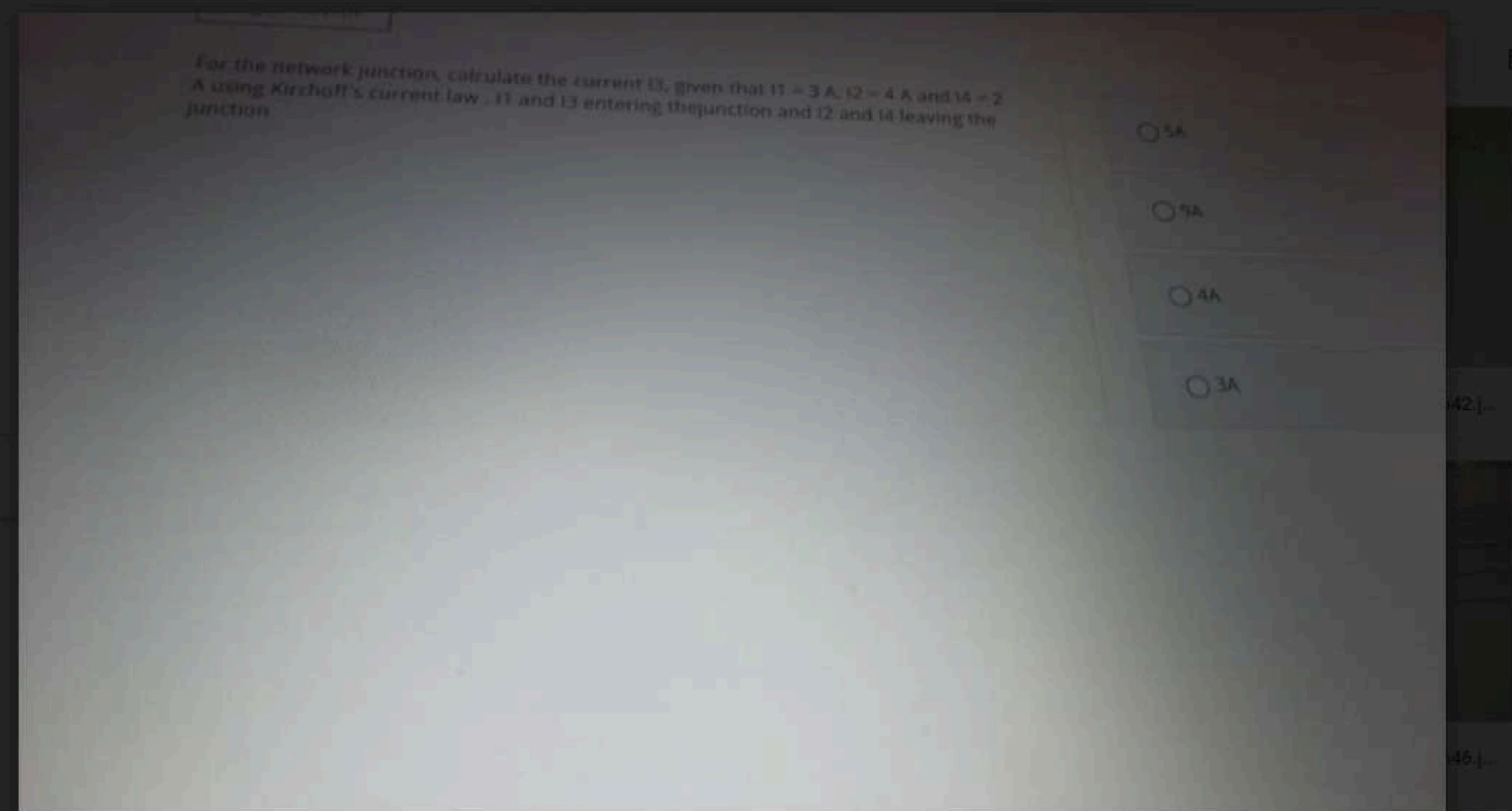

## Drive



Search in Drive

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

A bridge rectifier uses a capacitor of  $100 \mu\text{F}$  as a filter with a load resistance of  $1 \text{ k}\Omega$ . Its ripple factor for frequency of  $50 \text{ Hz}$  is

 0.288 0.144 0.0144 0.0288


## Drive

Search in Drive

If for star network  $R_1 = 5 \Omega$ ,  $R_2 = 10 \Omega$  and  $R_3 = 20 \Omega$ . Find  $R_{12}$

 7.5 ohm 5 ohm 17.5 ohm 15 ohm

Reset

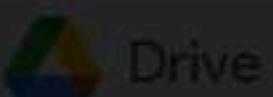

Drive



Search in Drive



New



My Drive



Shared with me



Recent



Starred



Trash



Storage

720.3 MB of 15 GB used

Buy storage

Shaver with me > Screenshot

Tag to Revisit

A half wave rectifier with  $RL = 1k\Omega$  is given an input of 10 V peak from a step-down transformer. DC load voltage using ideal diode is

3.18V


2.13V

9.18V

5.18V

## Drive

Search in Drive

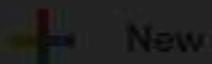


New



My Drive



Shared with me

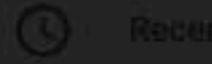

Recent



Starred



Trash



Storage

720.3 MB of 15 GB used

Buy storage

If  $R = 32 \Omega$ ,  $X_L = 34 \Omega$  are connected in series then impedance  $Z =$

45.69Ω

40

20

46Ω

## Drive

Search in Drive

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

47 of 50 answer

Tag to Revisit      Reset      Next >

A certain inverting amplifier has input signal voltage is 10 mVrms, R<sub>1</sub> of 100 kΩ and R<sub>f</sub> of 100 kΩ, find the output voltage.

-10mVrms, out of phase

-10Vrms, out of phase

-10mVrms, in phase

-1Vrms, out of phase

## Drive



Search in Drive

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

Tag to Revisit

A half wave rectifier with  $R_L = 1k\Omega$  is given an input of 10 V peak from a step-down transformer. DC load voltage using ideal diode is

 9.18 V 2.13 V 3.18 V 5.18 V

## Drive

Search in Drive

New

My Drive

Shared with me

Recent


Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

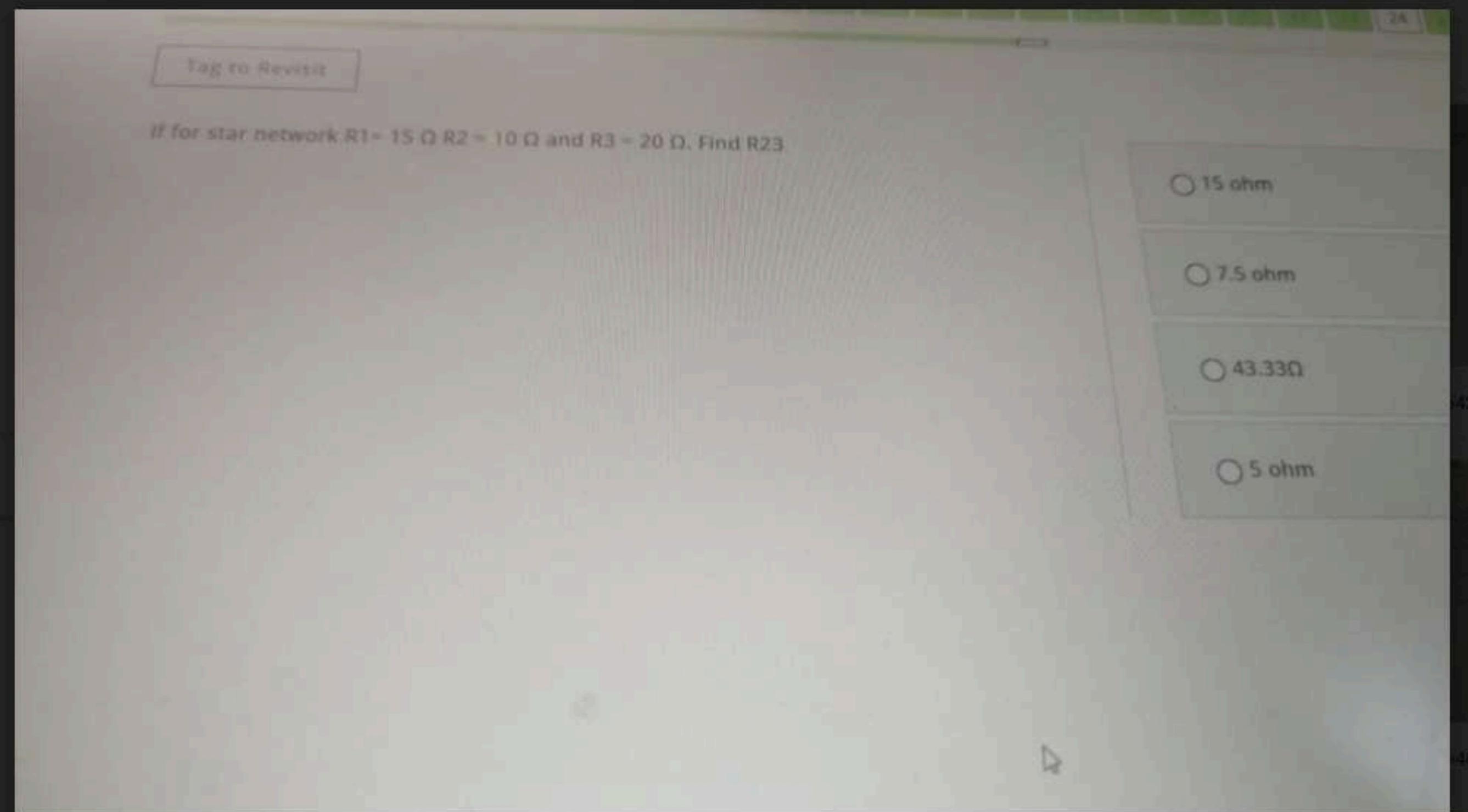

## Drive

Search in Drive



A certain inverting amplifier has input signal voltage is 10 mVrms, R<sub>1</sub> of 100 kΩ and R<sub>f</sub> of 100 kΩ, find the output voltage.

-10Vrms, out of phase

-10mVrms, in phase

-10mVrms, out of phase

-1Vrms, out of phase

## Drive

Search in Drive

New

My Drive

Shared with me

Recent


Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

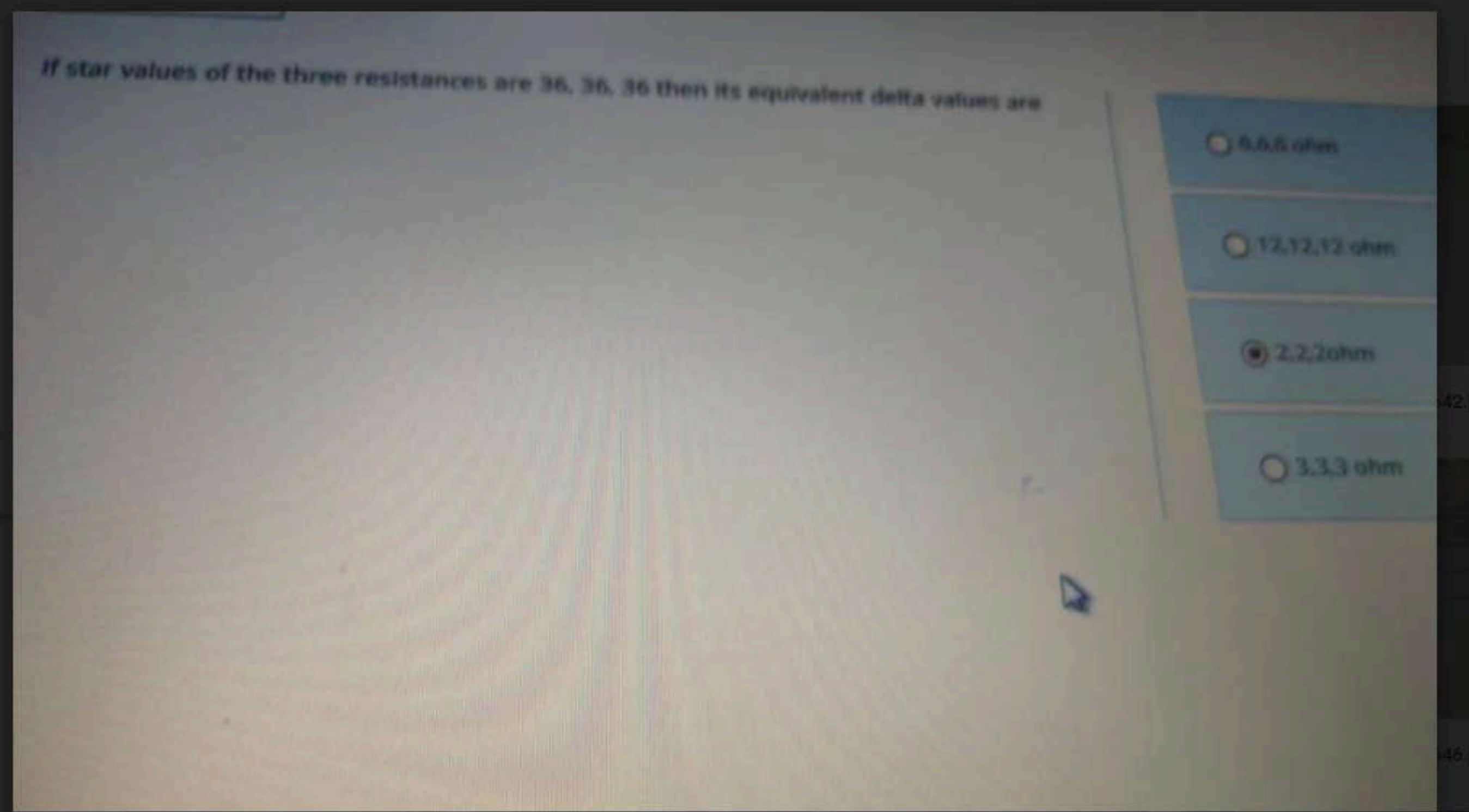

 Drive

Search in Drive

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

An ideal transformer will have maximum efficiency at a load such that \_\_\_\_\_

- copper loss < iron loss
- cannot be determined
- copper loss = iron loss
- copper loss > iron loss

## Drive




Search in Drive




New




My Drive

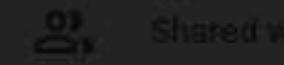


Shared with me

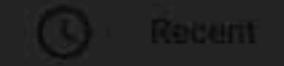

Recent

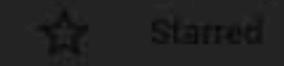

Starred

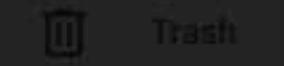


Trash



Storage

720.3 MB of 15 GB used

Buy storage

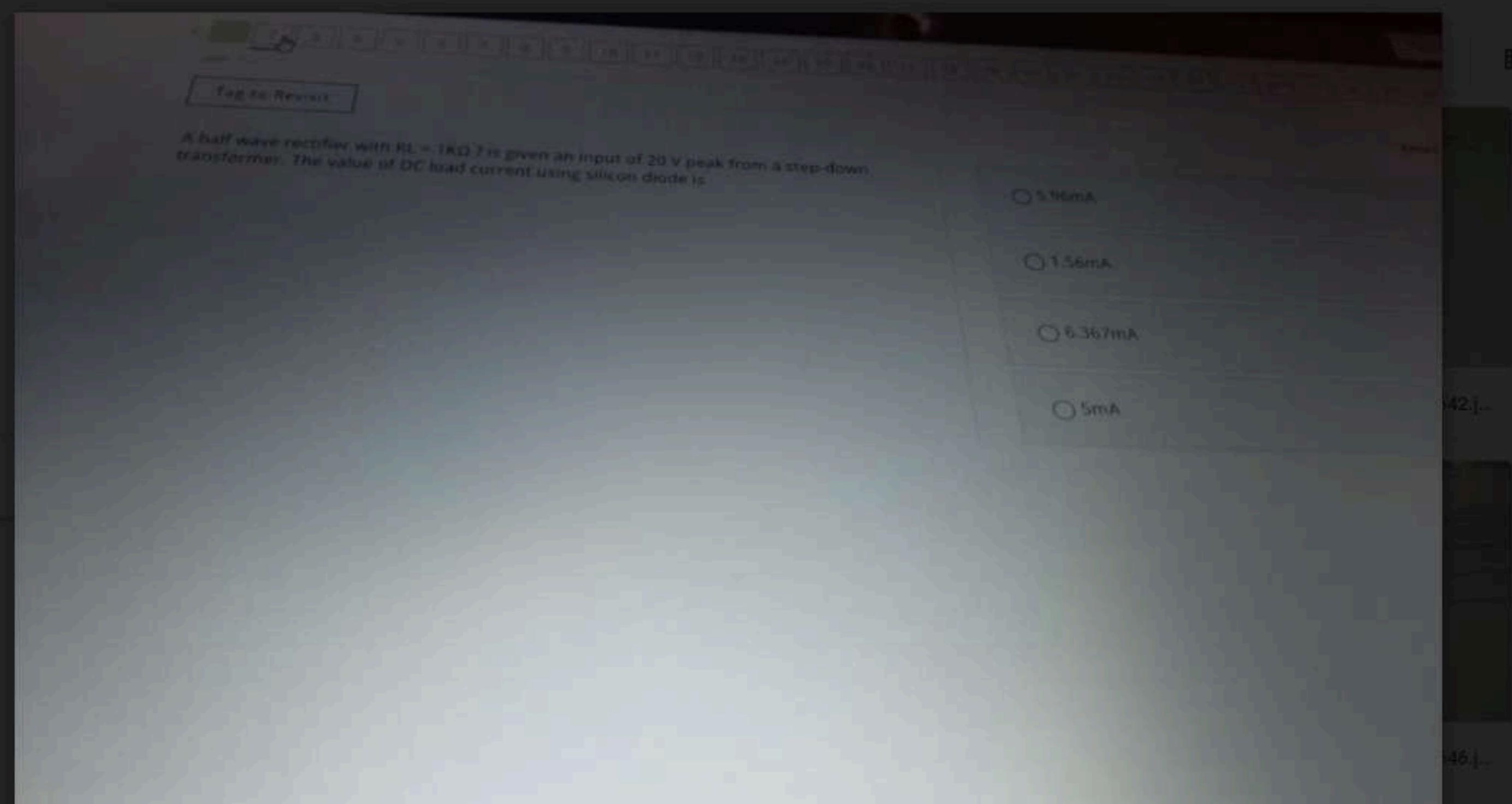

 Drive

Search in Drive

New

My Drive

Shared with me

Recent


Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

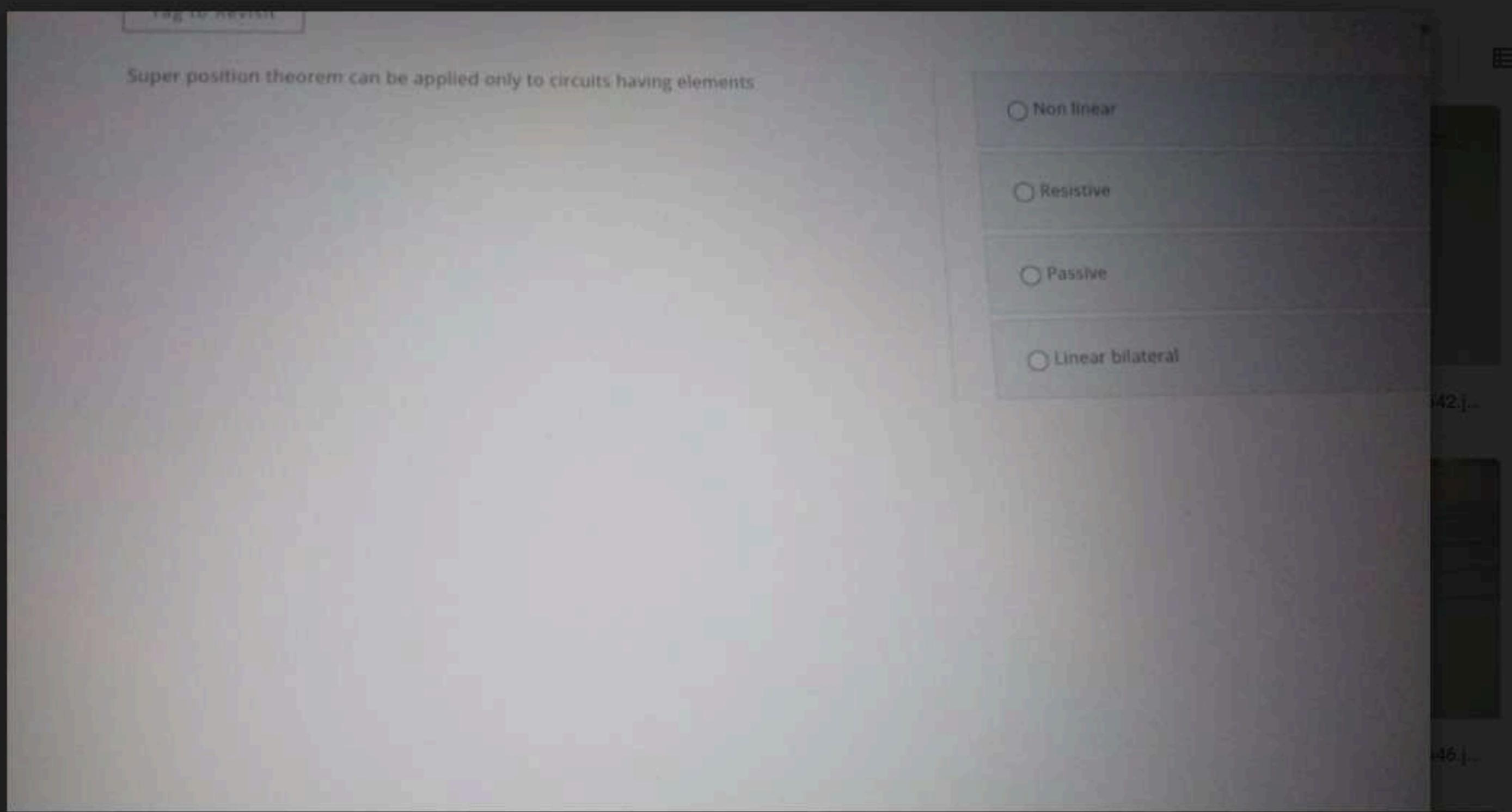

## Drive



Search in Drive

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

A 12 mA current source has an internal resistance,  $R_S$ , of 1.2 k $\Omega$ . The equivalent voltage source is

7.2V

72 mV

144 V

14.4 V

## Drive

Search in Drive

New

My Drive

Shared with me

Recent


Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

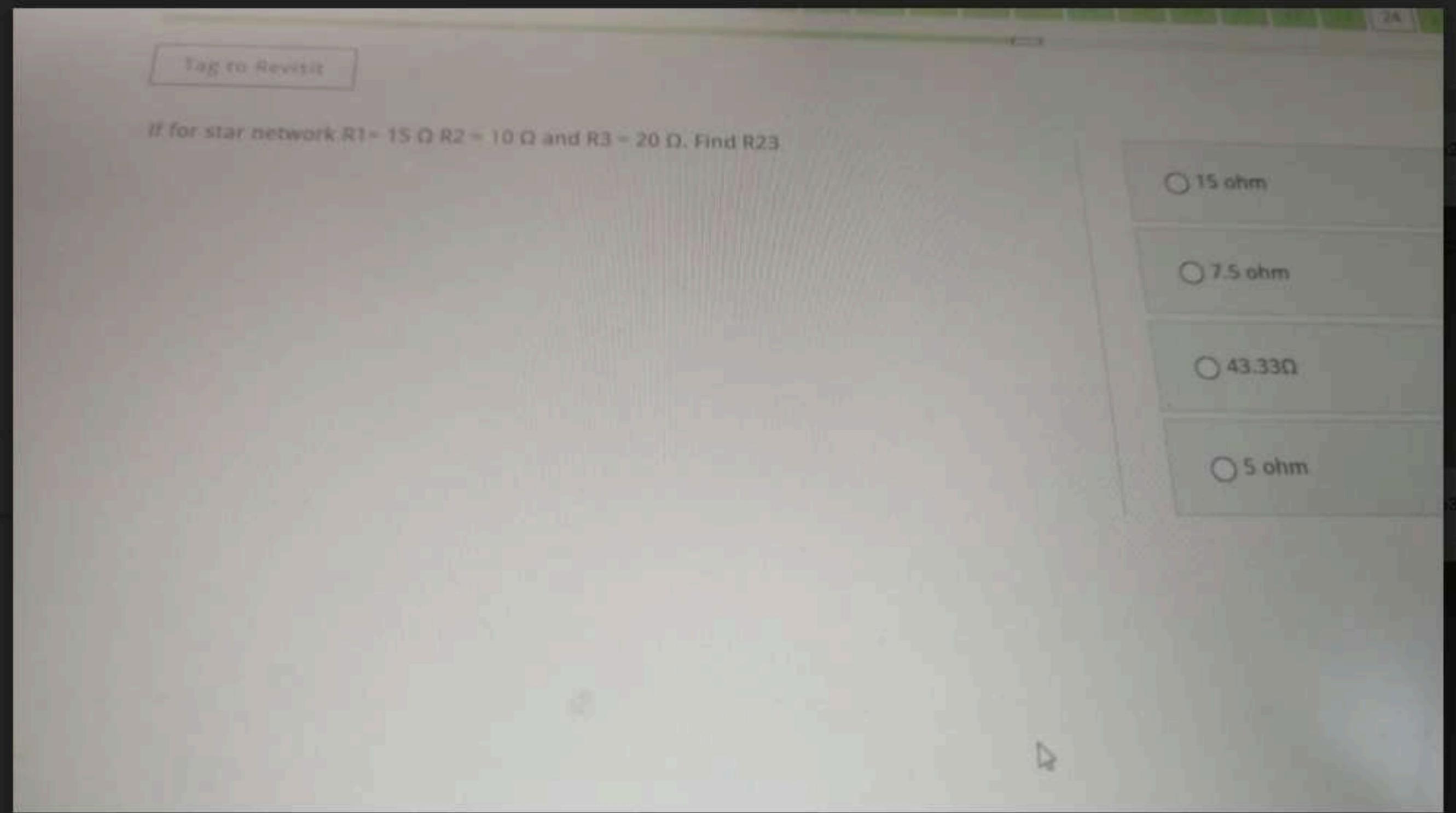

## Drive



Search in Drive

New

My Drive

Shared with me

Recent


Starred


Trash

Storage

720.3 MB of 15 GB used

Buy storage

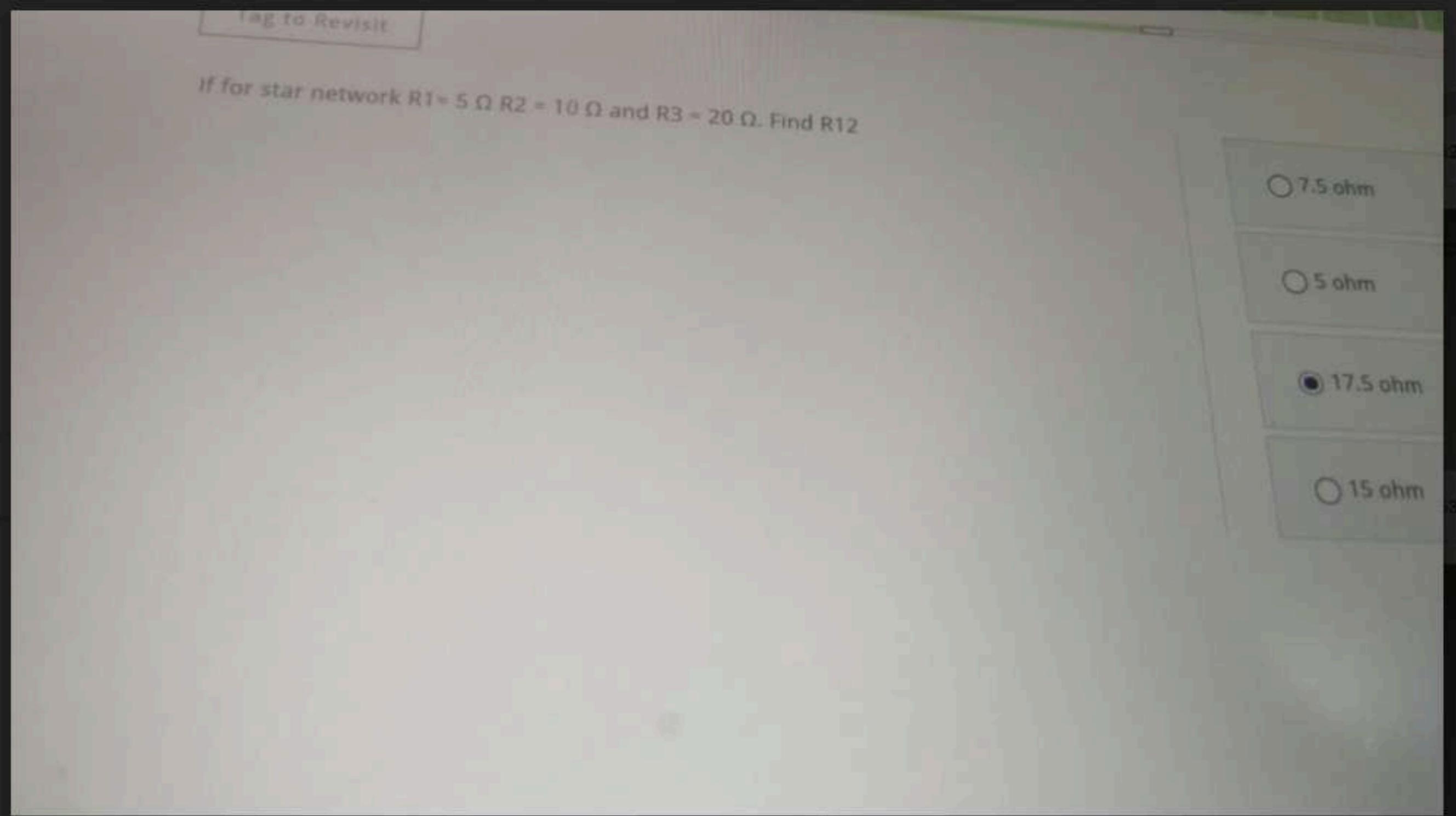

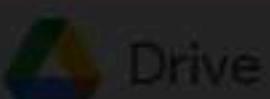

Drive



Search in Drive



New



My Drive



Shared with me



Recent



Starred



Trash



Storage

720.3 MB of 15 GB used

Buy storage

A bridge rectifier uses a capacitor of  $100 \mu\text{F}$  as a filter with a load resistance of  $1 \text{ k}\Omega$ . Its ripple factor for frequency of  $50 \text{ Hz}$  is

0.288  
 0.144  
 0.0144  
 0.0288



## Drive

Search in Drive

If for star network  $R_1 = 5 \Omega$ ,  $R_2 = 10 \Omega$  and  $R_3 = 20 \Omega$ . Find  $R_{12}$

 7.5 ohm 5 ohm 17.5 ohm 15 ohm

Reset

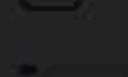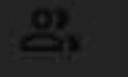

720.3 MB

Buy


Apps

Kite at Zerodha - T...

eConnect- Login BP...

Welcome to HDFC...

Home - Union Bank

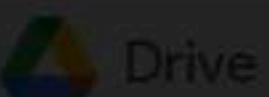

Drive


Search in Drive




New




My Drive

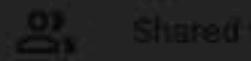

Shared with me

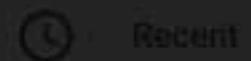


Recent

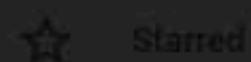

Starred



Trash

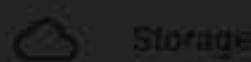


Storage

720.3 MB of 15 GB used

Buy storage


Shared with me &gt; Screenshot

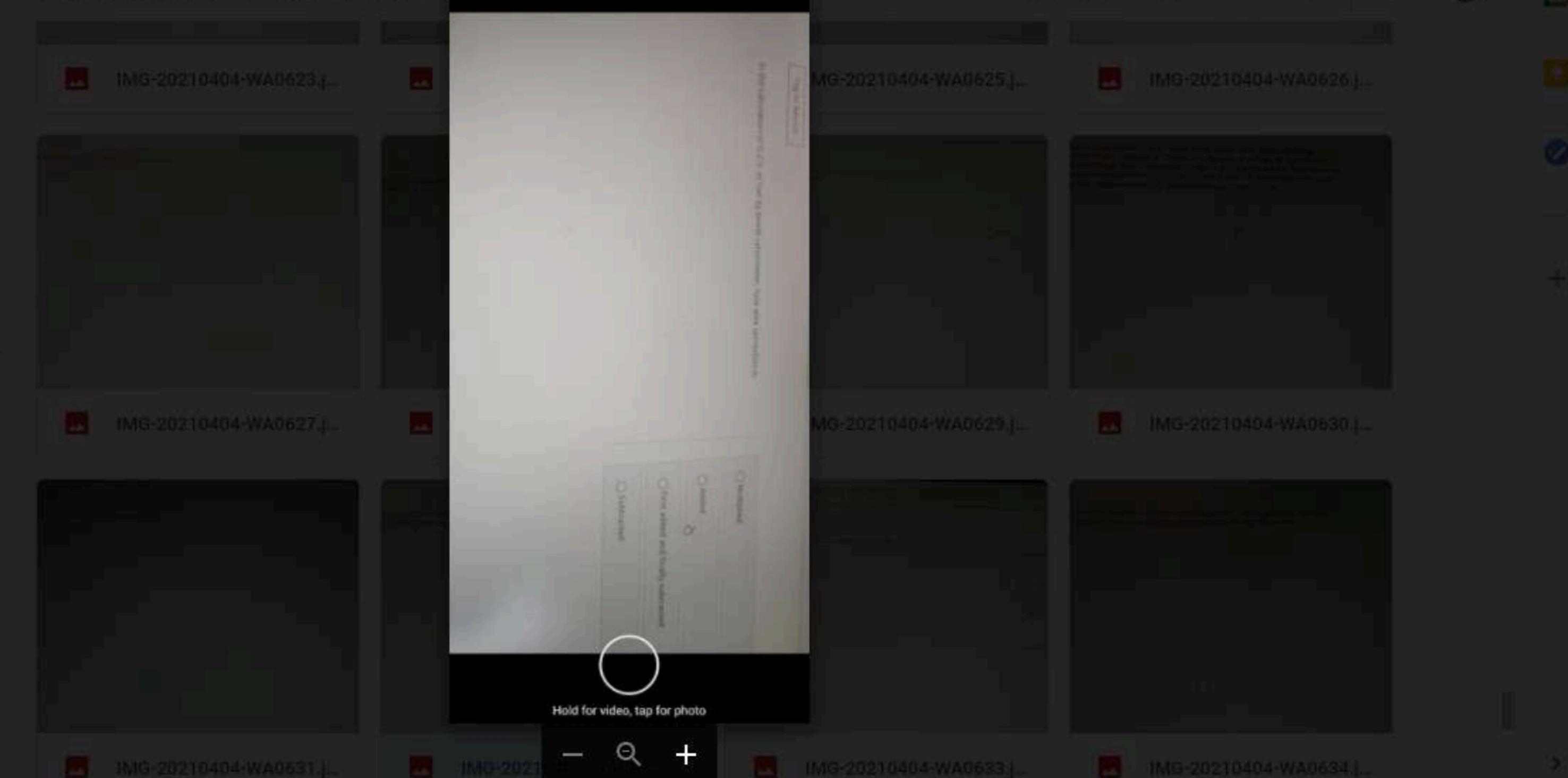

## Drive




Search in Drive

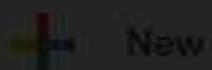

New



My Drive

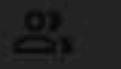

Shared with me



Recent



Starred




Trash



Storage

720.3 MB of 15 GB used

Buy storage

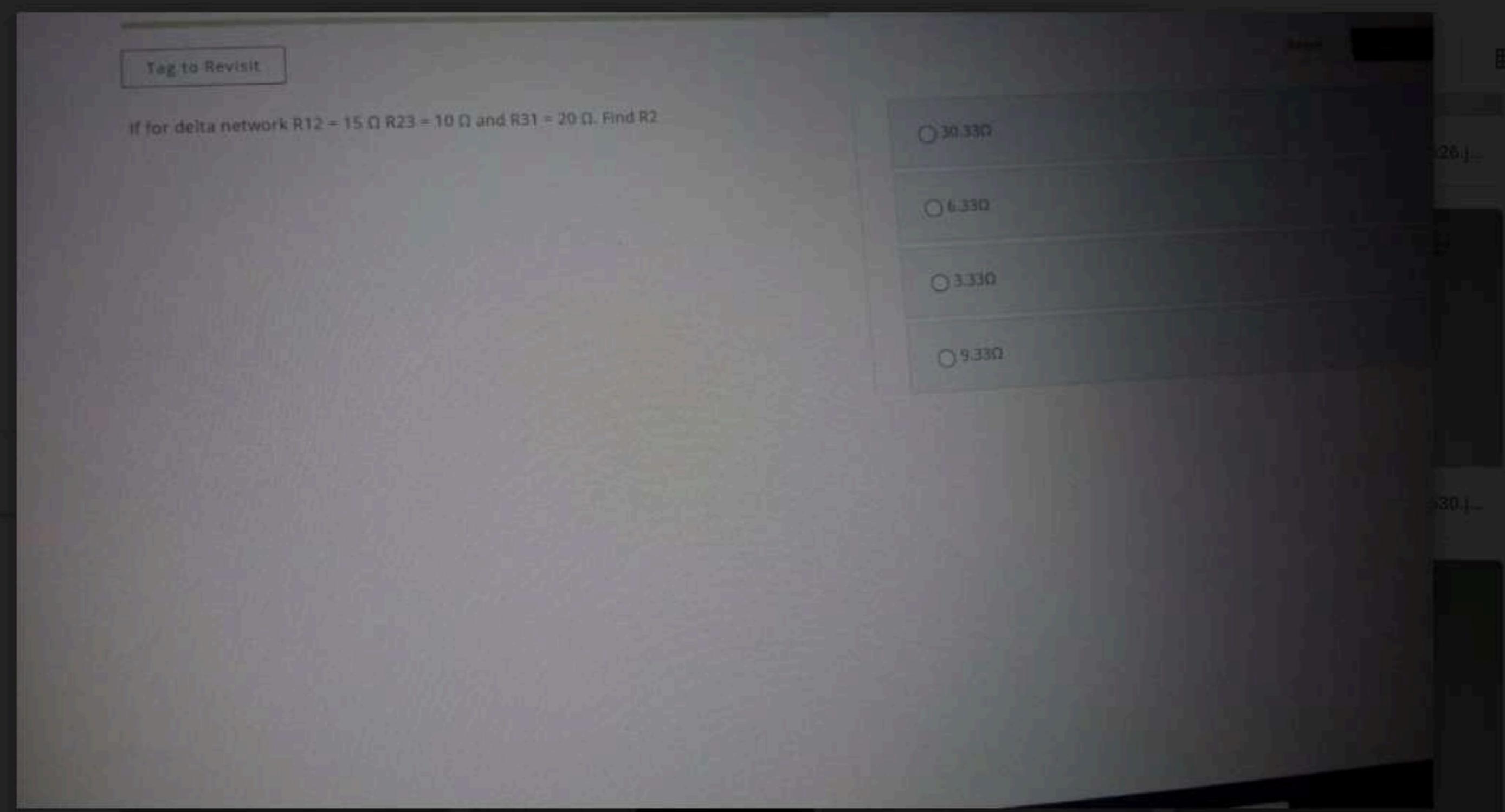

 Drive

Search in Drive

New

My Drive

Shared with me

Recent


Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

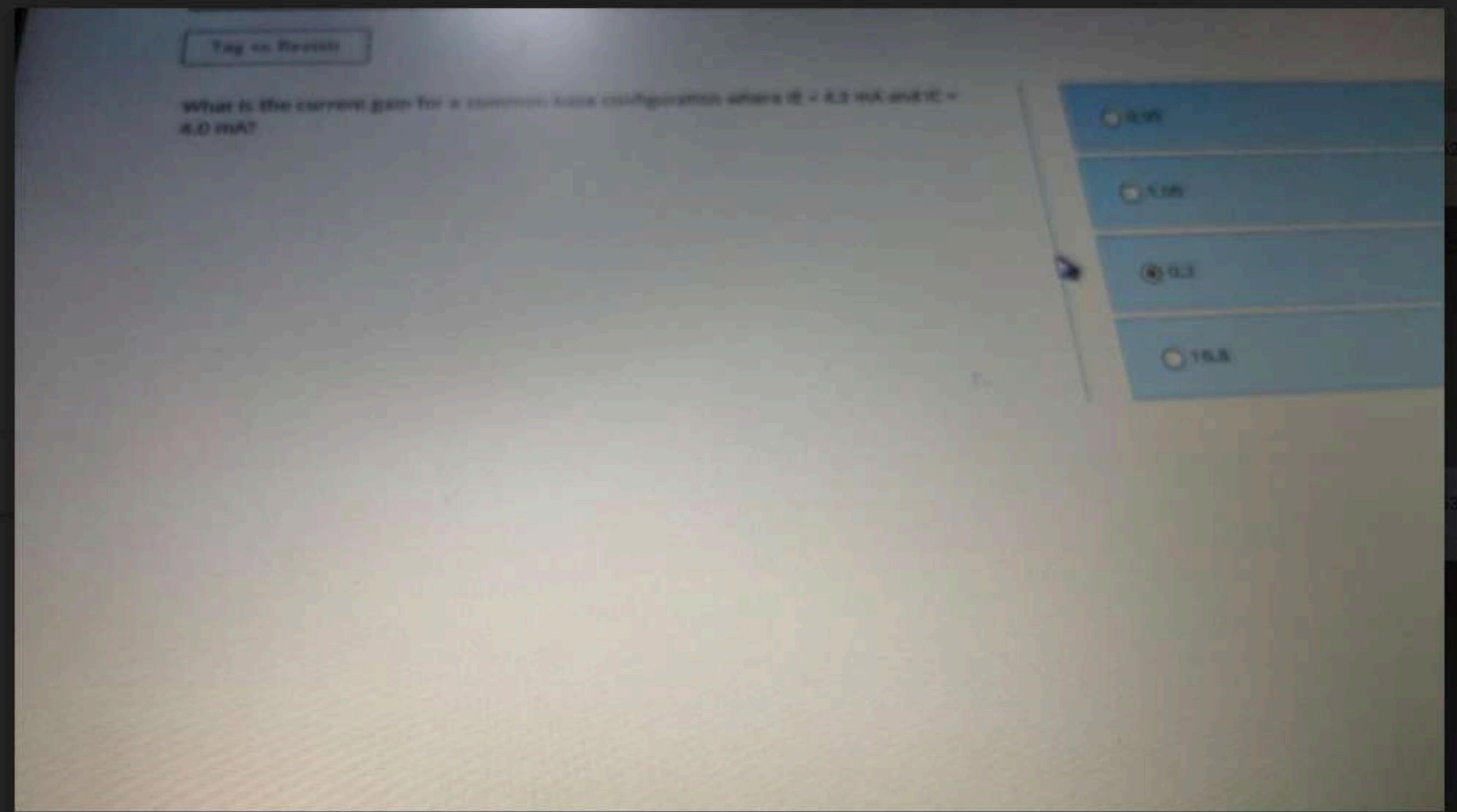

## Drive

Search in Drive

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

## Tag to Revisit

The corresponding Maxterm when X = 0, Y= 0 and Z = 1.

 $X'YZ$  $X'X'Z$  $X'+Y'+Z$  $X+Y+Z$



Drive




Search in Drive



New



My Drive

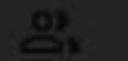

Shared with me



Recent



Starred



Trash



Storage

720.3 MB of 15 GB used

Buy storage

Shared with me > Screenshot

Tag to Revisit

A voltage  $V = 300 \cos 100 t$  is applied to a HWR with  $RL = 5 \text{ k}\Omega$ . The rectifier may be represented by an ideal diode in series with a resistance of  $1\text{k}\Omega$ . The value of  $I_m$  is given as

50 mA

500mA

56.56 mA

52 mA

App

Trade at Zerodha - T...

eConnect- Login BP...

Welcome to HDFC...

Home - Union Bank



My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

The peak value of a sine wave is 200 V. Its average value is

282.8 V

127.4 V

200V

141.4 V



Drive



Search in Drive



New



My Drive



Shared with me



Recent



Starred




Trash



Storage

720.3 MB of 15 GB used

Buy storage

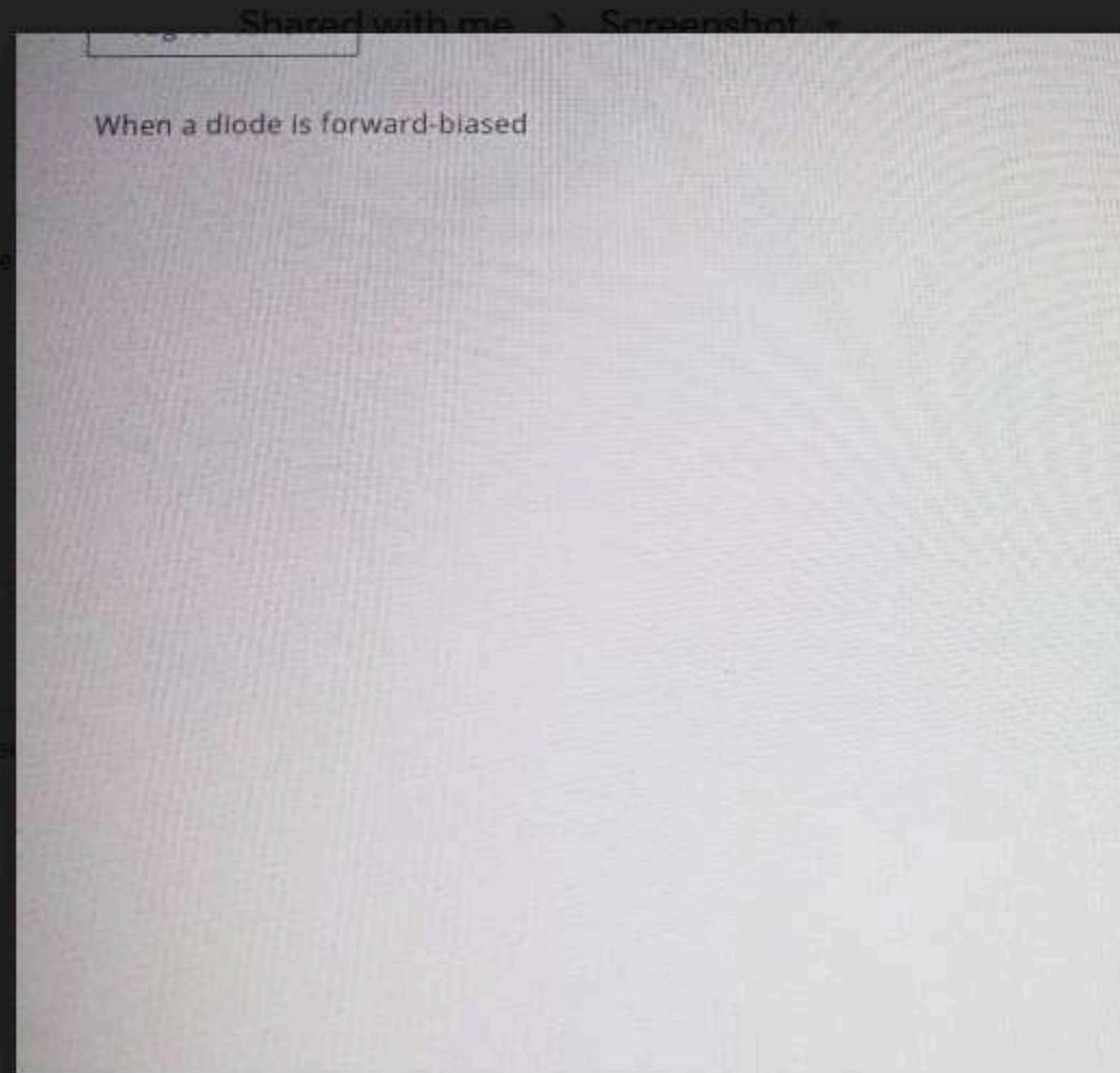 the current is produced by both holes and electrons the only current is hole current the only current is electron current the only current is produced by majority carriers

 Drive

Search in Drive

Tag to Revisit

When an AC source is connected across the resistive circuits,

 I and V are in phase V lags I current by 90 degrees V leads I by 180 degrees V leads I by 90 degrees

New

My Drive

Shared with me

Recent

Starred

Trash

Storage

720.3 MB of 15 GB used

Buy storage

 Drive

Search in Drive

Tag to Revisit

If the star connected circuit is transformed into delta connected circuit, which of the following statement is true?

 Ra =  $R_3/R_1 R_2 + R_2 R_3 + R_1 R_3$  Ra =  $R_1 R_2 + R_2 R_3 + R_1 R_3 / R_3$  Ra =  $R_3/R_1 + R_2$  Ra =  $R_1 + R_2 + R_3 / R_1 + R_2$ 

New

My Drive

Shared with me

Recent

Starred

Trash


Storage

720.3 MB of 15 GB used

Buy storage

 Drive

Search in Drive

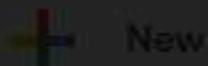


New



My Drive



Shared with me

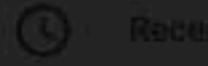

Recent



Starred



Trash



Storage

720.3 MB of 15 GB used

Buy storage


An alternating voltage has an equation  $v = 141.4 \sin 377t$ , what is the value of RMS voltage?

1.414V

141.4V

100

110V

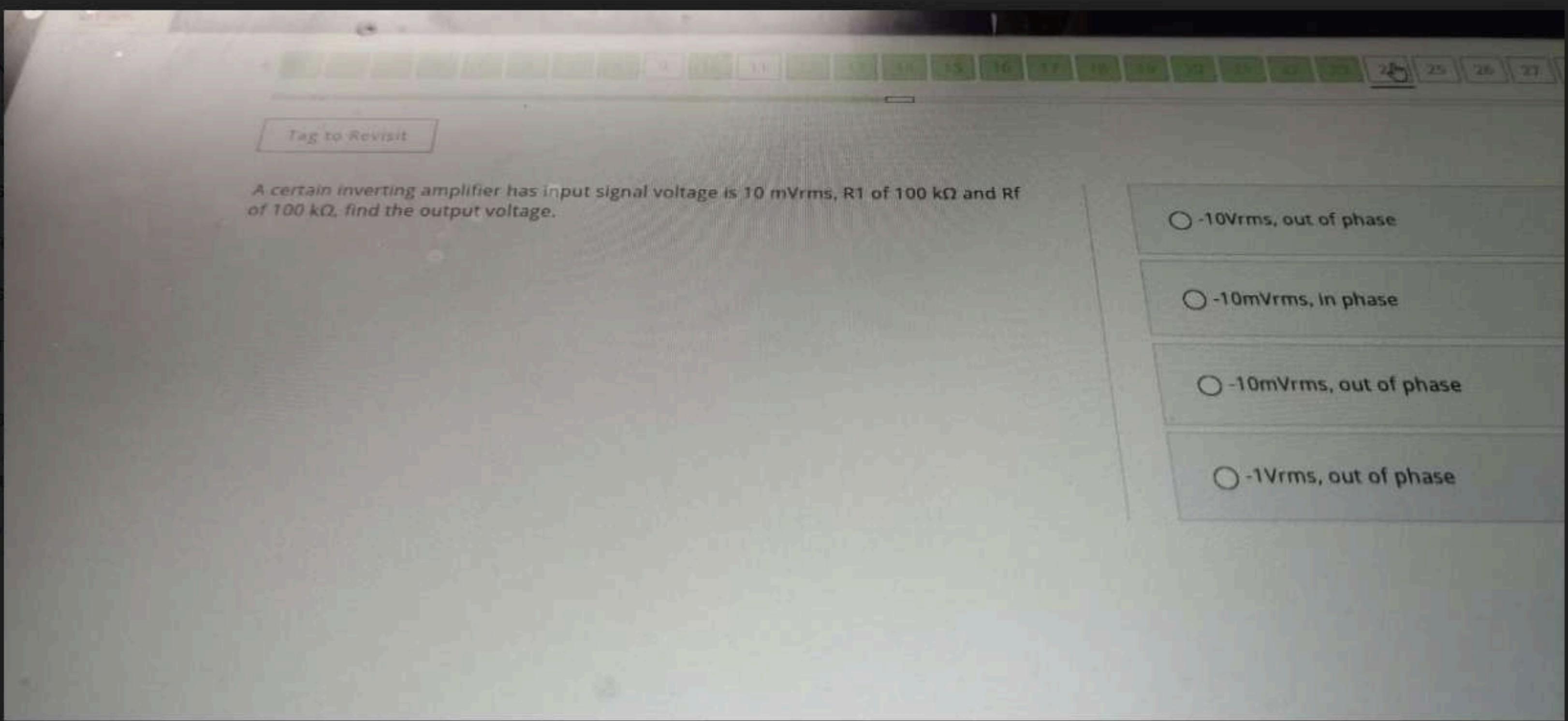

Tag to Revisit

Reset

Calculate current  $I_2$  in the parallel network consisting of  $R_1 = 20 \Omega$  and  $R_2 = 25 \Omega$  and supply voltage is 100 V.  $I_1$  and  $I_2$  are the currents flowing through  $R_1$  and  $R_2$  respectively.

12A

9A

5A

4A

Tag to Revisit

Reset

If self inductance is given by L, current is I then self induced EMF is given by

$e = -L \frac{dI}{dt}$

$e = -N \frac{dI}{dt}$

$e = -L \frac{d\phi}{dt}$

$e = -N \frac{dL}{dt}$





Tag to Revisit

While applying Super position Principle voltage source is replaced by a

Short circuit

Open circuit

battery

resistance

Tag to Revisit

Calculate current  $I_1$  in the parallel network consisting of  $R_1 = 20 \Omega$  and  $R_2 = 25 \Omega$  and supply voltage is 100 V.  $I_1$  and  $I_2$  are the currents flowing through  $R_1$  and  $R_2$  respectively.

5A

12A

4A

9A

◀ 1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25 26 27 ▶

47 of 50 answered

Tag to Revisit



Reset

Next &gt;

A certain inverting amplifier has input signal voltage is 1 Vrms, R<sub>1</sub> of 22 kΩ and R<sub>f</sub> of 220 kΩ, find the output voltage.

-10mVrms,out of phase

-10Vrms, out of phase

-10Vrms, out of phase

-10Vrms, out of phase

Untag

A voltage  $V = 300 \cos 100t$  is applied to a HWR with  $RL = 5 \text{ k}\Omega$ , the rectifier may be represented by an ideal diode in series with a resistance of  $1\text{k}\Omega$ . The value of  $Im$  is given as

 50 mA 56.56 mA 52 mA 500mA

RESET

NEXT

Tag to Revisit

If  $R = 32 \Omega$ ,  $XL = 34 \Omega$  are connected in series then impedance  $Z =$

46.69Ω

4Ω

2Ω

46Ω

Which is the correct sequential order of steps to be undertaken while applying Thevenin's theorem? A. Calculation of Thevenin's equivalent voltage B. Removal of branch impedance through which required current is to be estimated C. Estimation of equivalent impedance between two terminals of the branch D. Estimation of branch current by schematic representation of Thevenin's equivalent circuit

B, C, D, A

D, A, C, B

B, A, C, D

A, C, B, D

In series resonant circuit, impedance is \_\_\_\_\_

Minimum

None

Maximum

Zero

When an AC signal is connected across the capacitive circuits,

V lags I by 90 degrees

V leads I by 90 degrees

I and V are in phase

V leads I by 180 degrees

Tag to Revisit

Calculate current  $I_2$  in the parallel network consisting of  $R_1 = 20 \Omega$  and  $R_2 = 25 \Omega$  and supply voltage is 100 V.  $I_1$  and  $I_2$  are the currents flowing through  $R_1$  and  $R_2$  respectively.

12A

9A

5A

4A

[Tag to Revisit](#)[Reset](#)[Next](#)

If  $R_1 = 2 \Omega$ ,  $R_2 = 4 \Omega$ ,  $R_3 = 8 \Omega$  are connected in series and 2 A current is flowing through the series combination. Voltage drop  $V_{R2} =$

 4 V 16 V 28 V 8 V

Tag to Revisit

If  $R_1 = 2 \Omega$ ,  $R_2 = 4 \Omega$ ,  $R_3 = 8 \Omega$  are connected in series and 2 A current is flowing through the series combination. Voltage drop  $V_{R2} =$

4 V

16 V

28 V

8 V

Which of the following is the wrong expression?

$i_1N_2 = i_2N_1$

$i_1N_1 = i_2N_2$

$i_1v_1 = i_2v_2$

$v_2N_1 = v_1N_2$

Find the total voltage applied in a series RLC circuit when  $I = 3 \text{ mA}$ ,  $V_L = 30 \text{ V}$ ,  $V_C = 18 \text{ V}$  and  $R = 1000 \Omega$ .

3.95V

6.67V

32.67V

51 V

Tag to Revisit

If star values of the three resistances are 6,6,6 then its equivalent delta values are

18,18,18 ohm

2,2,2 ohm

6,6,6 ohm

16,16,16 ohm

A silicon transistor connected in common emitter configuration with voltage divider bias is shown in figure. If  $V_{cc} = 10V$ ,  $R_c = 1\text{ k}\Omega$ ,  $R_1 = 100\text{ k}\Omega$ ,  $R_2 = 10\text{ k}\Omega$ ,  $R_E = 100\text{ }\Omega$ . The Q point is at:

1.8 mA, 6.7V

1.2 mA, 7.8V

2.5 mA, 5.5 V

2 mA, 7.8 V

Reset

Next

Tag to Revisit

A power-supply transformer has a turns ratio of 5:1. What is the secondary voltage if the primary is connected to a 120 V rms source?

24 Vrms

48 Vrms

60 Vrms

15 Vrms

[Tag to Revisit](#)[Reset](#)[Next >](#)

Calculate the total current in the parallel network consisting of  $R_1 = 20 \Omega$  and  $R_2 = 25 \Omega$  and supply voltage is 100 V.  $I_1$  and  $I_2$  are the currents flowing through  $R_1$  and  $R_2$  respectively.

 9A 4A 12A 5A

Reset

Next >

Tag to Revisit

Holes in n-type semiconductor are

minority carriers that are thermally produced

majority carriers that are thermally produced

minority carriers that are produced by doping

majority carriers that are produced by doping

If  $R_1 = 2 \Omega$ ,  $R_2 = 4 \Omega$ ,  $R_3 = 8 \Omega$  are connected in series and 2 A current is flowing through the series combination. Voltage drop  $V_{R2} =$

8 V

16 V

4 V

28 V

[Reset](#)[Next >](#)[Tag to Revisit](#)

Calculate the effective resistance of parallel combination of  $R_1 = 6.8 \Omega$ ,  $R_2 = 4.7 \Omega$  and  $R_3 = 2.2 \Omega$ .

0.213 ohms

0.815 ohms

0.147 ohms

0.455 ohms