
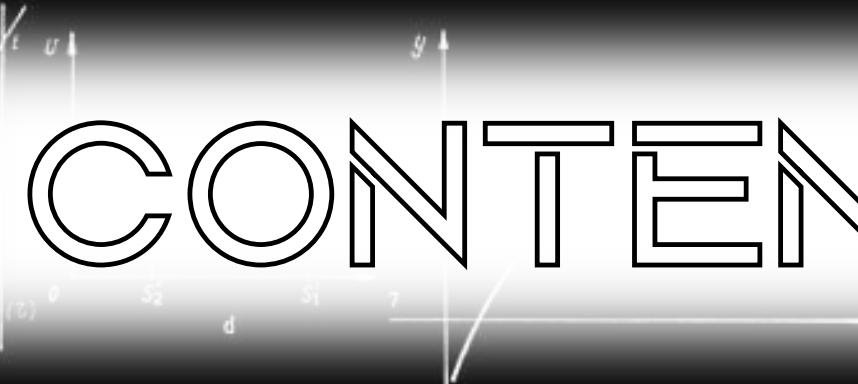


INTEGRAL CALCULUS IN ELECTRICAL CIRCUITS

Group Presentation in Integral Calculus


CONTENTS

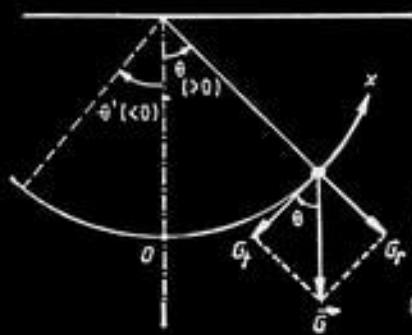

$$E_p = E_{p_{\max}} \Rightarrow \sin^2\left(3t_p + \frac{\pi}{3}\right) = 1 \\ = \sin\left(\frac{\pi}{2} + n\pi\right); n = 0, 1, 2, \dots$$

$$t_p = \frac{\pi}{3}\left(n + \frac{1}{6}\right); n = 0, 1, 2, \dots$$
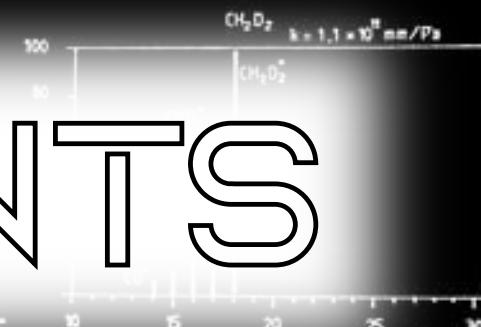
$$E_c = E_{c_{\max}} \Rightarrow \cos^2\left(3t_c + \frac{\pi}{3}\right) = 1 \Rightarrow \cos\left(3t_c + \frac{\pi}{3}\right) = \pm 1 = \cos(n\pi) \Rightarrow t_c = \frac{\pi}{3}\left(n - \frac{1}{3}\right)$$



$$E_p = E_{p_{\max}} \Rightarrow \sin^2\left(3t_p + \frac{\pi}{3}\right) = 1 \\ = \sin\left(\frac{\pi}{2} + n\pi\right); n = 0, 1, 2, \dots$$


$$t_p = \frac{\pi}{3}\left(n + \frac{1}{6}\right); n = 0, 1, 2, \dots$$

$$E_c = E_{c_{\max}} \Rightarrow \cos^2\left(3t_c + \frac{\pi}{3}\right) = 1 \Rightarrow \cos\left(3t_c + \frac{\pi}{3}\right) = \pm 1 = \cos(n\pi) \Rightarrow t_c = \frac{\pi}{3}\left(n - \frac{1}{3}\right)$$


$$\omega = \sqrt{\frac{k}{m}} = \sqrt{\frac{4\pi m_1 K_p}{3m_1}} = \sqrt{\frac{4\pi K_p}{3}}$$

$$\omega = \sqrt{\frac{g_0}{R_0}},$$

$$= 5,03 \cdot 10^3 \text{s}.$$

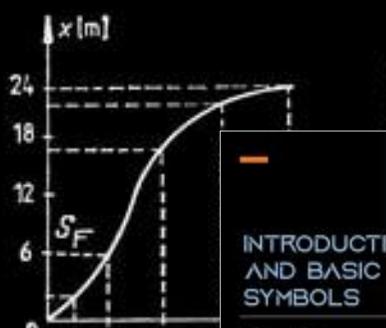

$$\frac{1 - \left(-\frac{1}{n+2}\right)^{n+1}}{1} + \frac{1}{1} \cdot \frac{1 - \left(-\frac{1}{n+1}\right)}{1} = \int_{-a}^0 x^2 e^{ax} dx = \frac{1}{a} (x^2 e^{ax}) \Big|_{-a}^0 - \frac{2}{a} \int_{-a}^0 x e^{ax} dx$$

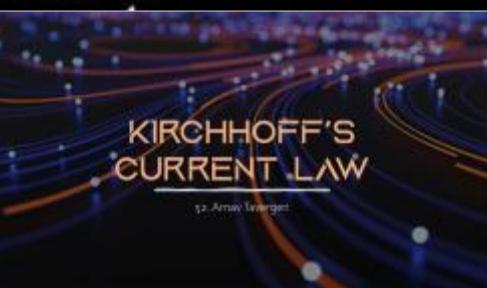


**BASIC EXAMPLE
INCLUDING
KIRCHHOFF'S
CURRENT LAW**

5.1. Balraj Tavanandi

**KIRCHOFF'S
VOLTAGE LAW**

6.0. Ashutosh Ukkade

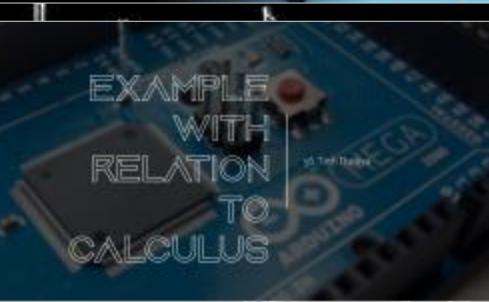


**APPLICATION
OF CALCULUS
IN DAILY LIFE
AND OTHER
FIELDS**

7.1. Vedant Shinde

**HISTORY AND
EVOLUTION OF
INTEGRAL CALCULUS**

5.4. KRISHNARAJ THADESAR

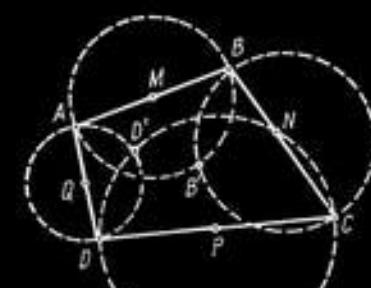

$I[\text{mA}]$	0	0	4	50	104	170
$U[\text{V}]$	0	0.5	0.6	0.8	0.9	1.0
$I[\text{mA}]$	0	-1.05	-2.1	-3.2	-4.2	-5.3
$U[\text{V}]$	0	-1	-2	-3	-4	-5
$I[\text{mA}]$	0	0	4	44	115	175

$$(x+t)I_2 + (xt-yz)I_3 = 0.$$

$$\begin{pmatrix} x & y \\ z & t \end{pmatrix} - \begin{pmatrix} x+t & 0 \\ 0 & x+t \end{pmatrix} = \begin{pmatrix} -t & y \\ z & -x \end{pmatrix}.$$



$$Q = \frac{Q_1 + Q_2}{2} = 13,275 \cdot 10^{-9} \text{ C}$$


$$U = \frac{Q}{C_1} = \frac{3}{2} U_0 = 1500 \text{ V}$$

$$= \frac{1}{2} Q U = \frac{9}{8} \epsilon_0 \frac{S}{d_1} U_0^2 = 9,956 \cdot 10^{-6} \text{ J}$$



INTRODUCTION AND BASIC SYMBOLS



71. Pranav Walvekar

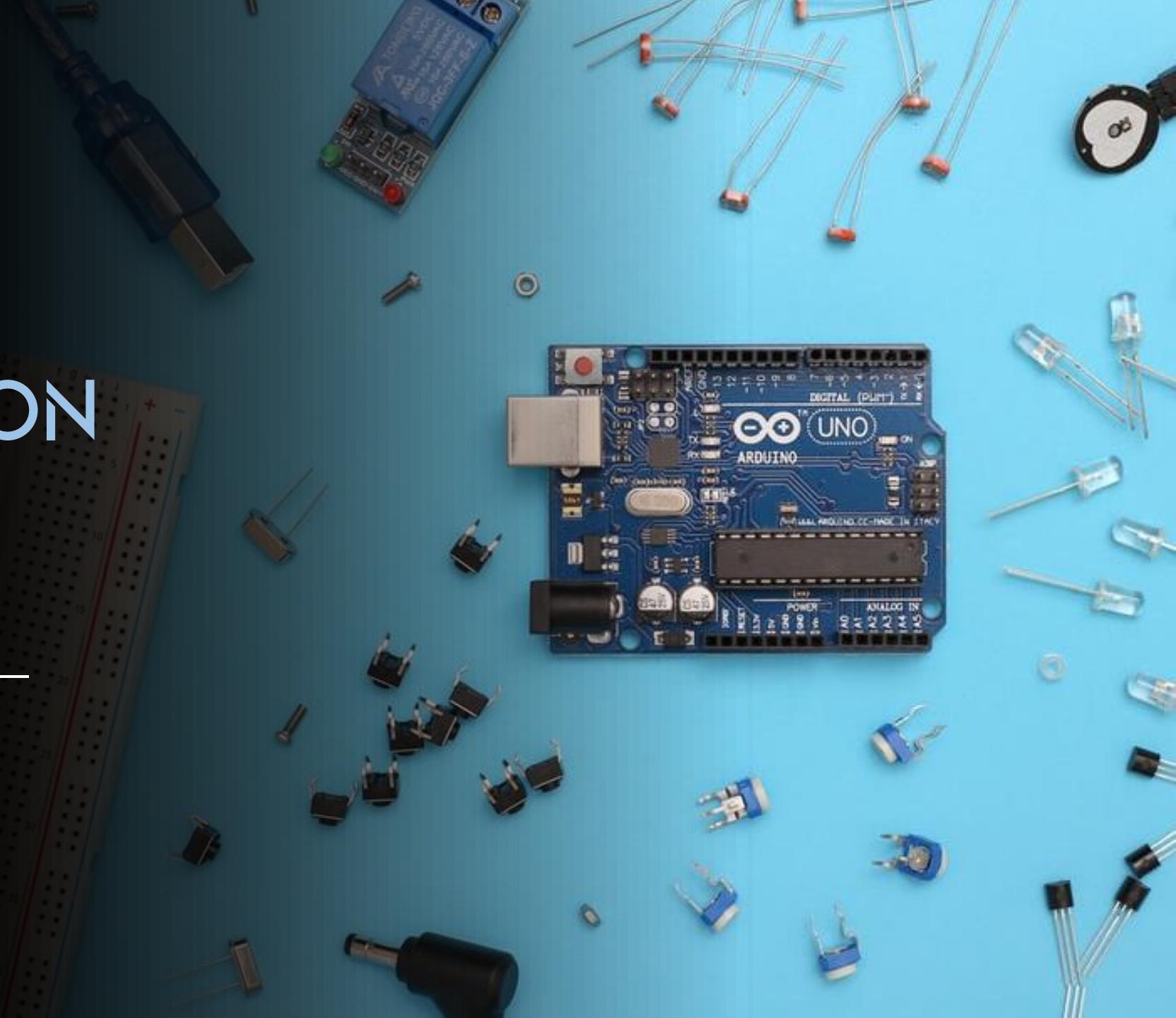


WHAT ARE ELECTRIC CIRCUITS?

The electric circuits are closed-loop or path which forms a network of electrical components, where electrons are able to flow. This path is made using electrical wires and is powered by a source, like a battery.

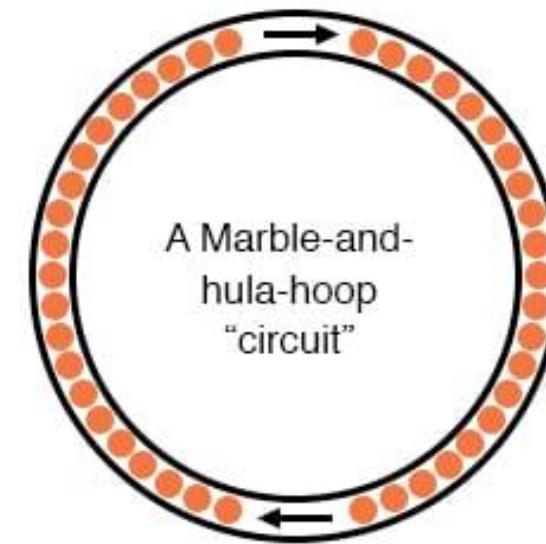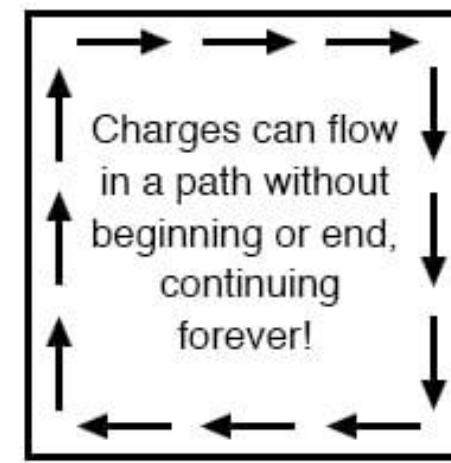The start of the point from where the electrons start flowing is called the source whereas the point where electrons leave the electrical circuit is called the return.



BASIC SYMBOLS

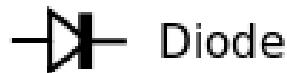

Diode



Capacitor




Inductor



Resistor



DC voltage source

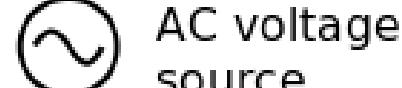

AC voltage source



And gate



Nand gate



Or gate



Nor gate



Xor gate




Inverter
(Not gate)



OPEN SWITCH



CLOSED SWITCH

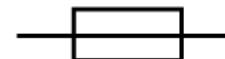

FUSE



BATTERY



CELL



AMMETER




BUZZER



LAMP/BULB



VOLTMETER

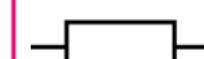

RESISTOR




BASIC FORMULAS

Quantity	Formula	Notations
Electric current	$I = \frac{Q}{t}$	<ul style="list-style-type: none"> I is the current Q is the charge flowing t is the time period
Resistance	$R = \rho \cdot \frac{L}{A}$	<ul style="list-style-type: none"> R is the resistance ρ is the resistivity value of the wire L is the length of the wire A is the cross-sectional area
Voltage	$\Delta V = I \cdot R$	<ul style="list-style-type: none"> ΔV is the electric potential difference
Power	$P = \frac{\Delta E}{t}$	<ul style="list-style-type: none"> P is the power ΔE is the energy gain or loss t is the time period
Series circuit	$R_{eq} = R_1 + R_2 + R_3 + \dots$	<ul style="list-style-type: none"> R_{eq} is the total resistance of the resistors placed in series R_1, R_2, \dots are the resistors placed in series
Parallel circuit	$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$	<ul style="list-style-type: none"> R_{eq} is the total resistance of the resistors placed in parallel R_1, R_2, \dots are the resistors placed in parallel

KIRCHHOFF'S CURRENT LAW

52. Arnav Tavergeri

KIRCHHOFF'S CURRENT LAW

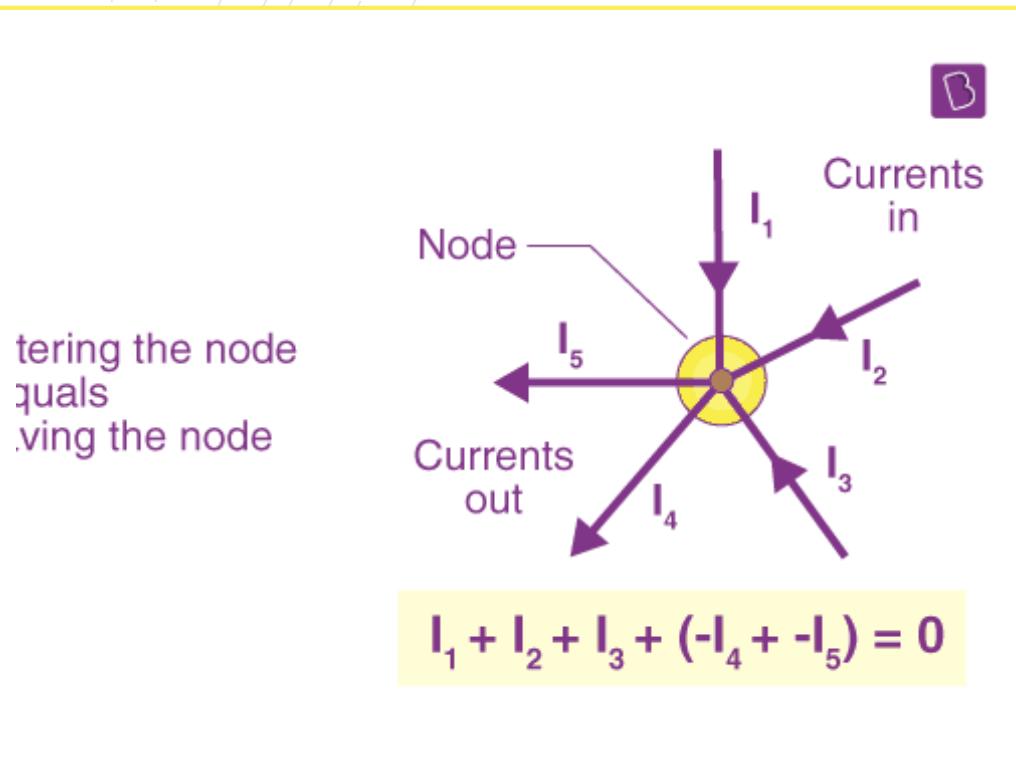

- According to this law, the total current entering a junction is equal to the charge leaving the node as no charge is lost.
- The equation for this diagram is $I_1 + I_2 + I_3 - I_4 - I_5 = 0$
- This law is applicable only when electric charge in circuit is constant.




- The kirchhoff's circuit law (KCL) is also based upon the property of Conservation of Charge. It relies on the fact that net charge in wires and components is constant.
- This law has many uses but at it's most basic, it is used with Ohm's law to perform Nodal Analysis.



BASIC EXAMPLE INCLUDING KIRCHHOFF'S CURRENT LAW

51. Balraj Tavanandi

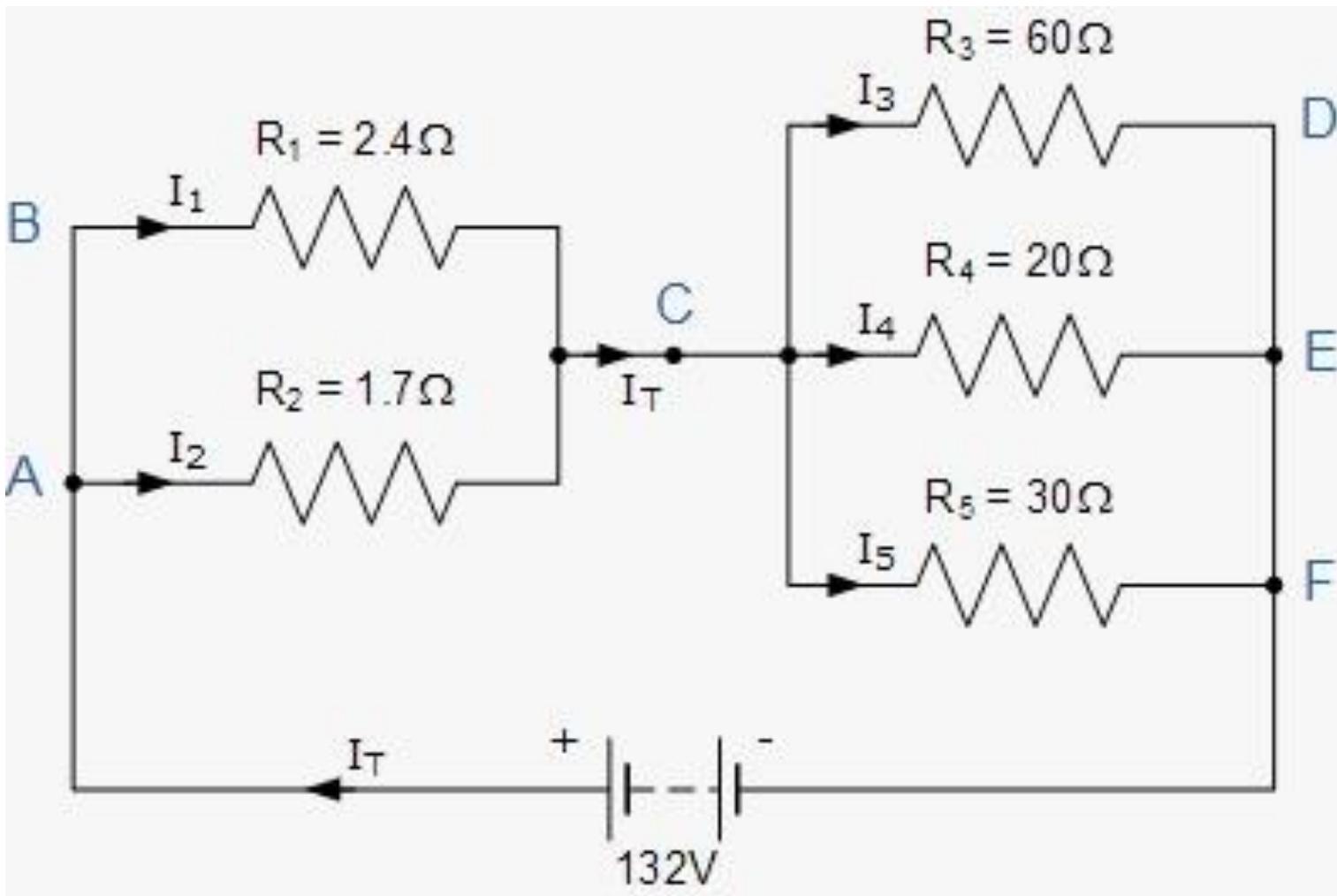PROBLEM 1
– FINDING
CURRENT
THROUGH
EACH
RESISTOR



CIRCUIT RESISTANCE R_{AC} AND R_{CF}

$$\frac{1}{R_{(AC)}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{2.4} + \frac{1}{1.7}$$

$$\frac{1}{R_{(AC)}} = 1 \quad \therefore R_{(AC)} = 1\Omega$$

$$\frac{1}{R_{(CF)}} = \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} = \frac{1}{60} + \frac{1}{20} + \frac{1}{30}$$


$$\frac{1}{R_{(CF)}} = 0.1 \quad \therefore R_{(CF)} = 10\Omega$$

CIRCUIT CURRENT I_T AND EQUIVALENT KCL CIRCUIT

$$R_T = R_{(AC)} + R_{(CF)} = 1 + 10 = 11 \Omega$$

$$I_T = \frac{V}{R_T} = \frac{132}{11} = 12 \text{ Amperes}$$

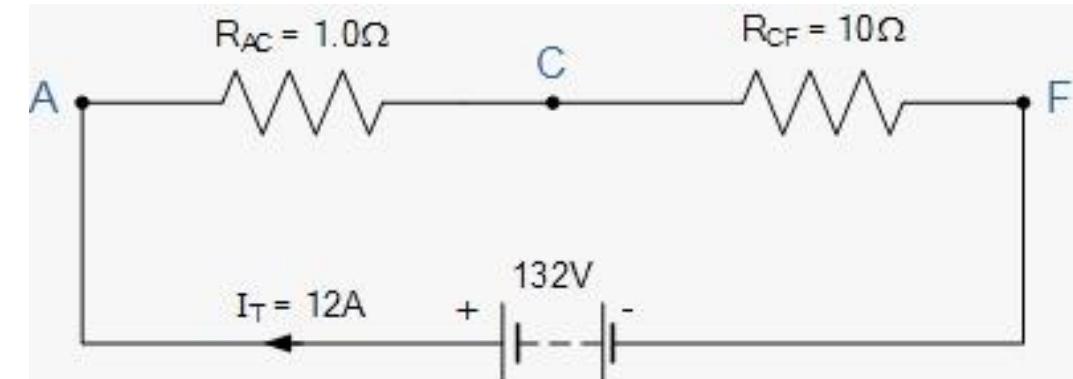Therefore, $V = 132V$, $R_{AC} = 1\Omega$, $R_{CF} = 10\Omega$'s and $I_T = 12A$.



RESULT

We can also double check to see if Kirchhoff's Current Law holds true as the currents entering the junction are positive, while the ones leaving the junction are negative, thus the algebraic sum is: $I_1 + I_2 - I_3 - I_4 - I_5 = 0$ which equals $5 + 7 - 2 - 6 - 4 = 0$.

So we can confirm by analysis that Kirchhoff's current law (KCL) which states that the algebraic sum of the currents at a junction point in a circuit network is always zero is true.

$$V_{AC} = I_T \times R_{AC} = 12 \times 1 = 12 \text{ Volts}$$

$$V_{CF} = I_T \times R_{CF} = 12 \times 10 = 120 \text{ Volts}$$

$$I_1 = \frac{V_{AC}}{R_1} = \frac{12}{2.4} = 5 \text{ Amps}$$

$$I_2 = \frac{V_{AC}}{R_2} = \frac{12}{1.7} = 7 \text{ Amps}$$

$$I_3 = \frac{V_{CF}}{R_3} = \frac{120}{60} = 2 \text{ Amps}$$

$$I_4 = \frac{V_{CF}}{R_4} = \frac{120}{20} = 6 \text{ Amps}$$

$$I_5 = \frac{V_{CF}}{R_5} = \frac{120}{30} = 4 \text{ Amps}$$

KIRCHOFF'S VOLTAGE LAW

6o. Ashutosh Ukande

STATEMENT

Kirchhoff's voltage law states that the voltage around a loop equals the sum of every voltage drop in the same loop for any closed network and equals zero.

$$\sum_{k=1}^n V_k = 0$$

EXAMPLE WITH RELATION TO CALCULUS

56. Tirth Thesiya

PROBLEM 2

In an electric circuit containing an inductance $L = 640 \text{ H}$; a resistance $R = 250\Omega$ & voltage $\mathcal{E} = 500 \text{ V}$. Find current ' i ' at any time ' t '. Also find time that elapses before the current reaches 90% of its max value.

Given

$$R = 250\Omega ; L = 640H ; E = 500V$$

By KVL;

$$(V.D \text{ across } R) + (V.D \text{ across } L) = E$$

$$\therefore RI + L \frac{di}{dt} = E$$

$$\therefore \frac{di}{dt} + \frac{R}{L} i = \frac{E}{L}$$

$$\therefore \frac{di}{dt} + \frac{250}{640} i = \frac{500}{640}$$

\therefore It is LDE in 'i' ;

So Here

$$P = \frac{25}{64} \quad \text{and} \quad Q = \frac{50}{64}$$

$$\therefore \text{IF} = e^{\int \frac{25}{64} dt} \\ = e^{(25/64)t}$$

$$\therefore \text{G.E. form will be} \\ i \times e^{(25/64)t} = \int e^{(25/64)t} \times \frac{50}{64} dt + K$$

$$\therefore i e^{\frac{25}{64}t} = \frac{50}{64} \int e^{\frac{25}{64}t} dt + K$$

$$\therefore i e^{\frac{25}{64}t} = \frac{25}{32} \times e^{\frac{25}{64}t} + K$$

$$\therefore \varrho = 2 + K e^{-\frac{25}{64}t} - \textcircled{1}$$

At $t=0$; $\dot{\varrho}=0$

$$\therefore \dot{\varrho} = 2 + K$$
$$\therefore \boxed{K = -2}$$

$$\therefore \boxed{\varrho = 2(1 - e^{-\frac{25}{64}t})} - \textcircled{2}$$

for

$$\therefore i_{\max} \Rightarrow t \rightarrow \infty$$

$$\therefore \boxed{i_{\max} = 2(1 - e^{-\infty})}$$
$$\boxed{i_{\max} = 2}$$

$$so \ 90\% \ of \ i_{max} \Rightarrow \frac{90}{100} \times i_{max} = \underline{\underline{1.8}}$$

\therefore at $i = 1.8$; $t = ?$


$$\therefore 1.8 = 2 \left(1 - e^{-\frac{25}{64}t} \right)$$

$$\therefore 0.9 = \left| 1 - e^{-\frac{25}{64}t} \right|$$

$$\therefore e^{-\frac{25}{64}t} = 0.1$$

$$\therefore -\frac{25}{64}t = -\ln(0.1)$$
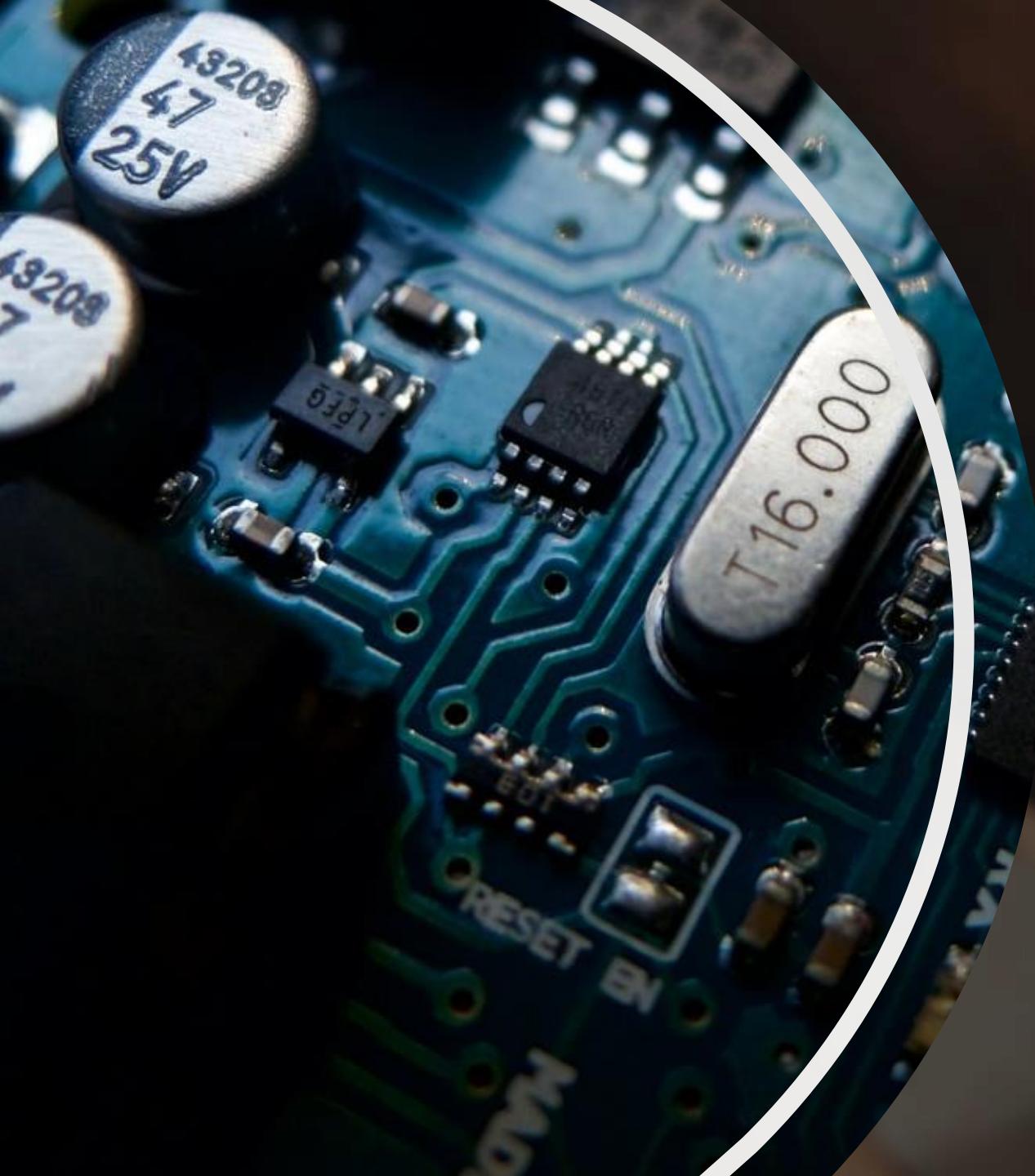
$$\therefore \boxed{t = 5.89 \text{ sec}}$$



APPLICATIONS OF INTEGRAL CALCULUS IN ELECTRIC CIRCUITS AND MUSIC

50. Atharva Tanawade

1. PROTECTING CIRCUITS WITH RESISTORS



As mentioned, KVL applies to simple circuits, such as lighting up an LED. As an LED has a specific junction voltage and the voltage source is often way higher, the difference will have to be dissipated elsewhere in the circuit according to the KVL.



If a limiting resistor is omitted, the copper trace takes the brunt of the voltage difference and gets overheated or broken in the process.


2. SIGNALING

But KVL is more than lighting up an LED without burning the copper trace. The whole idea that defines KVL is about the conservation of energy. The energy source (power voltage), is being dissipated in a closed loop. However, the unchanging constant is the current flowing through it. This phenomenon has led to the popular usage of the 4-20 mA current loop *signaling in industrial application.*

LIMITING RESISTORS

A simple circuit for an LED light KVL is the reason for a limiting resistor in LED circuitry.

WHEATSTONE'S BRIDGE

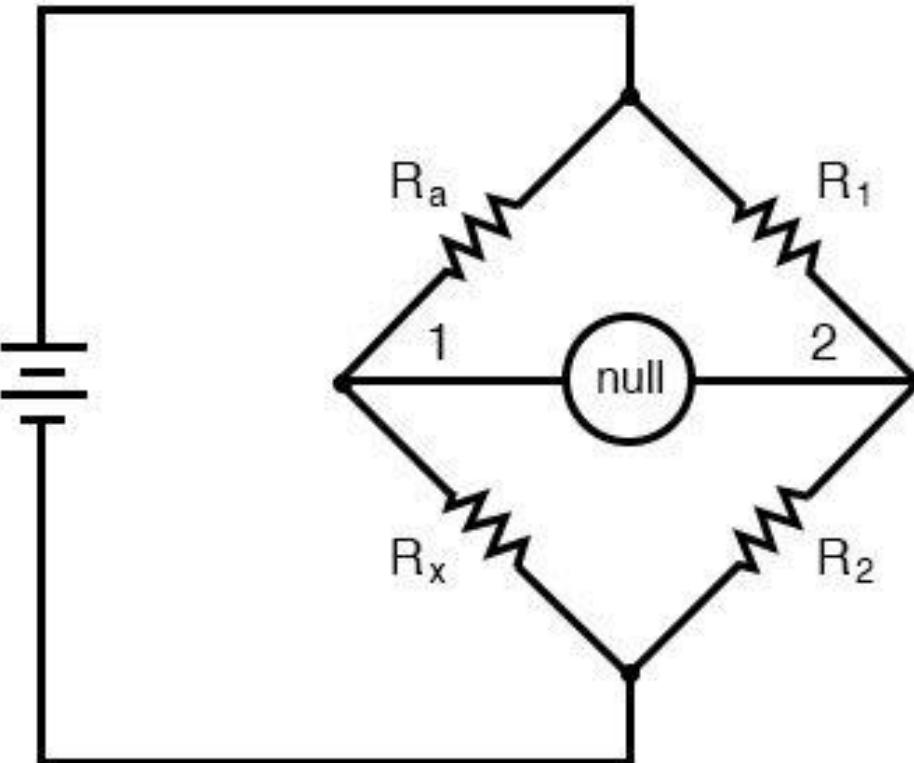

Bridge circuit is balanced when:

$$\frac{R_a}{R_x} = \frac{R_1}{R_2}$$

IC IN ELECTRONICS

Integral and differential calculus are crucial for calculating voltage or current through a capacitor. Integral calculus is also a main consideration in calculating the exact length of a power cable necessary for connecting substations that are miles apart from each other.

EXAMPLES


$i = \frac{dq}{dt}$ (current i Amps is the rate of change of charge q Coulombs).

$i = C \frac{dv}{dt}$ (current i Amps flowing in a capacitor is the capacitance C farads times the rate of change of voltage v Volts across the capacitor).

$v = L \frac{di}{dt}$ (voltage v Volts across an inductor is the inductance L henrys times the rate of change of current i Amps flowing in the inductor).

In an [RLC circuit](#) in series, by combining the above equations and Ohm's law ($v = iR$), we have $Ri(t) + L \frac{di}{dt} + \frac{1}{C} \int_0^t i(T) dT = v(t)$, which may be converted into a second order differential equation to solve for $i(t)$.

YEP, CALCULUS IS EVEN USED IN MUSIC

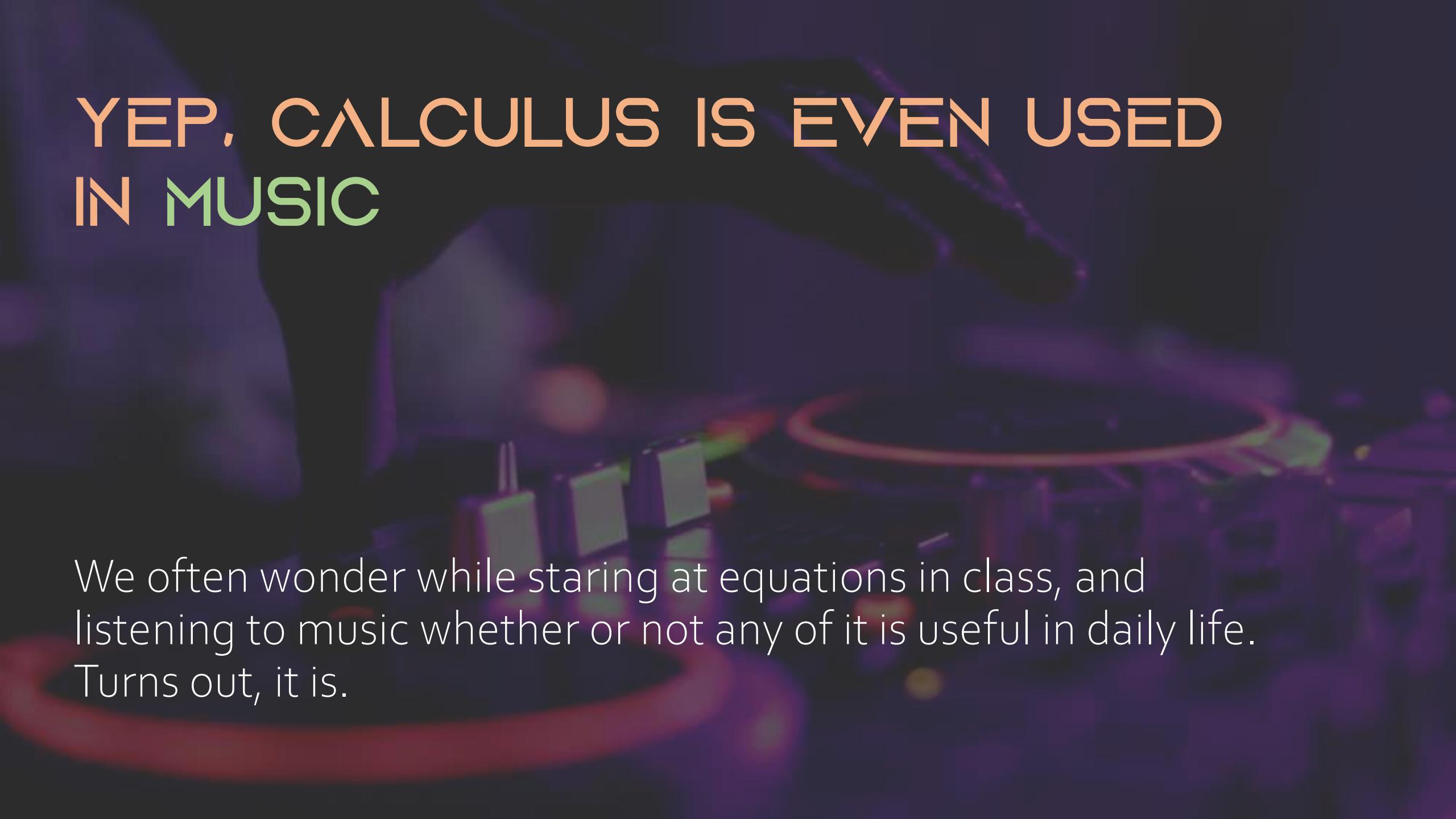

We often wonder while staring at equations in class, and listening to music whether or not any of it is useful in daily life. Turns out, it is.

Harmonics

An oscillation created by a damped harmonic is not infinite, as friction and air resistance will dissipate the energy. Calculus is used to anticipate these motions to make the proper adjustments and provide the best musical experience to the listeners.




ACOUSTICS

Resonance and forced oscillation can be computed using calculus. Air resistance varies at different frequencies and resonates throughout an enclosed space whenever a musical instrument is played. Through calculus, we can make improvements on acoustics and improve the listener's experience.

APPLICATION OF CALCULUS IN DAILY LIFE AND OTHER FIELDS

21. Vedant Shirode



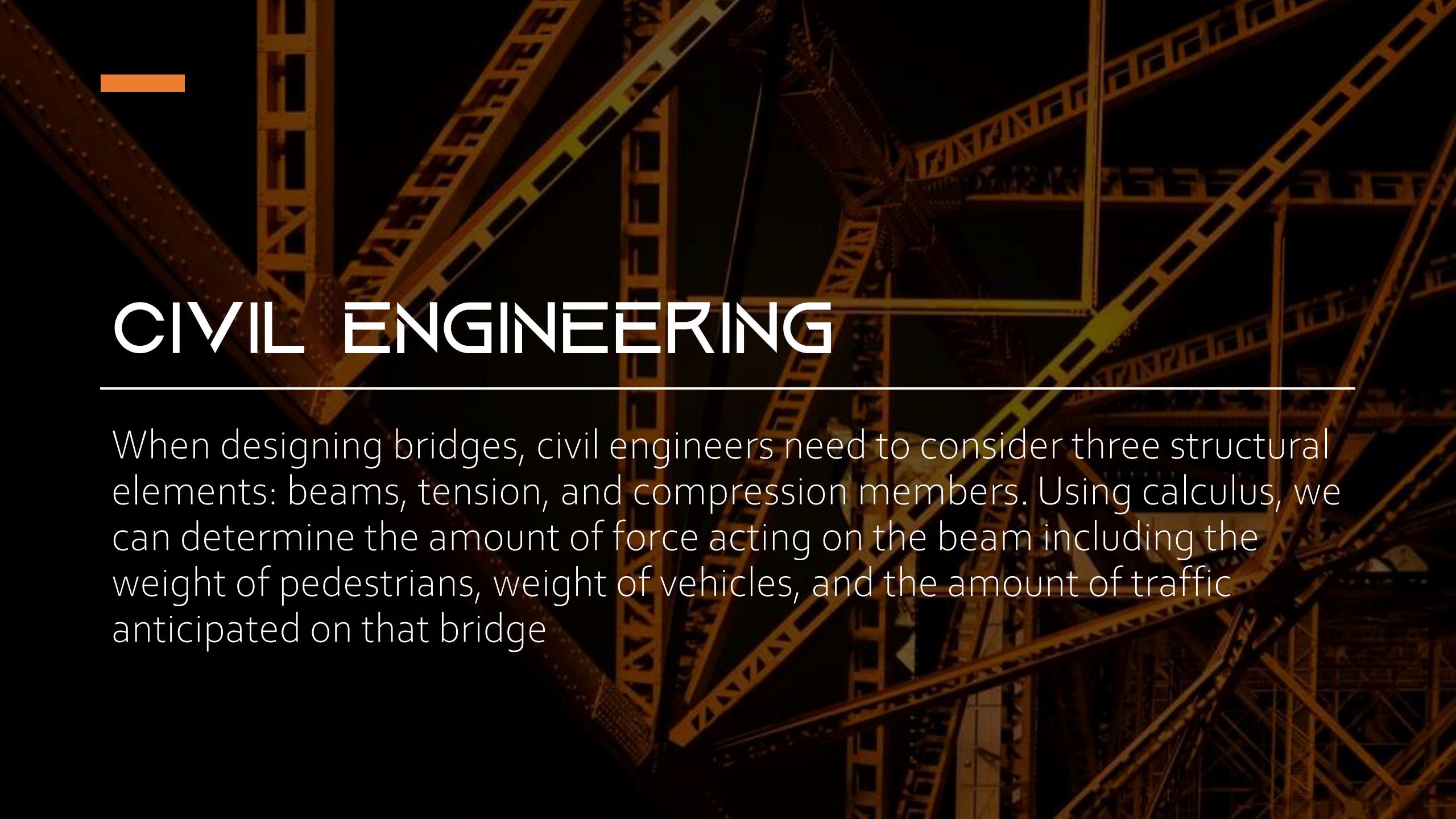


CIVIL ENGINEERING

When designing bridges, civil engineers need to consider three structural elements: beams, tension, and compression members. Using calculus, we can determine the amount of force acting on the beam including the weight of pedestrians, weight of vehicles, and the amount of traffic anticipated on that bridge



MECHANICAL ENGINEERING

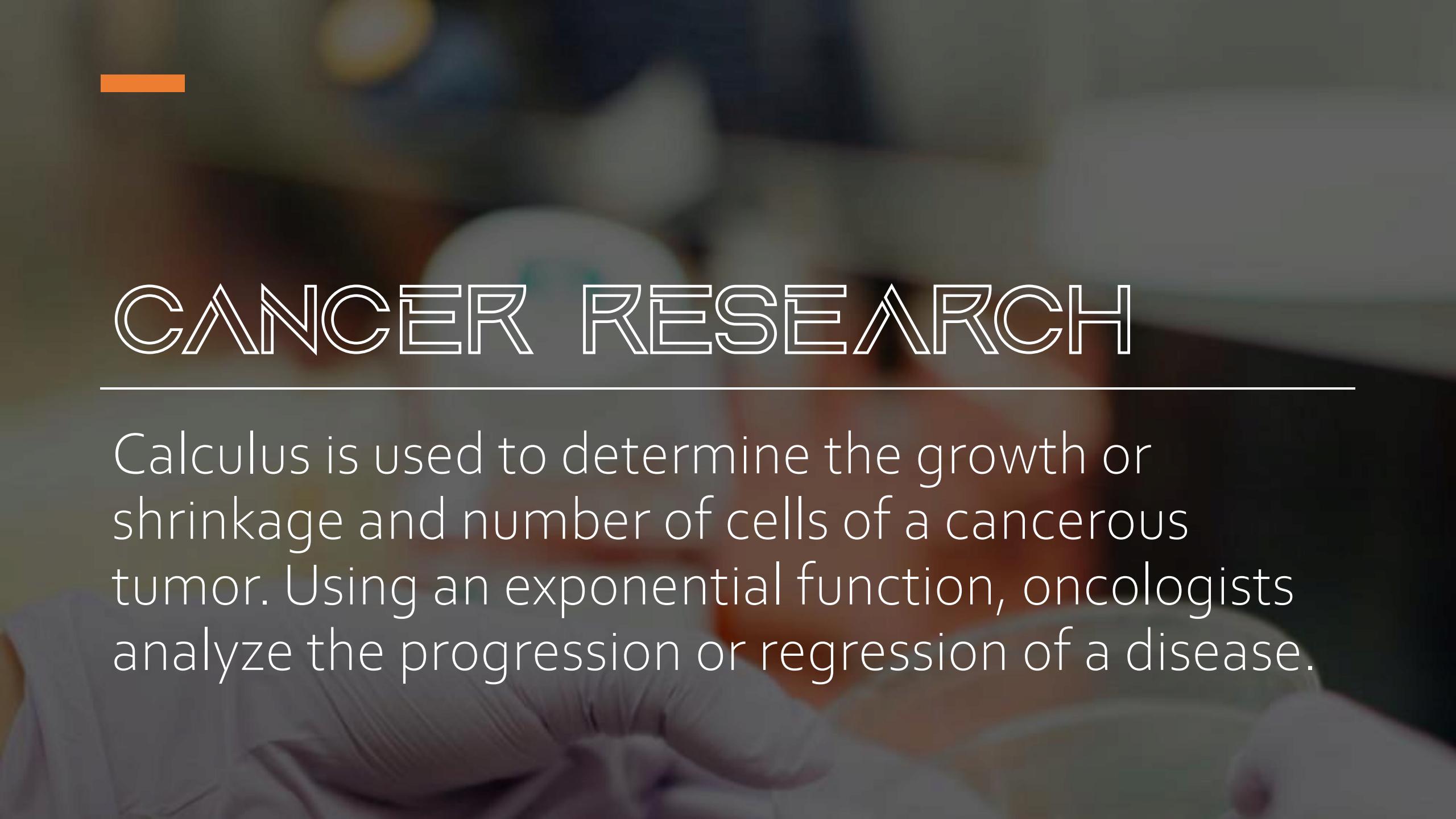The pump used for filling an overhead tank, gardening tools, cars, motorcycles, robots, and many household appliances are designed using the principles of calculus.



CANCER RESEARCH

Calculus is used to determine the growth or shrinkage and number of cells of a cancerous tumor. Using an exponential function, oncologists analyze the progression or regression of a disease.

BACTERIAL GROWTH


Biologists use differential calculus to compute the exact bacterial growth rate in a culture by varying environmental factors such as temperature and food source.



HEART TRANSPLANTS

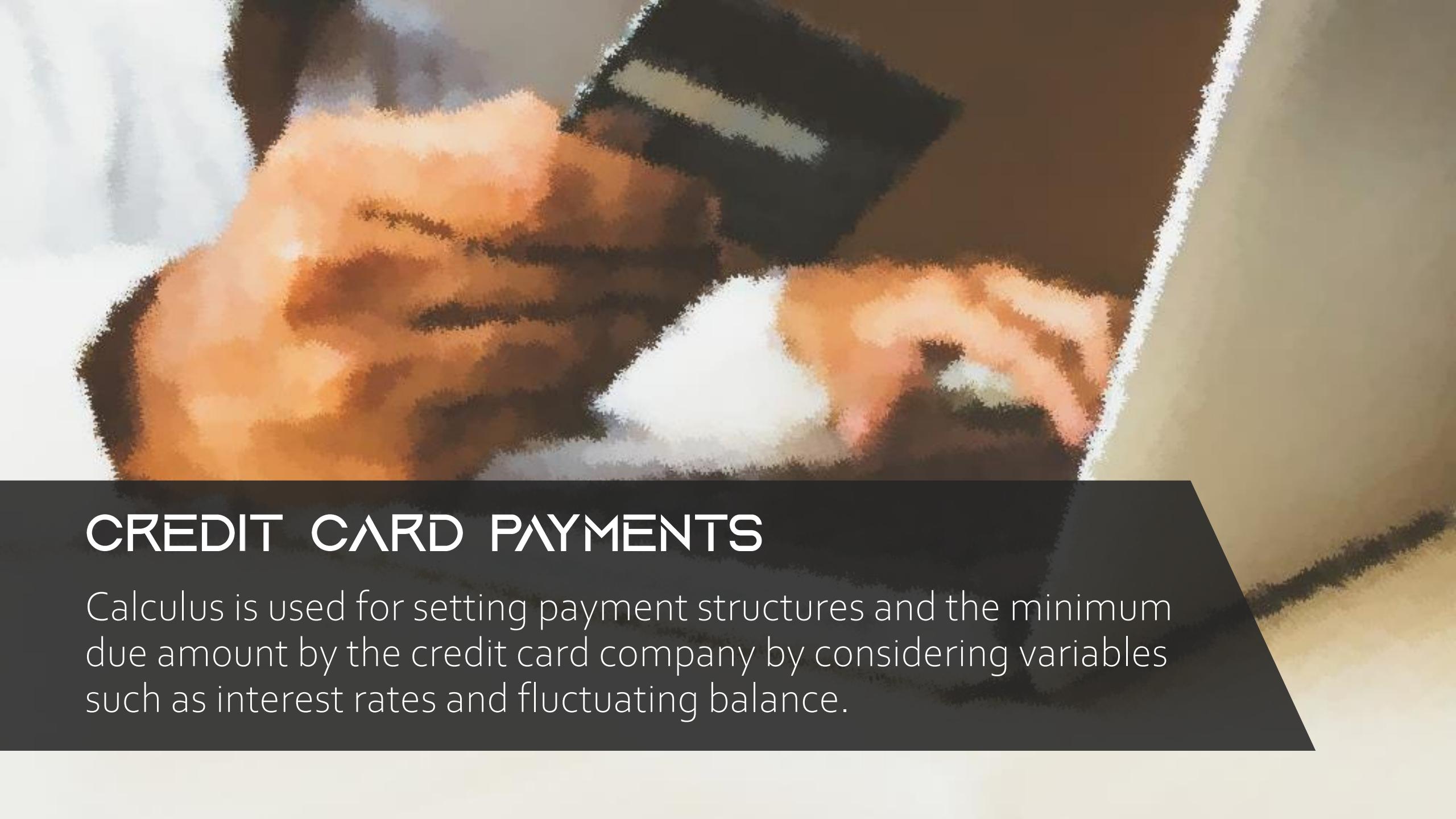
Cardiologists use differential calculus to understand the blood flow dynamics needed for building an artificial aorta model in order to make sure it is placed correctly during transplant.






CREDIT CARD PAYMENTS

Calculus is used for setting payment structures and the minimum due amount by the credit card company by considering variables such as interest rates and fluctuating balance.

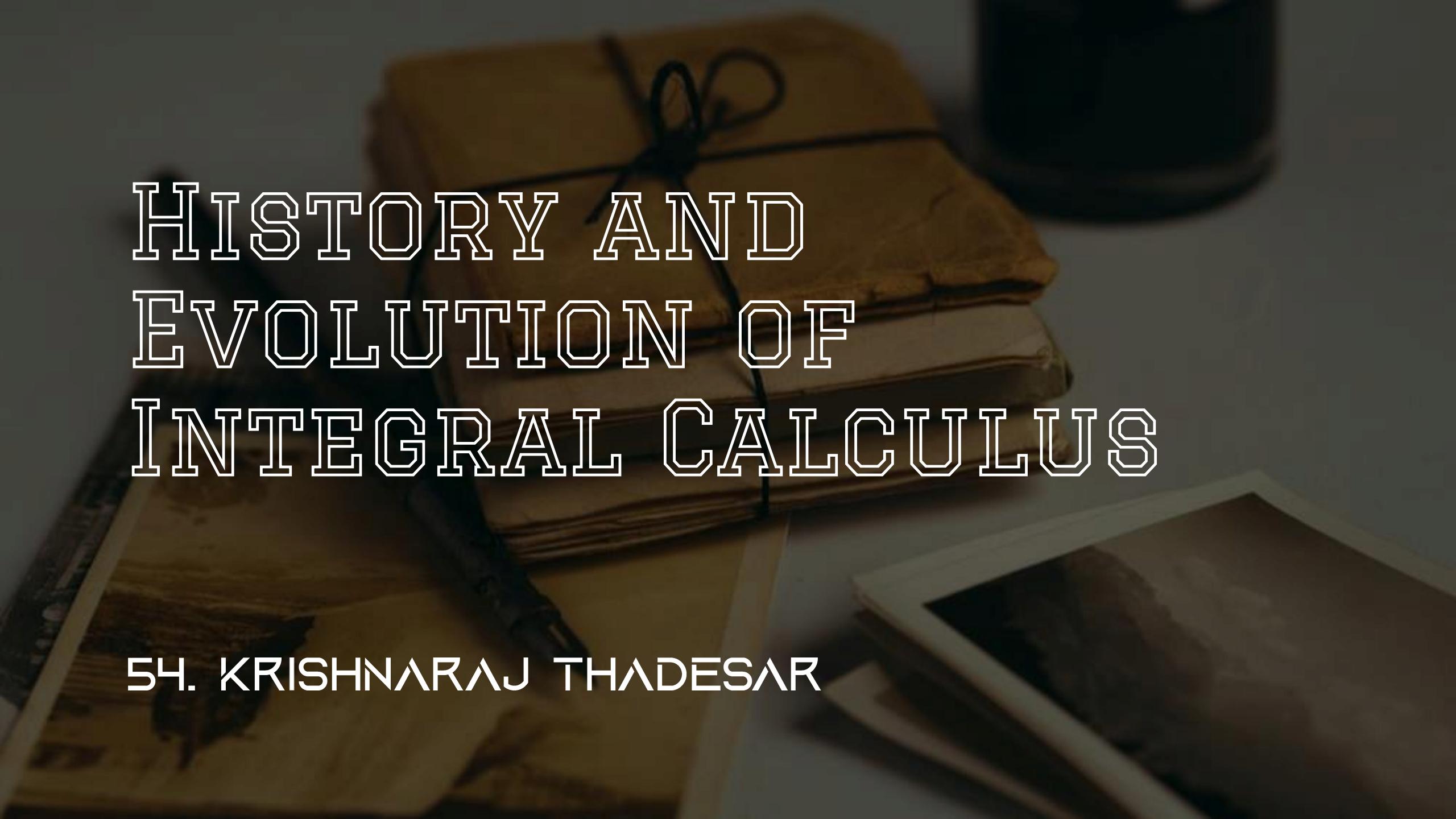The background of the slide features a stack of several old, yellowed books. A red ribbon bookmark is tied around the middle of the top book. The spines of the books are visible, showing various titles and authors. The overall lighting is warm and slightly dim, giving it an aged appearance.


HISTORY AND EVOLUTION OF INTEGRAL CALCULUS

54. KRISHNARAJ THADESAR

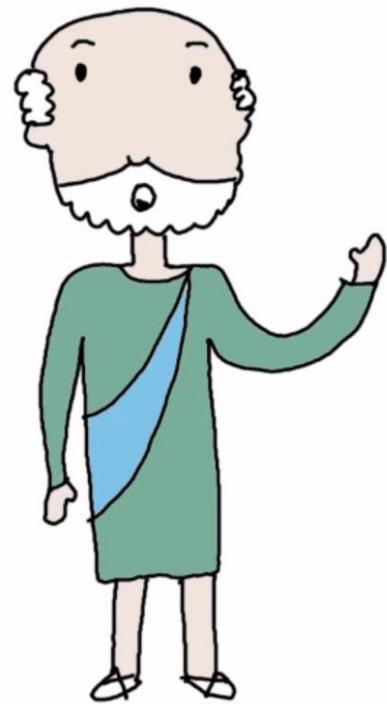


Archimedes

240 BC
"method of exhaustion"


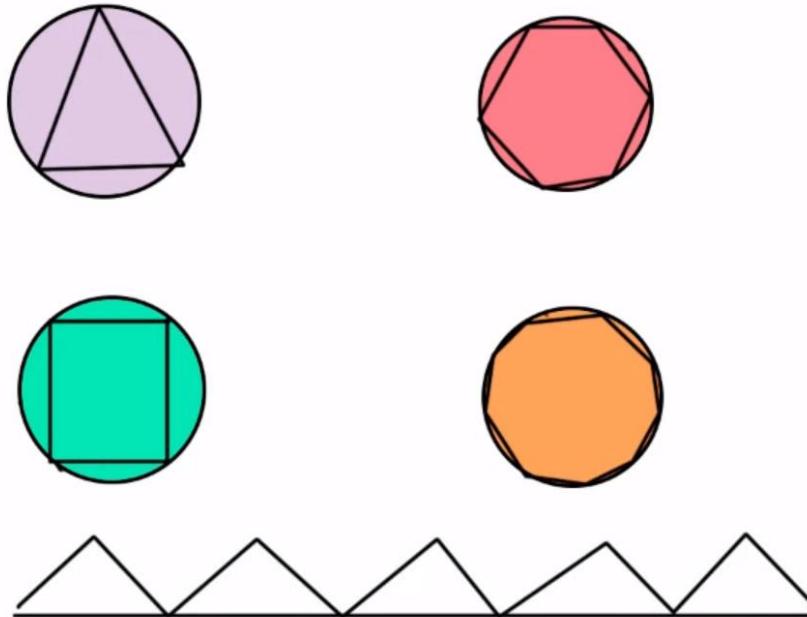


⋮



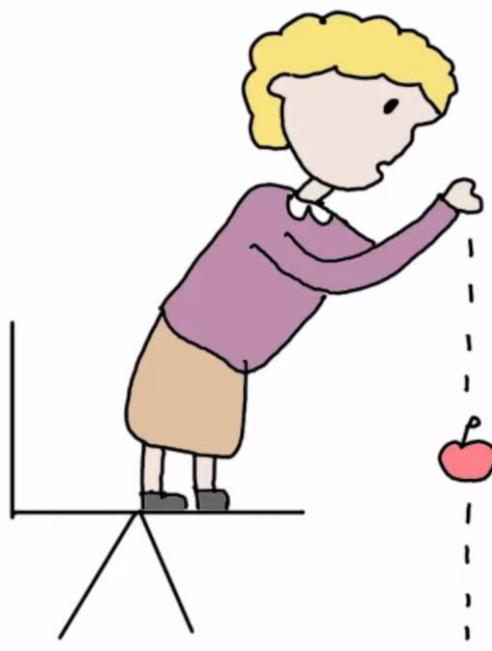


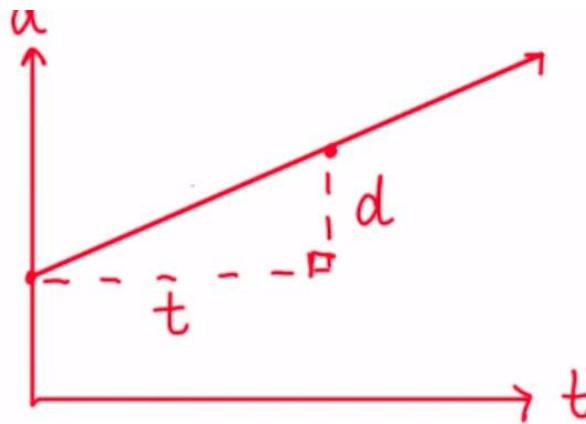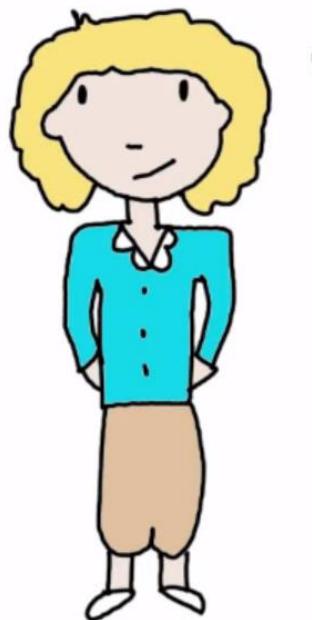How do I find the gradient anywhere on the function?





constant gradient

$$s = \frac{d}{t}$$

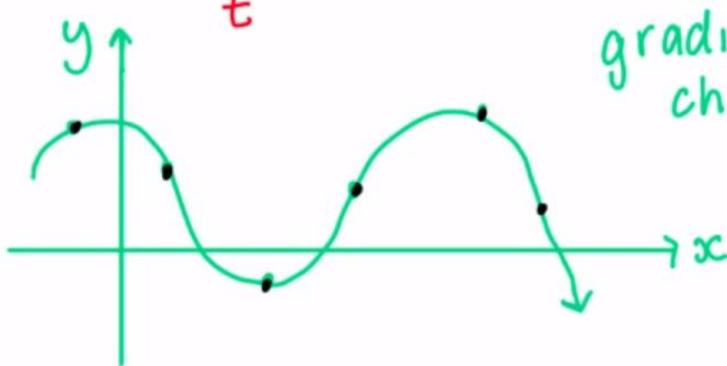


gradient always changing


I've got it!
THE DERIVATIVE!

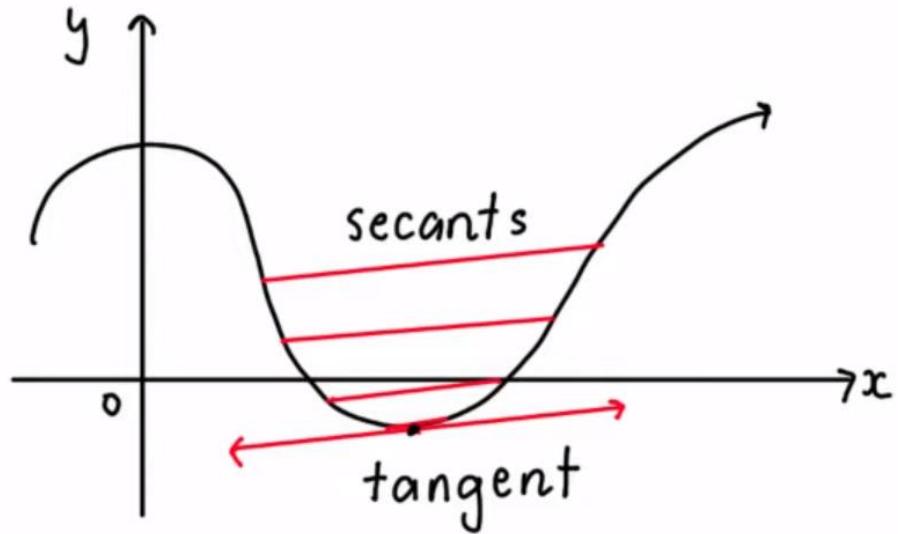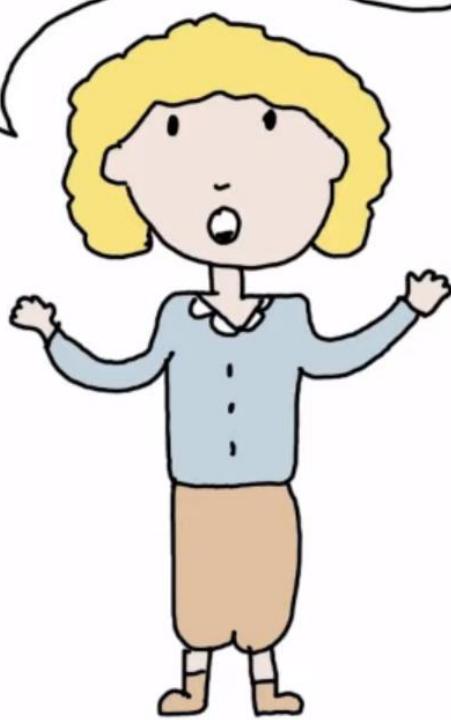

$$\text{secant} = \frac{\Delta y}{\Delta x} \rightarrow \frac{0}{0} \rightarrow \text{tangent}$$

The Derivative

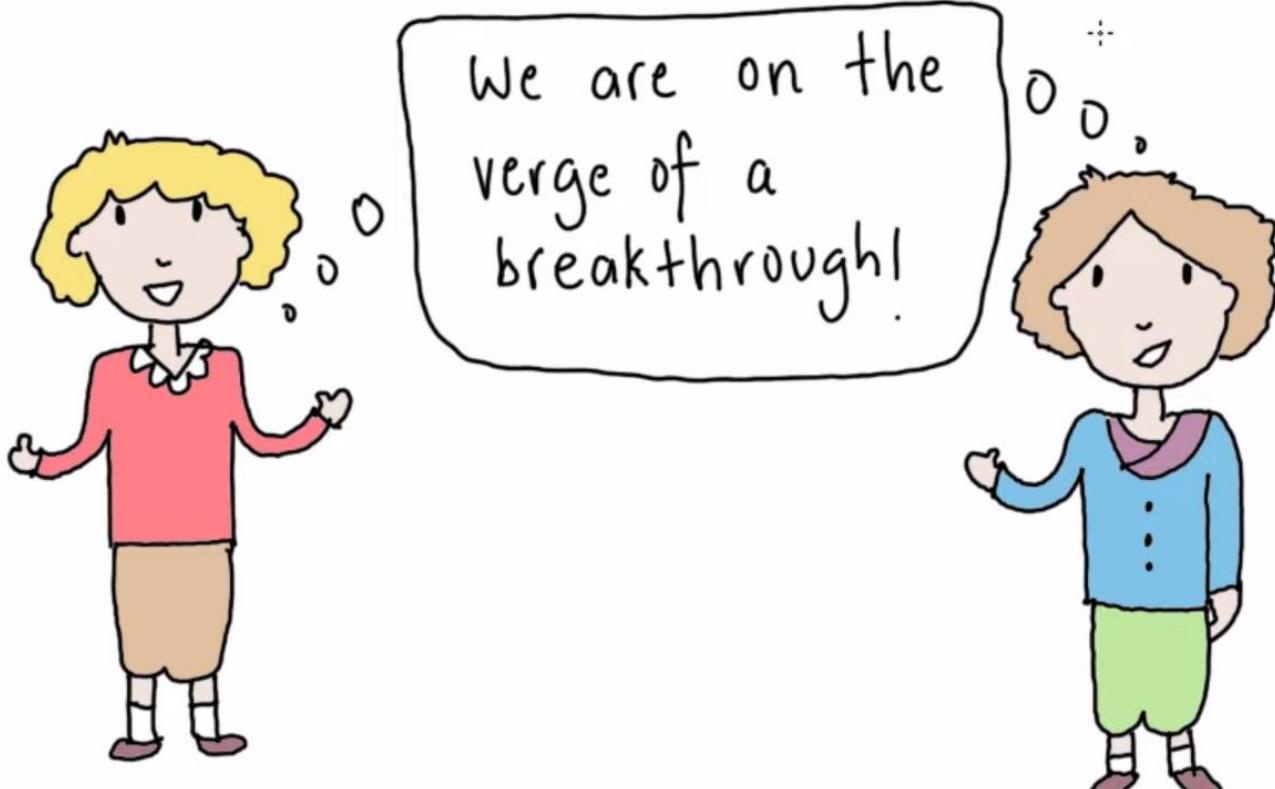

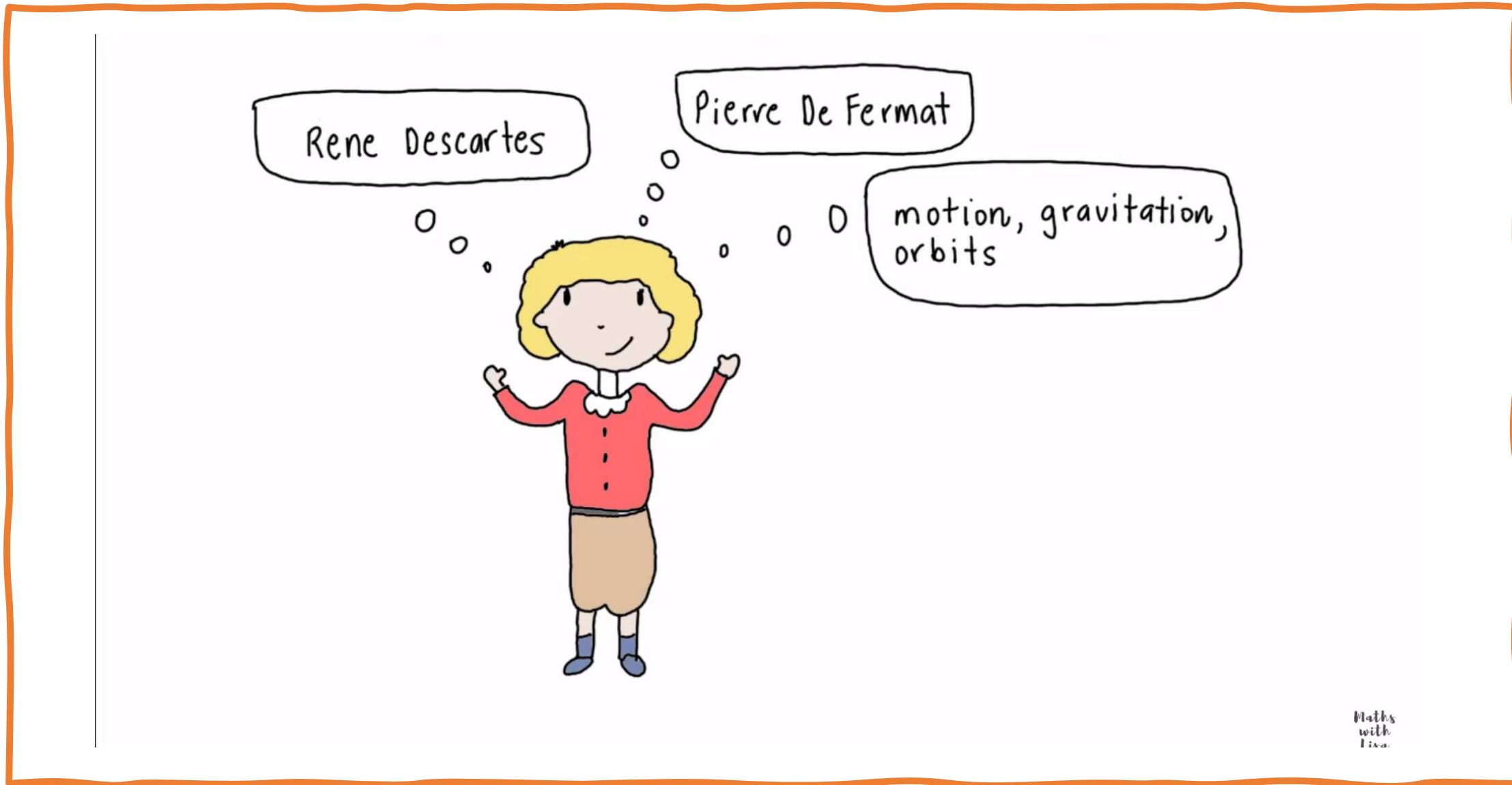

Fundamental Theorem of Calculus

Integration ← → Differentiation
(method of fluxion)
INVERSE OPERATIONS

$$\frac{d}{dx} \frac{4x^3 + x}{12x^2 + 1}$$

$$= 12x^2 + 1$$

$$\int 12x^2 + 1 \, dx$$


$$= \underline{\underline{4x^3 + x + C}}$$

The area of a circle
is πr^2



Greek Mathematics
(static)


Calculus describes
physics

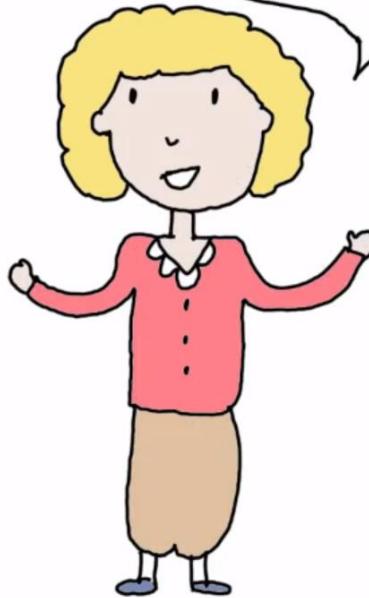



English + European Mathematics
(dynamic)

- motion
- change
- orbits planets
- motion of fluids

1646

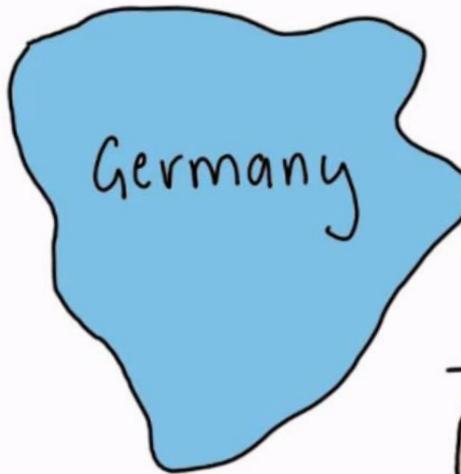


Professor of
moral
philosophy

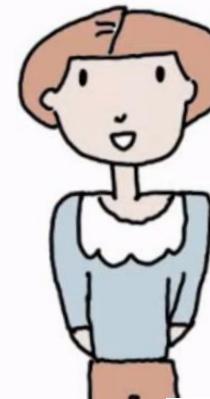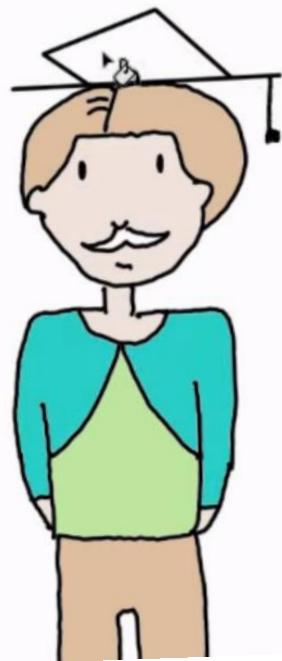

Hi, I'm
Gottfried

Integral Calculus

$$\int_a^b f(x) dx$$

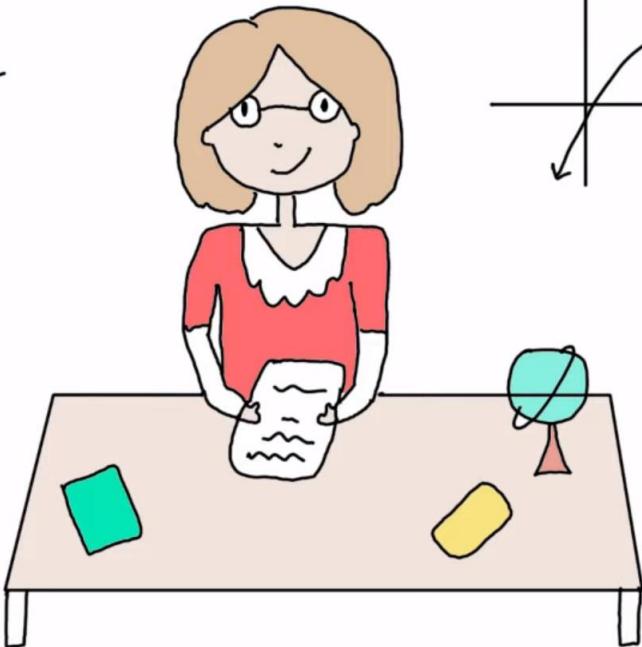


Integration \longleftrightarrow Differentiation




Integration + Differentiation
will be a whole NEW
system of mathematics!

Integral Calculus

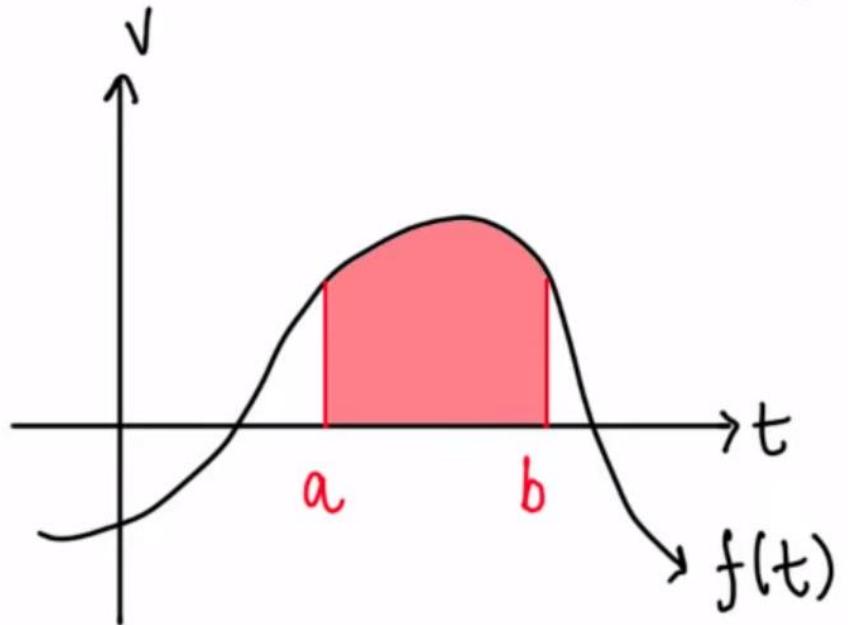

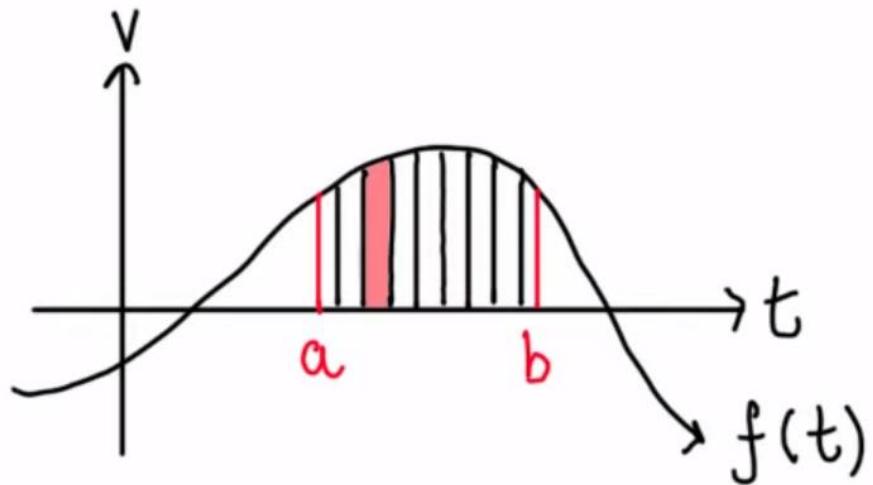
area = distance travelled
(d = primitive of velocity)




width each rectangle $\rightarrow 0$
= exact area under function

Calculus Controversy

I already discovered calculus guys!

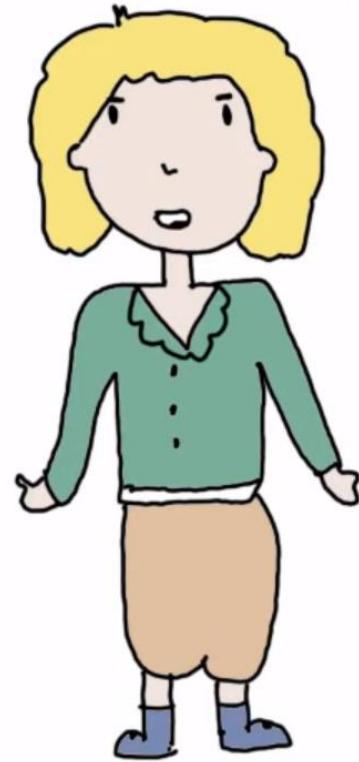


I published my theory of calculus first

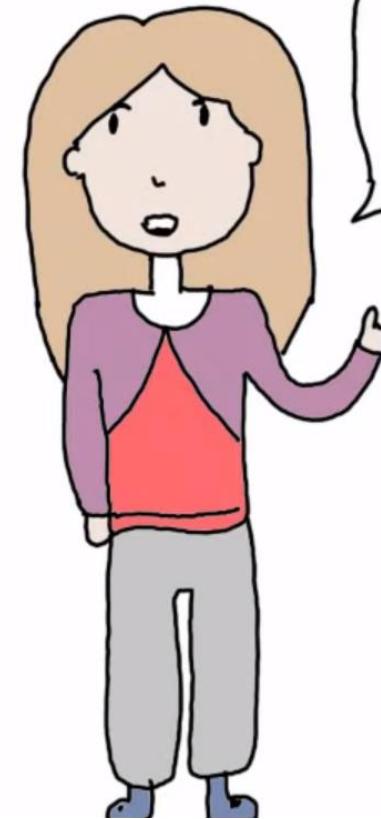


COINVENTORS OF CALCULUS

Discovered
calculus
first

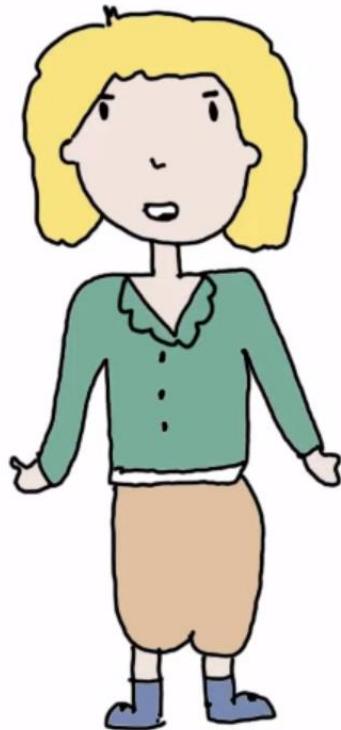

Published the
theory of
calculus
first

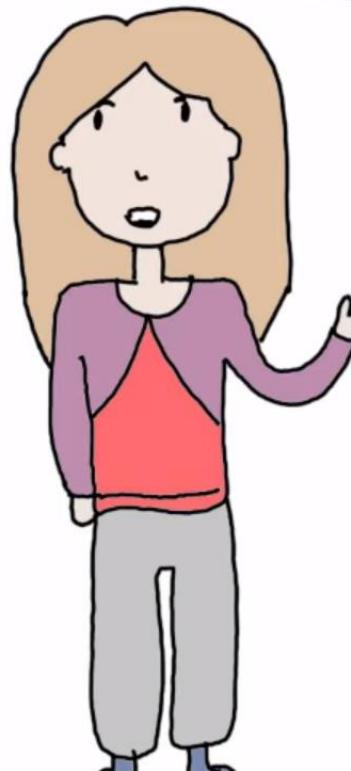

Leibniz's modern notation of calculus


$$\int_a^b f(x) dx = F(b) - F(a)$$

$$\frac{d}{dx} \int_a^x f(t) dt = f(x)$$

$$f'(x) = \lim_{\delta x \rightarrow 0} \left(\frac{\delta y}{\delta x} \right) = \frac{dy}{dx}$$

FUNDAMENTAL THEOREM OF CALCULUS


Calculus Models

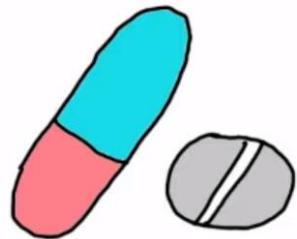

medicine



economics

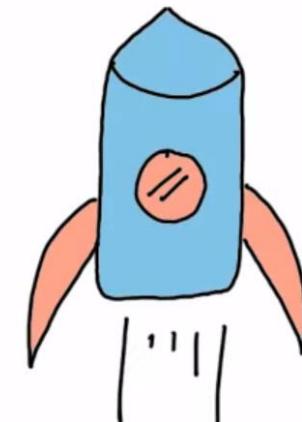


physics/
engineering

GROUP MEMBERS

- 109054. Krishnaraj Thadesar
- 109051. Balraj Tavanandi
- 109056. Tirth Thesiya
- 109052. Arnav Tavergeri
- 109050. Atharva Tanawade
- 109071. Pranav Walvekar
- 109021. Vedant Shirode
- 109060. Ashutosh Ukande

BIBLIOGRAPHY

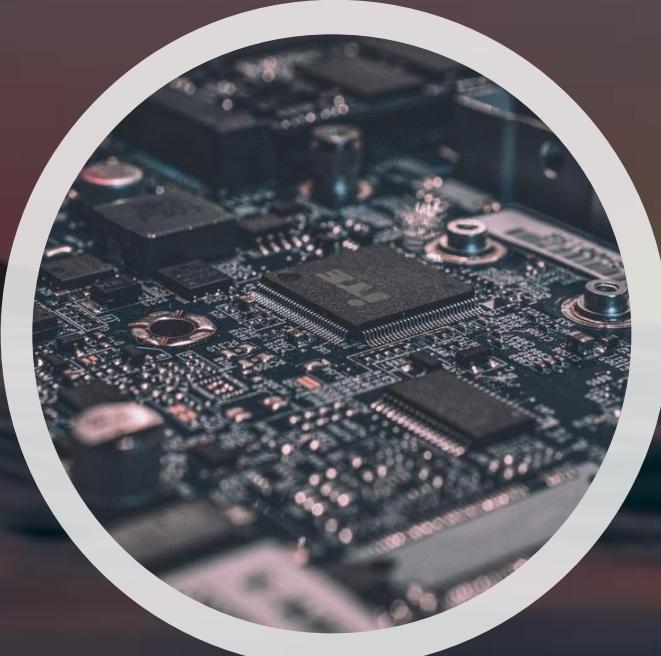- <https://byjus.com/physics/kirchhoffs-law/#:~:text=Kirchhoff's%20voltage%20law%20states%20that,closed%2onetwork%20and%20equals%20zero>.
- <https://www.youtube.com/watch?v=6wb6otcilmQ> History of Calculus by Lisa Math
- https://www.whitman.edu/mathematics/calculus_online/chapter09.html
- <https://www.quora.com/Why-is-the-application-of-integral-calculus-in-physics>



Thank You!