

FY BTech 2021-22

BEEE Lab

Expt No. 3

# **Zener Diode –Voltage Regulator**

Mrs. P. S. Mahajani

School of ECE


MITWPU Pune

## **Expt 6. - Steps involved in the labwork**

- What is a Zener diode?
- Understanding the circuit diagram of a voltage regulator
- How to design the component values ?
- Building a circuit in Tinkercad by selecting components
- Simulate the circuit to take the readings and Complete the observation tables for part 1 & 2
- Calculate Percentage line and load regulation for the circuit

▶ **FIGURE 3-2**

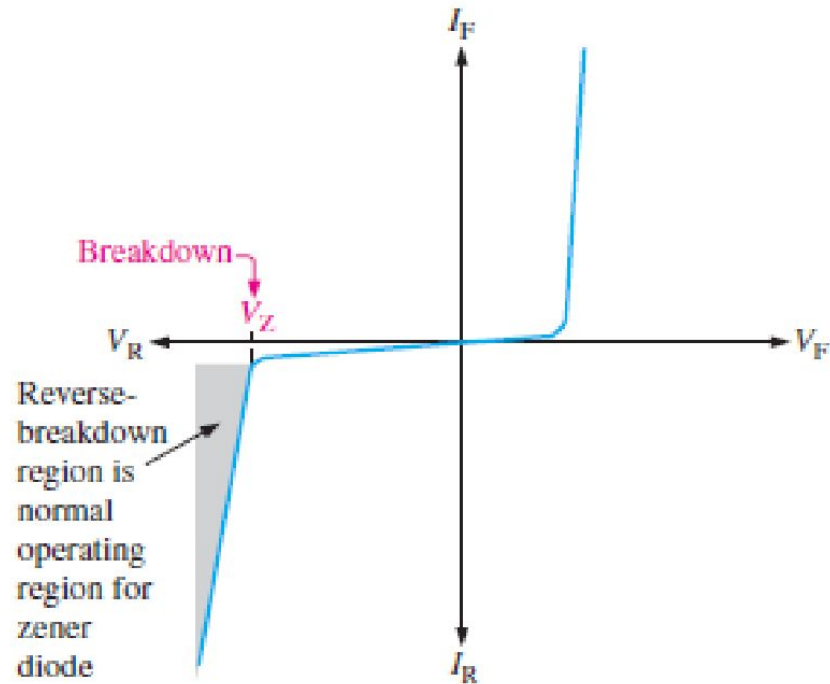
General zener diode  $V$ - $I$  characteristic.




Reverse biased Zener diode behavior

▶ **FIGURE 3-3**

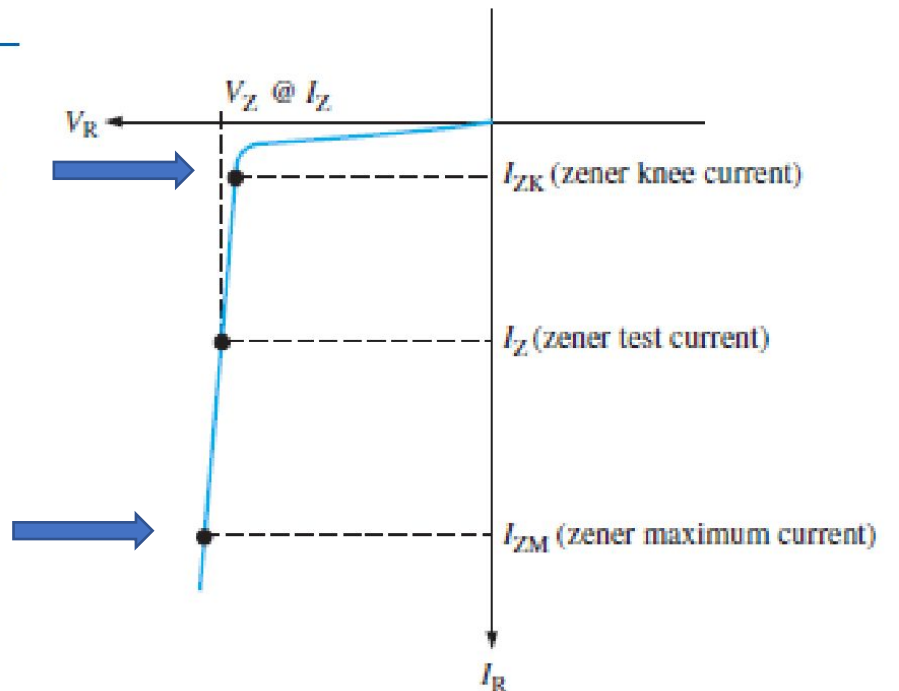
Reverse characteristic of a zener diode.  $V_Z$  is usually specified at a value of the zener current known as the test current.



# Zener Diode Characteristics

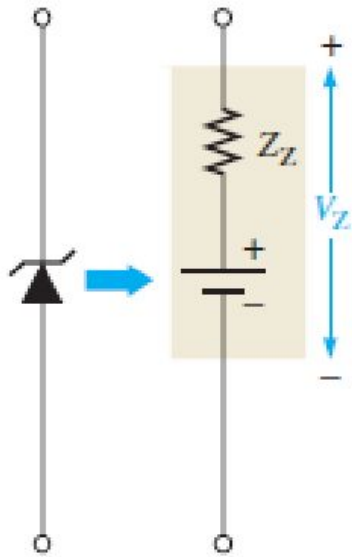

(a) Practical model

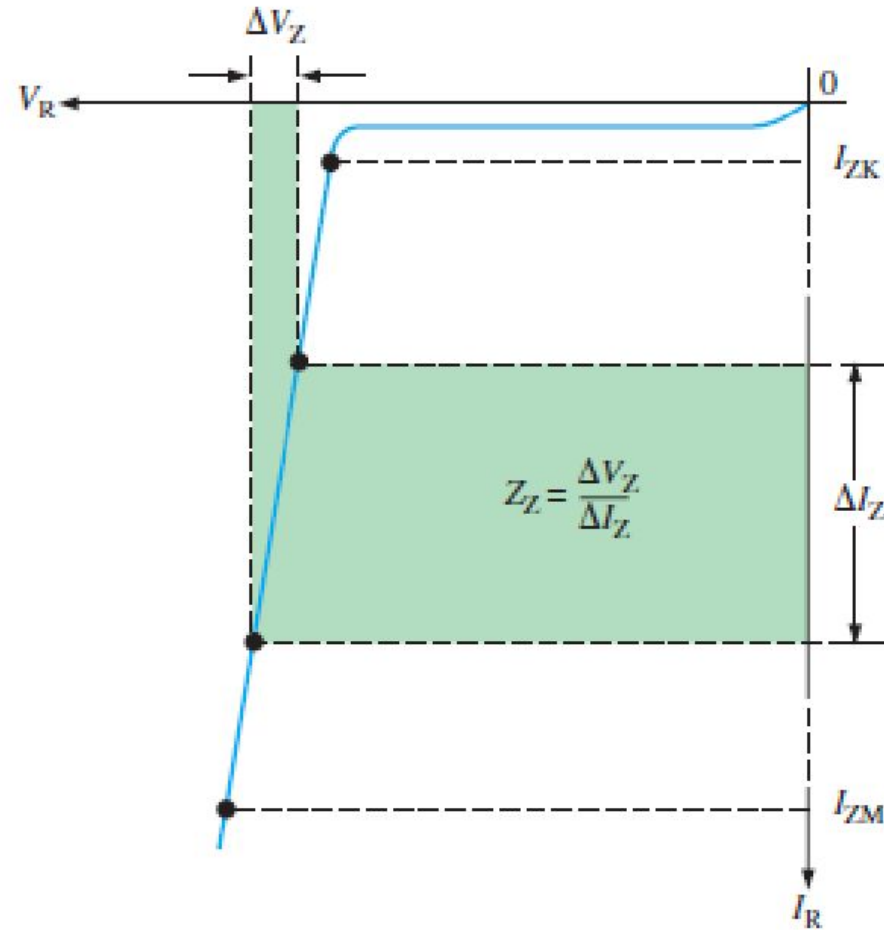

(b) Characteristic curve. The slope is exaggerated for illustration.

◀ FIGURE 3-5

Practical zener diode equivalent circuit and the characteristic curve illustrating  $Z_L$ .

# Datasheet of a Zener diode

## 1N4728A to 1N4764A


Vishay Semiconductors




### Electrical Characteristics

1N4728A...1N4764A

Partnumber	Nominal Zener Voltage <sup>1)</sup>	Test Current	Maximum Dynamic Impedance			Maximum Reverse Leakage Current		Surge Current <sup>3)</sup>	Maximum Regulator Current <sup>2)</sup>
	$V_Z$ at $I_{ZT}$	$I_{ZT}$	$Z_{ZT}$ at $I_{ZT}$	$Z_{ZK}$ at $I_{ZK}$	$I_{ZK}$	$I_R$	Test Voltage $V_R$	at $T_A = 25^\circ\text{C}$ $I_R$	$I_{ZM}$
	V	mA	$\Omega$	$\Omega$	mA	$\mu\text{A}$	V	mA	mA
1N4728A	3.3	76	10	400	1	100	1	1380	276
1N4729A	3.6	69	10	400	1	100	1	1260	252
1N4730A	3.9	64	9	400	1	50	1	1190	234
1N4731A	4.3	58	9	400	1	10	1	1070	217
1N4732A	4.7	53	8	500	1	10	1	970	193
1N4733A	5.1	49	7	550	1	10	1	890	178
1N4734A	5.6	45	5	600	1	10	2	810	162
1N4735A	6.2	41	2	700	1	10	3	730	146
1N4736A	6.8	37	3.5	700	1	10	4	660	133
1N4737A	7.5	34	4	700	0.5	10	5	605	121
1N4738A	8.2	31	4.5	700	0.5	10	6	550	110

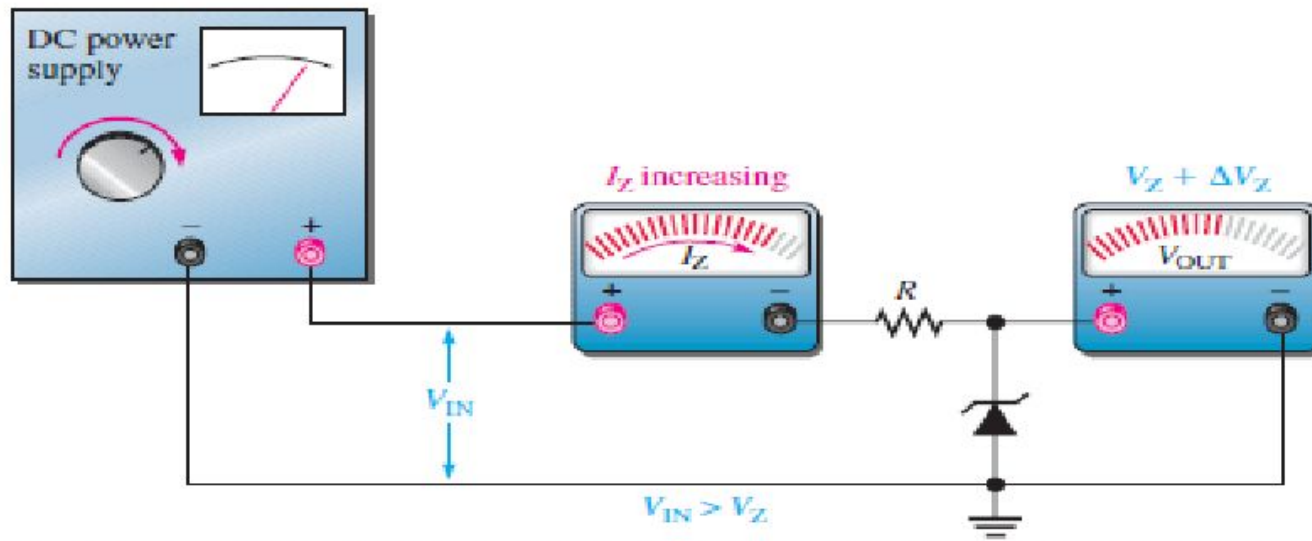

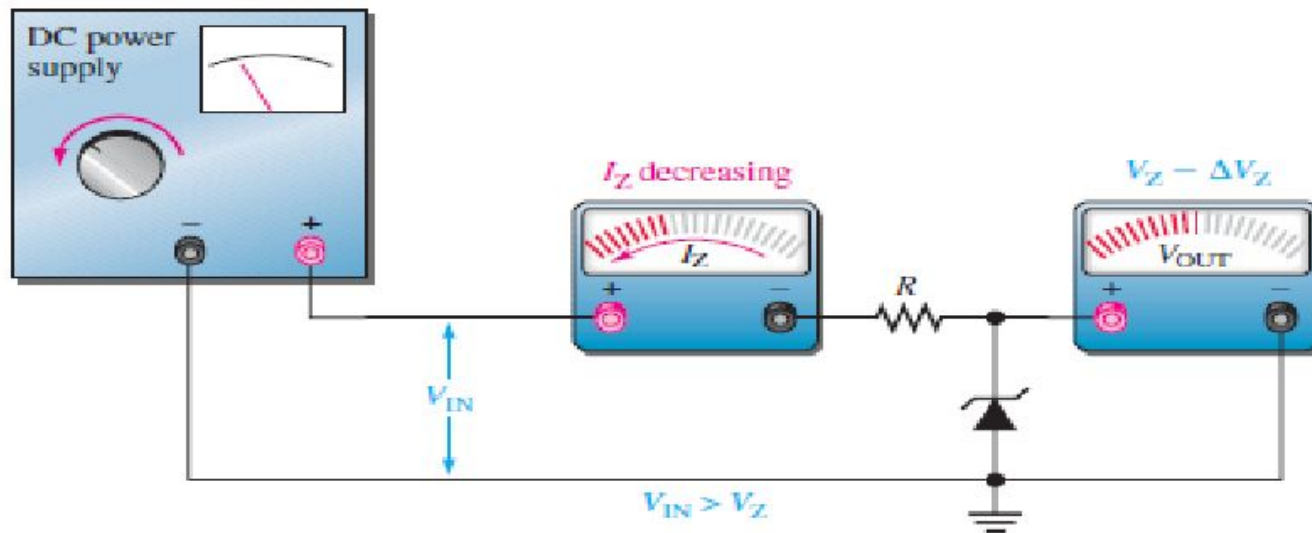(a) As the input voltage increases, the output voltage remains nearly constant ( $I_{ZK} < I_Z < I_{ZM}$ ).




(b) As the input voltage decreases, the output voltage remains nearly constant ( $I_{ZK} < I_Z < I_{ZM}$ ).

FIGURE 3-9


Zener regulation of a varying input voltage.
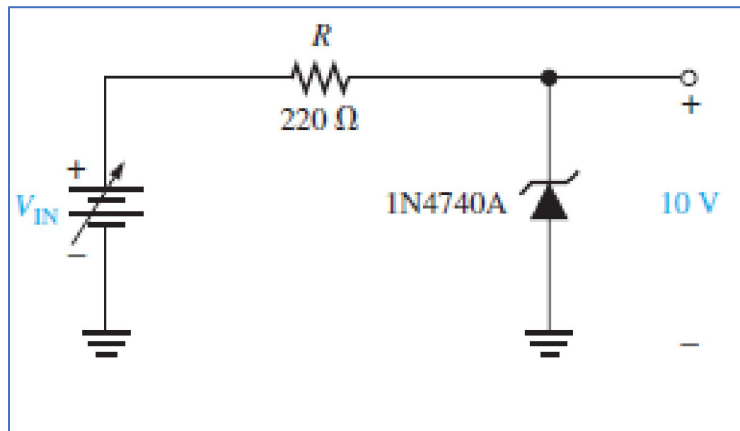
## Zener Regulation with a Variable Input Voltage

Zener diode regulators can provide a reasonably constant dc level at the output, but they are not particularly efficient. For this reason, they are limited to applications that require only low current to the load. Figure 3–9 illustrates how a zener diode can be used to regulate a dc



Load resistance  
 $R_L$  not connected

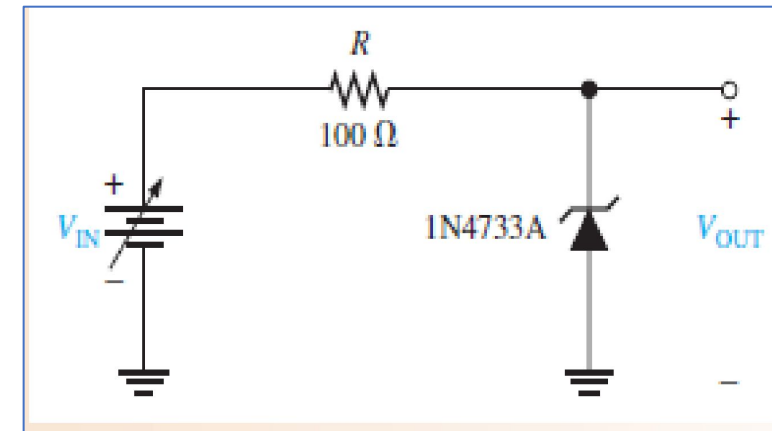


No Load  
condition



## Zener Regulation with a Variable Load

Figure 3–13 shows a zener voltage regulator with a variable load resistor across the terminals. The zener diode maintains a nearly constant voltage across  $R_L$  as long as the zener current is greater than  $I_{ZK}$  and less than  $I_{ZM}$ .

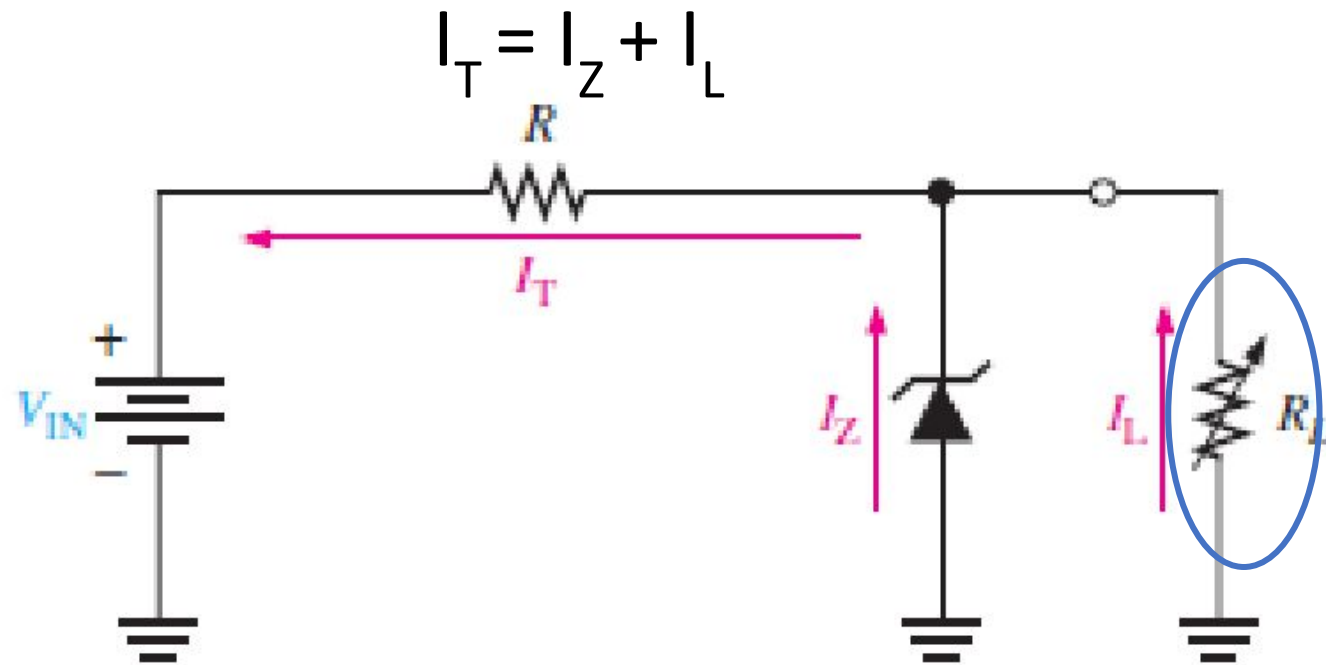


◀ **FIGURE 3–13**

Zener regulation with a variable load.


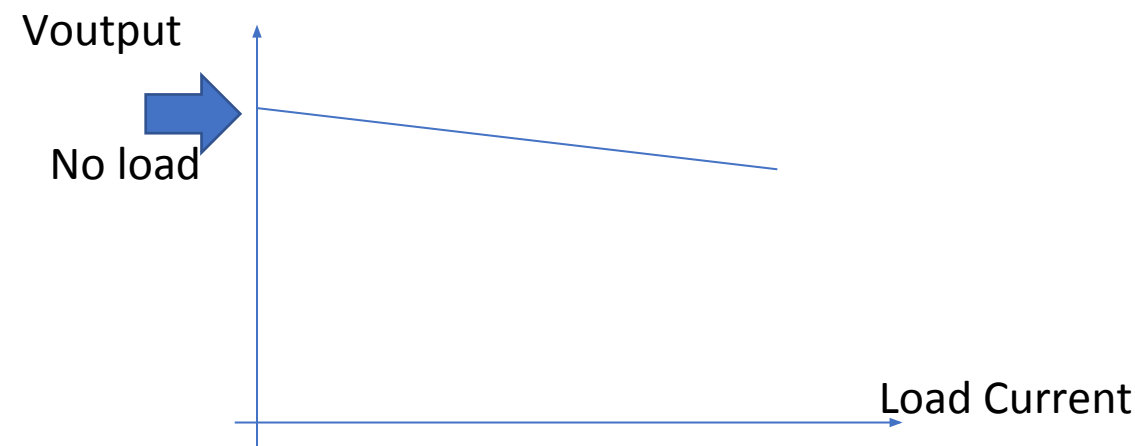
## From No Load to Full Load

When the output terminals of the zener regulator are open ( $R_L = \infty$ ), the load current is zero and *all* of the current is through the zener; this is a no-load condition. When a load resistor ( $R_L$ ) is connected, part of the total current is through the zener and part through  $R_L$ . The total current through  $R$  remains essentially constant as long as the zener is regulating. As  $R_L$  is decreased, the load current,  $I_L$ , increases and  $I_Z$  decreases. The zener diode continues to regulate the voltage until  $I_Z$  reaches its minimum value,  $I_{ZK}$ . At this point the load current is maximum, and a full-load condition exists. The following example will illustrate this.




# Design and simulate Zener regulator for following specifications in Tinkercad

- **Data given:**


$V_Z = 5.1V$ ,  $I_{Zknee} = 1mA$ ,  $I_{Zmax} = 178mA$

$V_{in} = 15V$ ,  $R_S = 220\ \Omega$

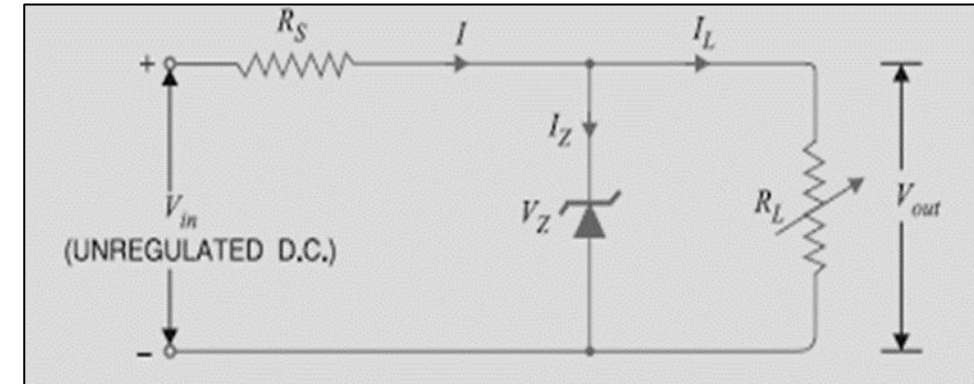

- Part 1: For load regulation , Find  $R_{Lmin}$  and  $R_{Lmax}$
- Part 2: For line regulation with  $R_L = 1.2K\Omega$ , find  $V_{inmin}$  and  $V_{inmax}$
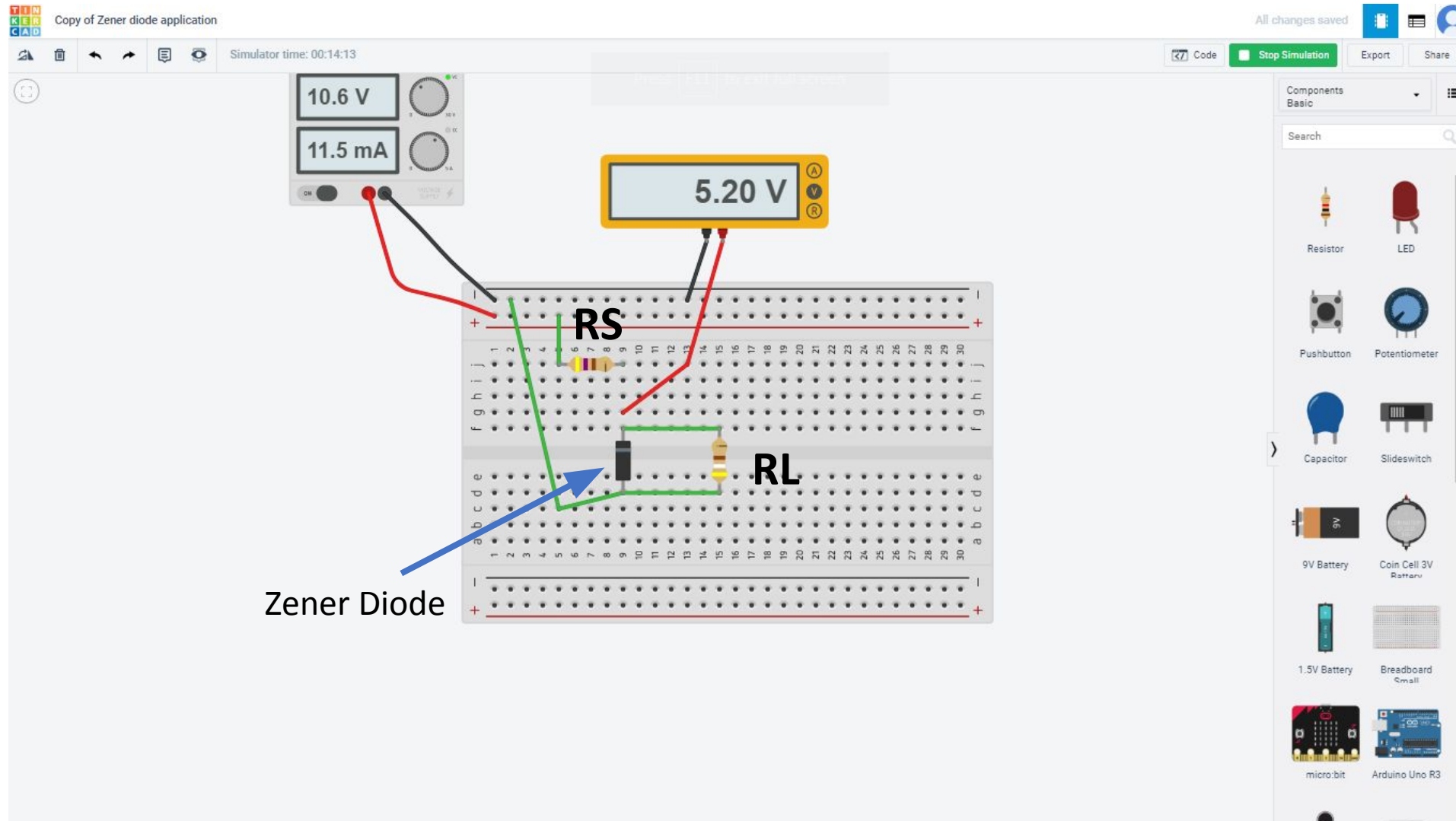
# Tinkercad circuit design for Zener Regulator






# Component List in Tinkercad circuit



TINKERCAD

Copy of Zener diode application

All changes saved



Component List

Press F11 to exit full screen

Download CSV

Name	Quantity	Component
P1	1	10.6 , 3 Power Supply
Meter1	1	Voltage Multimeter
UZener diode	1	5.1 V Zener Diode
R1	1	470 $\Omega$ Resistor
R2	1	490 $\Omega$ Resistor


# Load Regulation by changing $R_L$

Note down output voltage and  $I_L$  for 5 different values of  $R_L$  with a constant  $V_{in}$

Sr. No	$I_L$ (mA)	$V_o$ (V)	$R_L$ ( $\Omega$ )
1	$I_{L1} =$	$V_{o1} =$	
2	$I_{L2} =$	$V_{o2} =$	
3	$I_{L3} =$	$V_{o3} =$	
4	$I_{L4} =$	$V_{o4} =$	
5	$I_{L5} =$	$V_{o5} =$	

Percentage Load Regulation
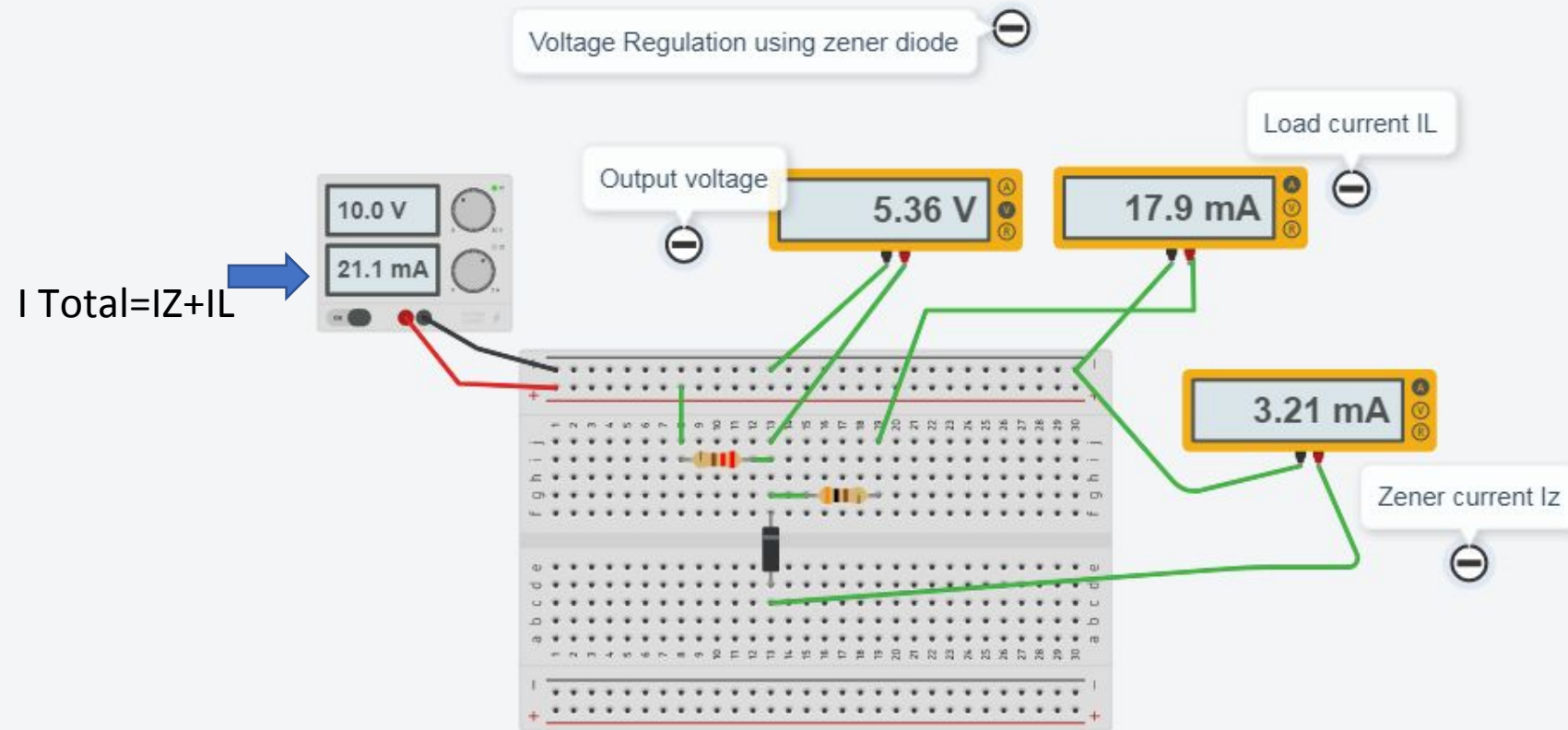
$$\% \text{ Load regulation} = (V_{NL} - V_{FL}) / V_{FL} \times 100$$



# Observations for load and line regulation

**For Load regulation:**  $V_{in} = \underline{\hspace{2cm}}$  (Constant)

Sr. No	$I_L$ (mA)	$V_o$ (V)	$R_L$ ( $\Omega$ )
1	$I_{L1} =$	$V_{o1} =$	
2	$I_{L2} =$	$V_{o2} =$	
3	$I_{L3} =$	$V_{o3} =$	
4	$I_{L4} =$	$V_{o4} =$	
5	$I_{L5} =$	$V_{o5} =$	

**Plot a graph for  
 $V_o$  vs  $I_L$**

**For Line regulation:**  $R_L = \underline{\hspace{2cm}}$  (Constant)

Sr. No	$V_{in}$ (V)	$V_o$ (V)
1	$V_{in1} =$	$V_{o1} =$
2	$V_{in2} =$	$V_{o2} =$
3	$V_{in3} =$	$V_{o3} =$
4	$V_{in4} =$	$V_{o4} =$
5	$V_{in5} =$	$V_{o5} =$



**Plot a graph for  
 $V_o$  vs  $V_{in}$**



23-11-20

# Zener Regulator in Tinkercad Load Regulation

$R_L$	$I_L$ (mA)	$V_L = V_{\text{output}}$	$I_Z$
$115 + 250 \Omega$	44.5	5.14	0.3 mA
$115 + 270 \Omega$	42.1	5.29	2.04 mA
$115 + 300 \Omega$	41.6	5.31	2.4
$115 + 400 \Omega$	40.7	5.36	3.11
$115 + 500 \Omega$	39.8 mA	5.4	3.8 mA
$115 + 700 \Omega$	38.2	5.48	5.11
$115 + 1K$	35.9	5.58	6.89 mA
	12.9 mA		25.2 mA

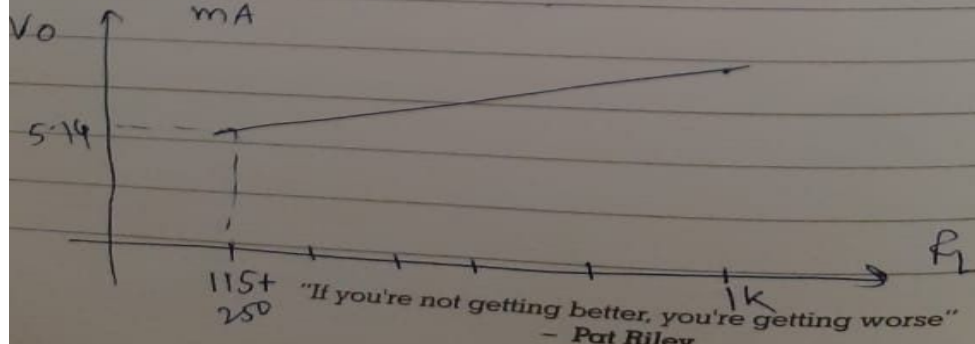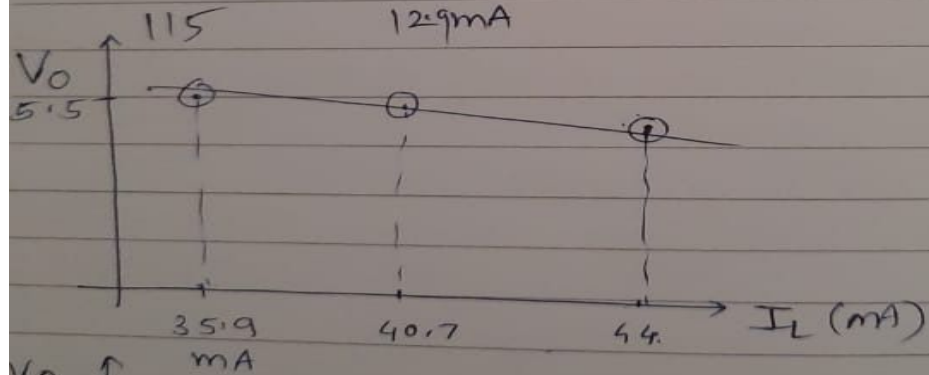

"If you're not getting better, you're getting worse"  
- Pat Riley

# What is Line Regulation?

- Line Regulation is the change in output voltage due to variation of the input voltage with all other factors held constant. It is expressed as a percent of the nominal output voltage. A power supply with tight line regulation delivers optimum voltages throughout the operating range.
- The line regulation gives the ability of a power supply to maintain the specified output voltage despite the changes or variations in the input line voltage. The value is calculated from the ratio of the change in the output voltage to the change in the input voltage, but usually expressed as a percentage:
- Line Regulation =  $\Delta V_o / \Delta V_i$

# Calculations

- 1. Percentage Line Regulation

$$\% \text{ Line Regulation} = (\Delta V_o / \Delta V_{in}) \times 100$$

- 2. Percentage Load Regulation

$$\% \text{ Load regulation} = (V_{NL} - V_{FL}) / V_{FL} \times 100$$

Thank You!