

FY BTech

BEEE Expt No. 5


BEEE Expt 5 OPAMP

Tinkercad simulation- Two circuits

- Inverting Amplifier
- Noninverting amplifier

IC 741

LM741 Pinout Diagram

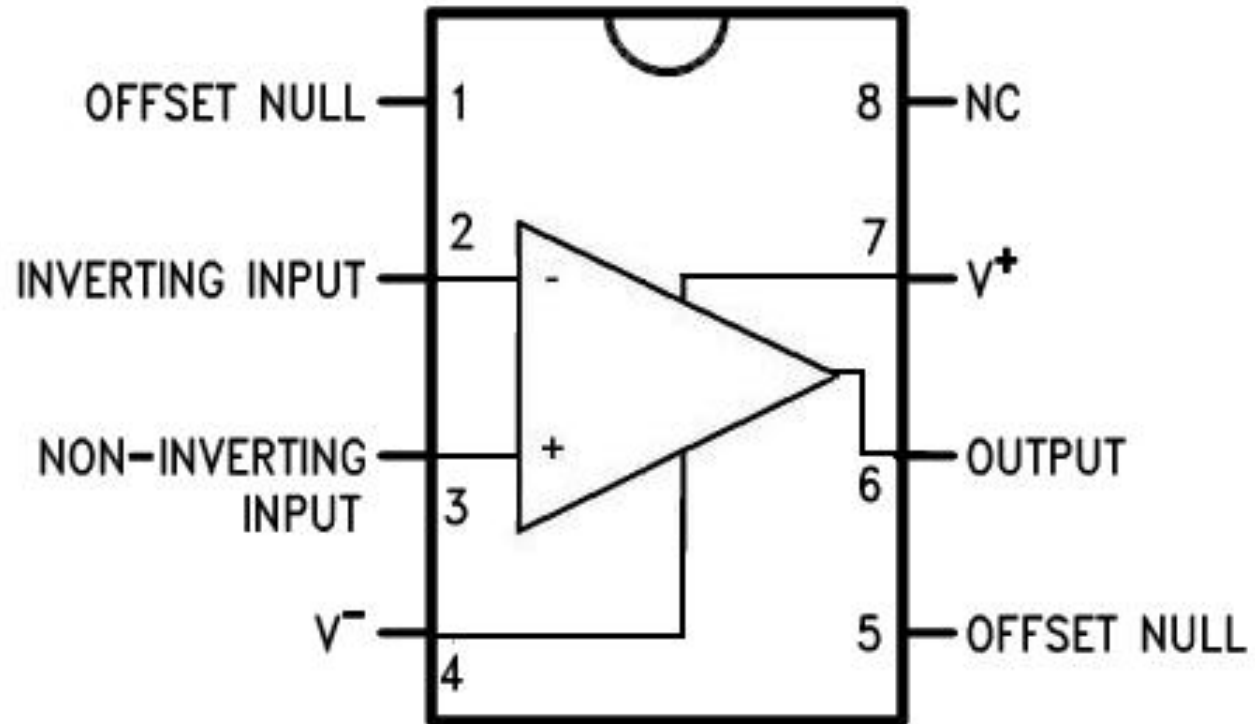


Dual power supply- $+V_s$ and $-V_s$

- 12 V and -12 V

Noninverting Amplifier


- An op-amp connected in a closed-loop configuration as a noninverting amplifier with a controlled amount of voltage gain is shown in Figure.
- The input signal is applied to the noninverting (+) input.
- The output is applied back to the inverting input through the feedback circuit (closed loop) formed by the input resistor R_i and the feedback resistor R_f .
- This creates negative feedback as: Resistors R_i and R_f form a voltage-divider circuit, which reduces V_{out} and connects the reduced voltage V_f to the inverting input.

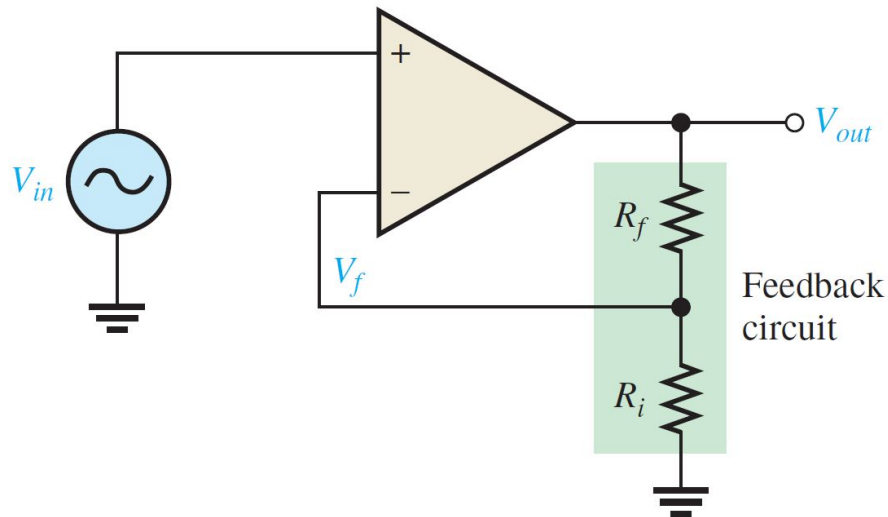


The feedback voltage is expressed as

$$V_f = \left(\frac{R_i}{R_i + R_f} \right) V_{out}$$

Noninverting amplifier with DC input

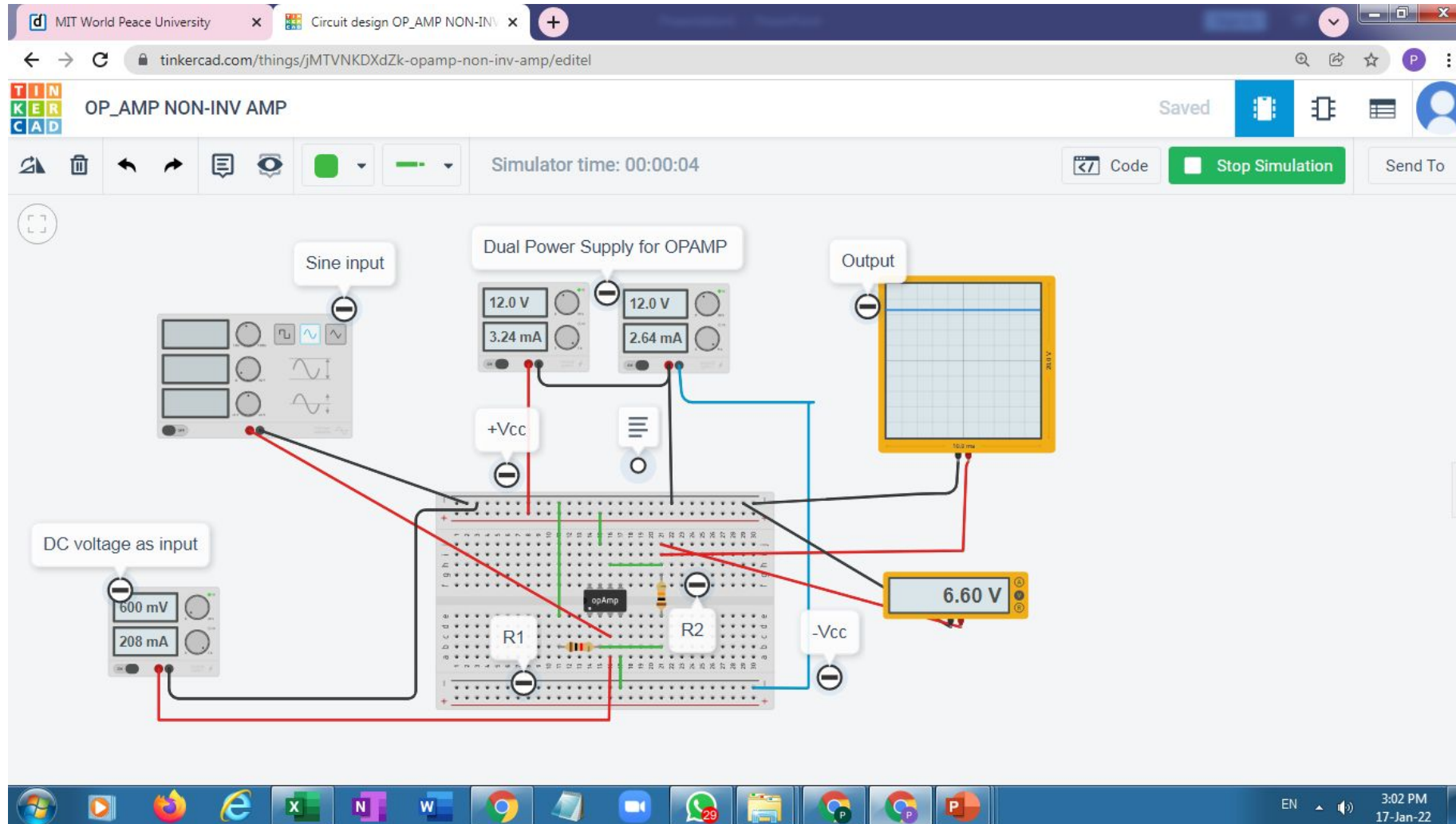



Non inverting amplifier with AC input

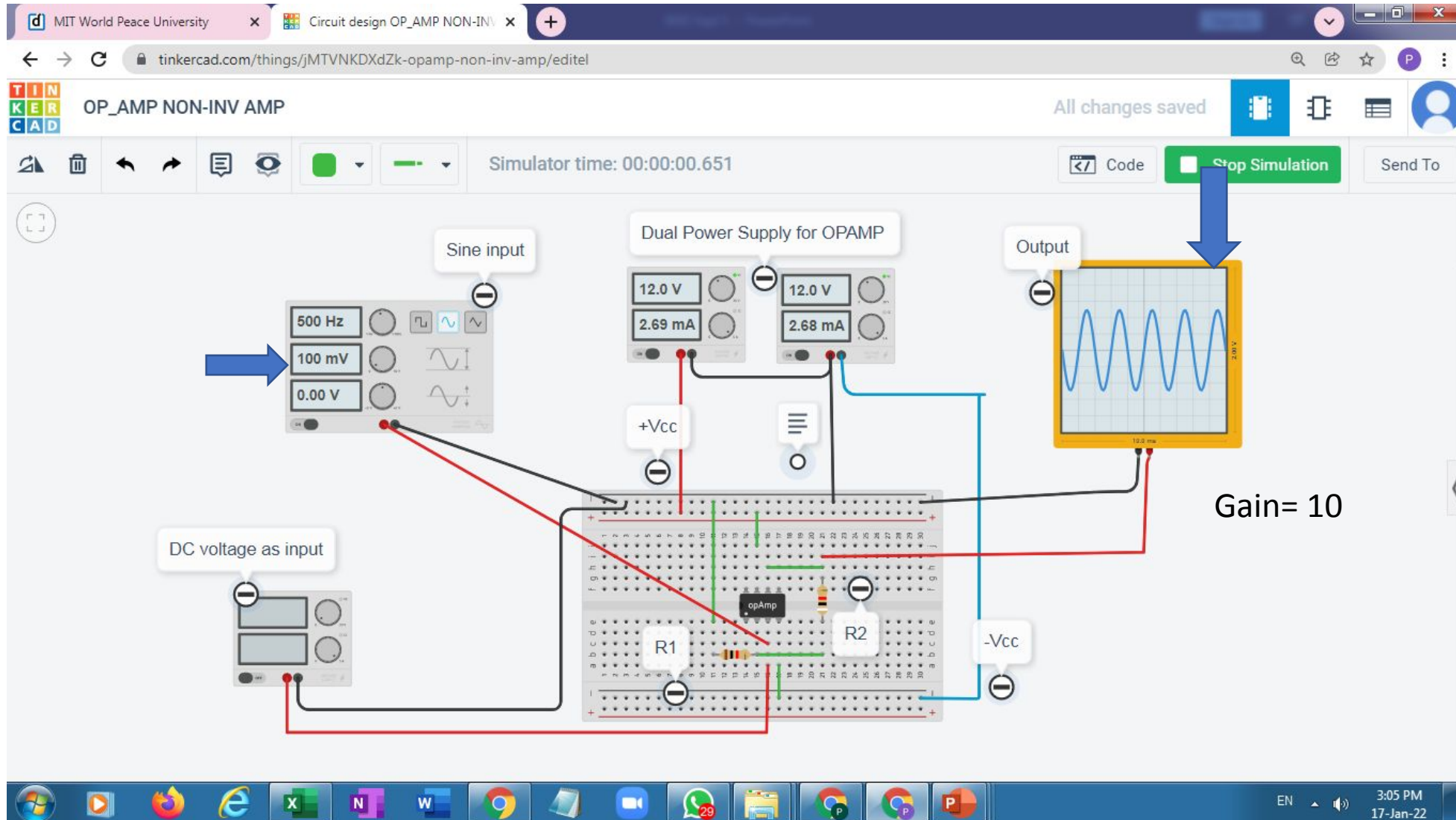

Inverting Amplifier

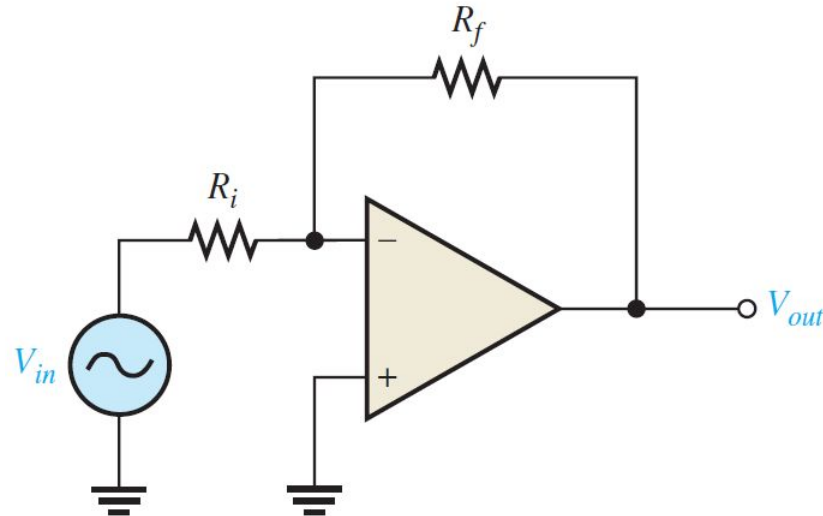- An op-amp connected as an inverting amplifier with a controlled amount of voltage gain is shown in Figure
- The input signal is applied through a series input resistor R_i to the inverting (-) input.
- Also, the output is fed back through R_f to the same input. The noninverting (+) input is grounded.



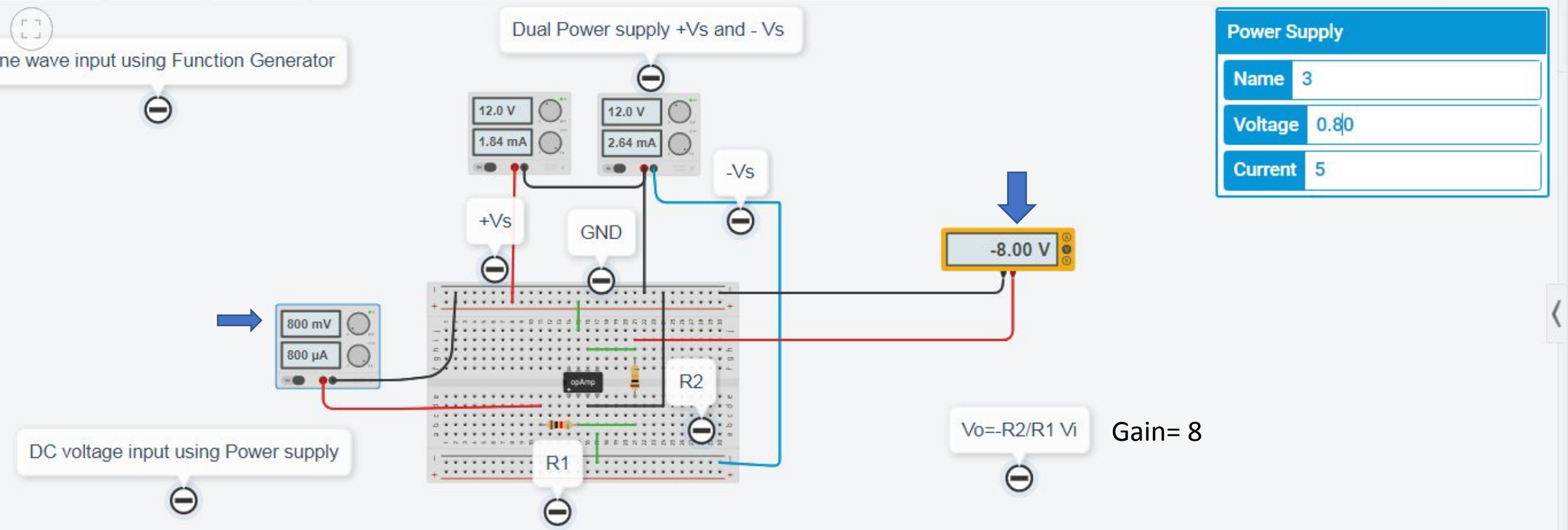

Power Supply	
Name	3
Voltage	0.80
Current	5

Observation table

1. Inverting Amplifier(AC input)

Sr. No.	Input Voltage V_{in}	R_1	R_2	Output Voltage V_o	Gain (Practical) V_o / V_{in}	Gain (Theoretical) $-R_2 / R_1$
1						
2						
3						

2. Inverting Amplifier(DC input)

Sr. No.	Input Voltage V_i (DC)	R_1	R_2	Output Voltage V_o	Gain (Practical) V_o / V_{in}	Gain (Theoretical) $-R_2 / R_1$
1						
2						
3						
4						
5						

Observation Table

.Non-Inverting Amplifier (AC Input)

Sr. No.	Input Voltage $V_{in(AC)}$	R_1	R_2	Output Voltage V_o	Gain (Practical) V_o / V_{in}	Gain (Theoretical) $1 + (R_2 / R_1)$
1						
2						
3						

4.Non-Inverting Amplifier (DC Input)

Sr. No.	Input Voltage V_{in}	R_1	R_2	Output Voltage V_o	Gain (Practical) V_o / V_{in}	Gain (Theoretical) $1 + (R_2 / R_1)$
1						
2						
3						

Conclusion